

Group Number:

NAMES (FIRST AND LAST NAME):

In-Class Assignment 2

ELEN 21/COEN 21 – Fall 2022

Instructor: Maria Kyrarini

Date: 10/18/2022

Time: 1 hour and 30 minutes

Number of Problems: 4

Important Notes:

- Be sure to read all the problems carefully and answer all questions.
- Be sure to answer all parts of each question.
- **Submit only one answer for each question.**
- Multiple solutions for one question will not be graded.
- **Clearly SHOW and EXPLAIN all the steps of your work.**
- **Answers without detailed explanations will NOT be graded (excluding Problem 1).**
- The Engineering School Honor Code applies.

Problem 1 (20 points)

True/False questions – Circle the correct answer (**no explanation is needed**).


i. The decimal value of the following 2's complement number 10010011 is -115.	True/False
ii. Latch is an edge-sensitive device, while Flip-flop is a level-sensitive device.	True/False
iii. An arithmetic logic unit (ALU) is a digital circuit used to perform only arithmetic operations.	True/False
iv. A D-flip flop and a NOT gate are only needed to implement a T-flip flop.	True/False
v. We wrote our full names and our group number on page 1.	True/False

Problem 2 (40 points)

For the following sequential circuit, do the following:


- Write the truth table. [10 points]
- Redesign this circuit by replacing the T_1 Flip-Flop with negative edge D Flip-Flop, the T_0 Flip-Flop with negative edge JK Flip-Flop and a minimal AND-OR-NOT-XOR gate network. [20 points]
- Draw the circuit you have redesigned. [10 points]

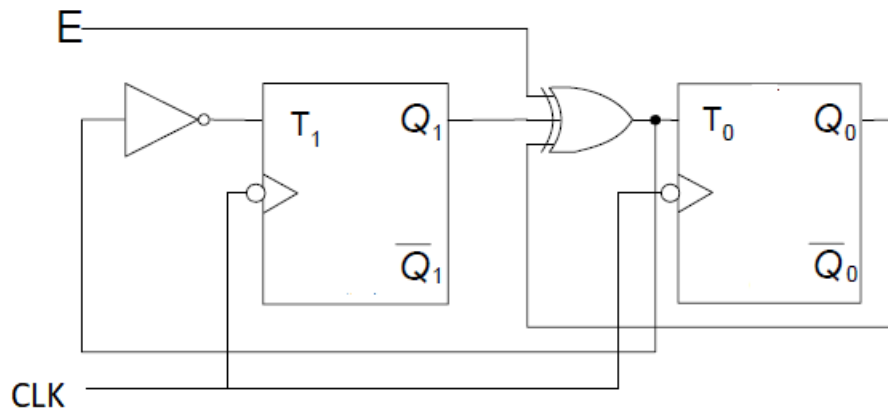Reminder: $x \oplus y = \bar{x} \cdot \bar{y} + x \cdot y$



Problem 3 (20 points)

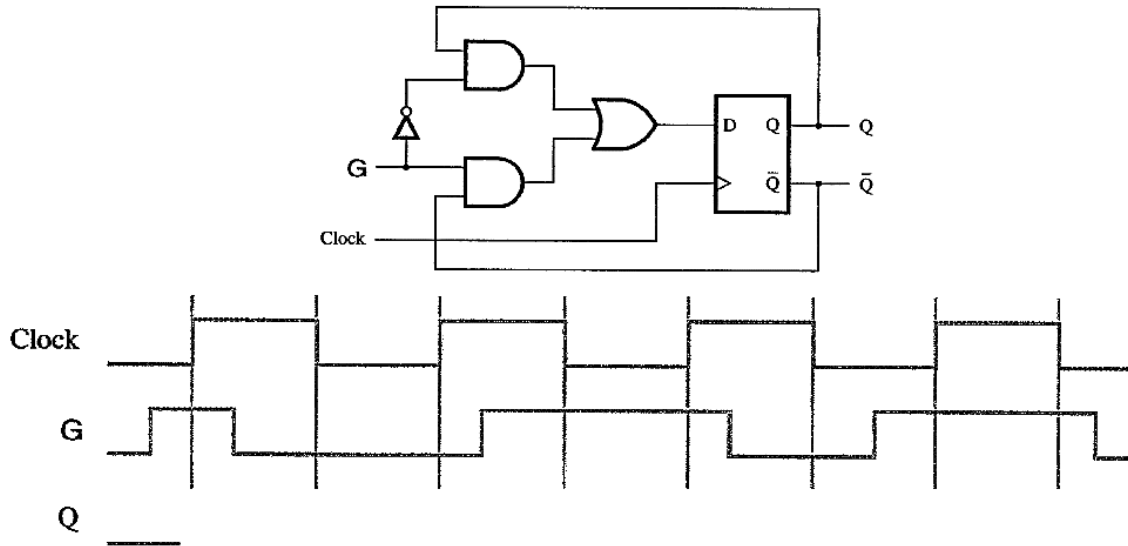- a) Draw the timing diagram of the output Q of the following circuit. Consider that initially $Q = 0$. (15 points)
- b) What circuit is this? (5 points)



Problem 4 (20 points)

The following two signed 2's complement numbers are given: $A = 1001\ 0111\ 0101$ and $B = 1100\ 1001\ 0110$.

- (a) Subtract number A from number B and show the result. DO NOT use decimal equivalents. [10 points]
- (b) Is the result correct? Explain your answer. [10 points]

Boolean Algebra Properties

5a.	$x \cdot 0 = 0$	10a.	$x \cdot y = y \cdot x$	<i>Commutative</i>
5b.	$x + 1 = 1$	10b.	$x + y = y + x$	
6a.	$x \cdot 1 = x$	11a.	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	<i>Associative</i>
6b.	$x + 0 = x$	11b.	$x + (y + z) = (x + y) + z$	
7a.	$x \cdot x = x$	12a.	$x \cdot (y + z) = x \cdot y + x \cdot z$	<i>Distributive</i>
7b.	$x + x = x$	12b.	$x + y \cdot z = (x + y) \cdot (x + z)$	
8a.	$x \cdot \bar{x} = 0$	13a.	$x + x \cdot y = x$	<i>Absorption</i>
8b.	$x + \bar{x} = 1$	13b.	$x \cdot (x + y) = x$	
9.	$\bar{\bar{x}} = x$	14a.	$x \cdot y + x \cdot \bar{y} = x$	<i>Combining</i>
		14b.	$(x + y) \cdot (x + \bar{y}) = x$	
		15a.	$\overline{x \cdot y} = \bar{x} + \bar{y}$	<i>DeMorgan's theorem</i>
		15b.	$\overline{x + y} = \bar{x} \cdot \bar{y}$	
		16a.	$x + \bar{x} \cdot y = x + y$	
		16b.	$x \cdot (\bar{x} + y) = x \cdot y$	
		17a.	$x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$	<i>Consensus</i>
		17b.	$(x + y) \cdot (y + z) \cdot (\bar{x} + z) = (x + y) \cdot (\bar{x} + z)$	