

Homework 5

ELEN 21/COEN 21

Instructor: Maria Kyrarini

1. A universal shift register can shift in both the left-to-right and right-to-left directions, and it has parallel-load capability. Draw a circuit for such a 4-bit universal shift register.

Hint:

S1	S0	Selection Mode
0	0	Hold
0	1	Shift Left
1	0	Shift Right
1	1	Parallel Load