

# Electric Circuits I

## Laboratory 4 – Network Analysis and Wheatstone Bridge

### Objective:


- To verify experimentally the function of a resistive network.
- To verify experimentally the operation of a typical bridge circuit to measure the resistance of unknown resistors.
- To apply the Wheatstone Bridge to various applications.


### I. Equipment:

- DC Power Supply (Keysight EDU36311A)
- Digital Multimeter (Keysight EDU34450A)
- 5 unknown resistors from TA
- Breadboard for connecting resistors
- Resistance Decade  $R_{adj}$



- Two resistors,  $R_1$  and  $R_2$ , are between 1kΩ to 10kΩ.

Thermistor	<p>Photoresistor</p> 
------------	--

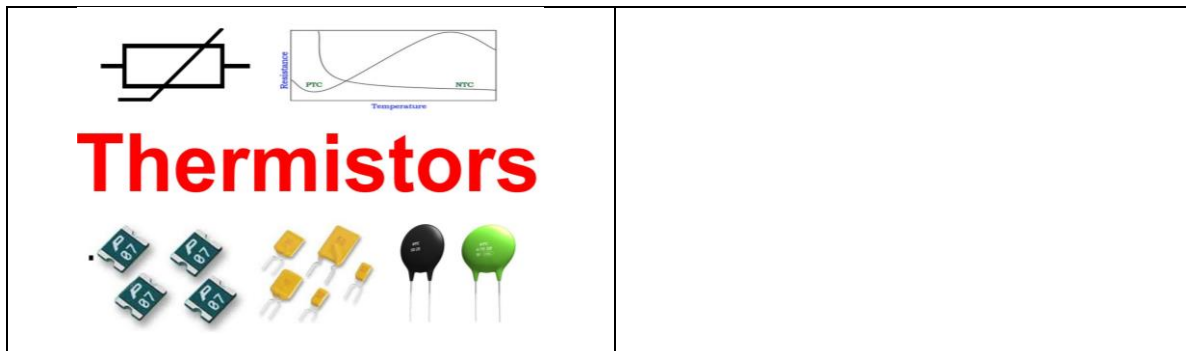

## II. Background & Theory

### A. Resistive Networks

We can quickly analyze a resistive network by combining series and parallel resistors. With Ohm's law, we can determine other voltages across or currents going through elements using voltage or current division.

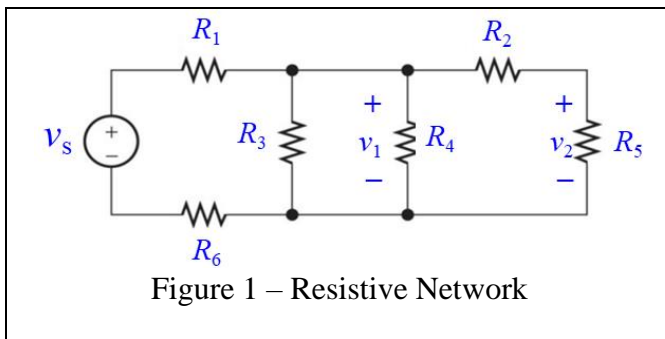


Figure 1 – Resistive Network

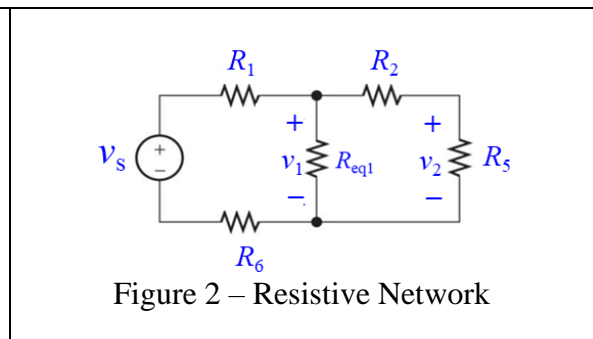


Figure 2 – Resistive Network

**Figure 1** and **Figure 2** show an example of a resistive network where we need to determine the voltages  $v_1$  and  $v_2$  based on the known values of resistors and the supply voltage  $v_s$ . In **Figure 2**, we combine two parallel resistors  $R_3$  and  $R_4$  into an equivalent resistor  $R_{eq1}$ :

$$R_{eq1} = R_3 || R_4$$

We can temporarily combine series and parallel resistors in **Figure 2** as,


$$R_{eq2} = R_{eq1} || (R_2 + R_5)$$

From there, we can apply voltage division to determine  $v_1$  and  $v_2$ :

$$v_1 = \left( \frac{R_{eq2}}{R_1 + R_{eq2} + R_6} \right) v_s,$$

$$v_2 = \left( \frac{R_5}{R_2 + R_5} \right) v_1.$$

## B. Wheatstone Bridge

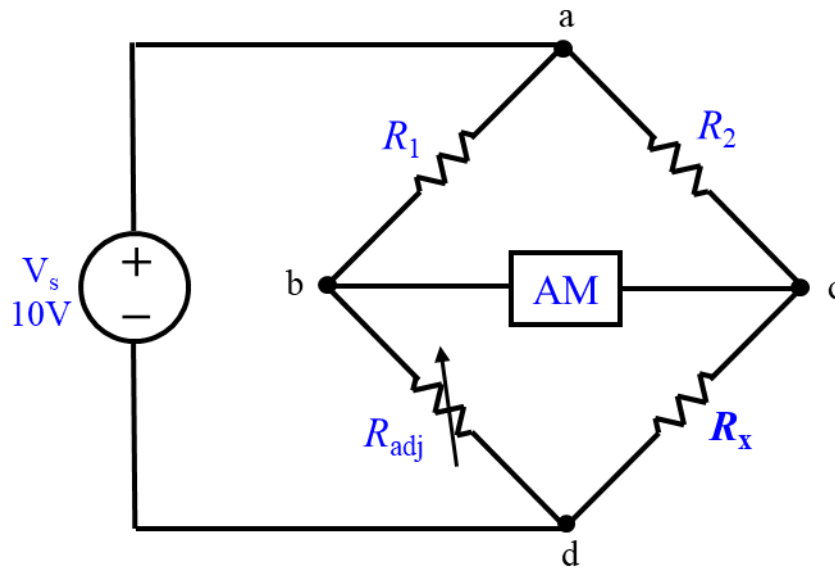

**Figure 3** – Wheatstone Bridge

The circuit diagram of a Wheatstone bridge is shown in **Figure 3**. In the circuit,  $R_x$  is a known resistor, and  $R_{adj}$  is an adjustable resistor. An ammeter (AM) measures the current between nodes b and c ( $I_{bc}$ ).  $R_{adj}$  is adjusted until the ammeter shows zero ( $I_{bc} = 0A$ ) or the bridge is balanced. The unknown  $R_x$  is calculated as:

$$\begin{aligned} V_{ab} &= V_{ac} \\ V_{bd} &= V_{cd} \\ \frac{V_{ab}}{V_{bd}} &= \frac{V_{cd}}{V_{cd}} \Leftrightarrow \frac{R_1 I_{R1}}{R_{adj} I_{R1}} = \frac{R_2 I_{R2}}{R_x I_{R2}} \Leftrightarrow \frac{R_1}{R_{adj}} = \frac{R_2}{R_x} \\ \Rightarrow R_x &= \left( \frac{R_2}{R_1} \right) R_{adj} \quad (1) \end{aligned}$$

## III. Prelab Assignment:

*The prelab assignments should be completed and submitted to Camino before the lab.*

1. Select 6 resistors ( $R_1$  to  $R_6$ ) from the standard resistor values in **Table 1** between  $1k\Omega$  to  $20k\Omega$ .
1. With  $v_s = 12V$ , create a MATLAB script to
  - a. calculate the voltages  $v_1$  and  $v_2$  in **Figure 1**.
  - b. calculate the currents going through  $R_4$  and  $R_5$  ( $i_{R_4}$  and  $i_{R_5}$ ) in **Figure 1**.
  - c. calculate the dissipated power in  $R_4$  and  $R_5$  ( $P_{R_4}$  and  $P_{R_5}$ ) in **Figure 1**.

**Table 1 – Standard Resistor Values (K = \* 1e3, M = \*1e6)**

1.0	5.6	33	160	820	3.9K	20K	100K	510K	2.7M
1.1	6.2	36	180	910	4.3K	22K	110K	560K	3M
1.2	6.8	39	200	1K	4.7K	24K	120K	620K	3.3M
1.3	7.5	43	220	1.1K	5.1K	27K	130K	680K	3.6M
1.5	8.2	47	240	1.2K	5.6K	30K	150K	750K	3.9M
1.6	9.1	51	270	1.3K	6.2K	33K	160K	820K	4.3M
1.8	10	56	300	1.5K	6.6K	36K	180K	910K	4.7M
2.0	11	62	330	1.6K	7.5K	39K	200K	1M	5.1M
2.2	12	68	360	1.8K	8.2K	43K	220K	1.1M	5.6M
2.4	13	75	390	2K	9.1K	47K	240K	1.2M	6.2M
2.7	15	82	430	2.2K	10K	51K	270K	1.3M	6.8M
3.0	16	91	470	2.4K	11K	56K	300K	1.5M	7.5M
3.3	18	100	510	2.7K	12K	62K	330K	1.6M	8.2M
3.6	20	110	560	3K	13K	68K	360K	1.8M	9.1M
3.9	22	120	620	3.2K	15K	75K	390K	2M	10M
4.3	24	130	680	3.3K	16K	82K	430K	2.2M	15M
4.7	27	150	750	3.6K	18K	91K	470K	2.4M	22M
5.1	30								

**IV. Laboratory Part 1 – Resistive Network**

1. Use the digital multimeter to measure 6 resistors chosen in the prelab assignments. Record their measured values in **Table 2** below.

**Table 2 – Resistance Values**

	$R_1$	$R_2$	$R_3$	$R_4$	$R_5$	$R_6$	
Nominal Values							k $\Omega$
Measured Values							k $\Omega$

2. Use the MATLAB script to recalculate voltages and currents with measured values of resistors and record them (theoretical values) in **Table 3**.
3. Build the circuit in **Figure 1** with  $v_s = 12V$ . Measure the voltages and currents, record them in **Table 3**, and compare them with the results from the theoretical calculations.

**Table 3 – Voltages and Currents**

	Theoretical (V)	Measured (V)	Percent Error
$v_1$			
$v_2$			
$i_{R4}$			
$i_{R5}$			

4. If there are any discrepancies, explain them.

## V. Laboratory Part 2 – Measuring Unknown Resistance with Wheatstone Bridge

1. Select two new resistors or reuse the two resistors in **Part 1**. Measure  $R_1$  and  $R_2$  with an ohmmeter. Build the Wheatstone bridge in **Figure 3**. Record all values in **Table 4** – Resistance Values.

**Table 4** – Resistance Values

Resistor	Nominal Value (k $\Omega$ )	Measured with Ohmmeter (k $\Omega$ )
$R_1$		
$R_2$		

2. Obtain 5 known resistors from TA. Measure the resistance of each resistor using an ohmmeter and record all values in **Table 5** – Unknown Resistance Values.


**Table 5** – Unknown Resistance Values

Resistor	Measured with Ohmmeter (k $\Omega$ )	Measured with Wheatstone Bridge (k $\Omega$ )	Percent Error
$R_a$			
$R_b$			
$R_c$			
$R_d$			
$R_e$			

3. Measure each unknown resistor using the Wheatstone bridge. Set the ammeter in  $\mu A$  range. Adjust the decade resistor  $R_{adj}$  until the reading on the ammeter is close to zero. Using the measured values of  $R_1$  and  $R_2$ , calculate the value of the unknown resistor using **Eq. 1**
4. Compare the measured values of resistors by the Ohmmeter and the Wheatstone bridge. Explain if they are different.

## VI. Laboratory Part 3 – Wheatstone Bridge Applications


### A. Temperature Measurement with Wheatstone Bridge

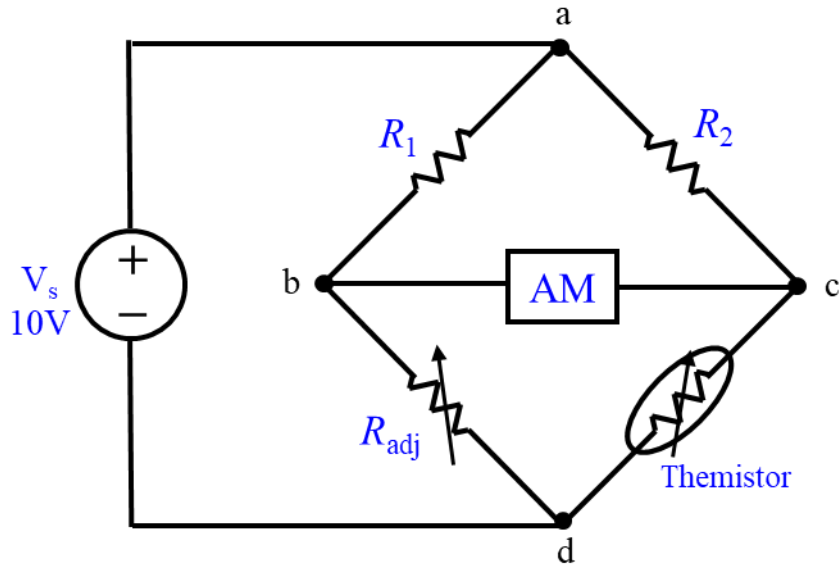

**Figure 4** – Temperature Measurement with Wheatstone Bridge

1. Replace  $R_x$  with a thermistor, as in **Figure 4**. Adjust  $R_{adj}$  until the reading of the ammeter is close to zero. It is the setting at room temperature of the thermistor.
2. Increase or decrease the temperature of the thermistor and see how the reading of the ammeter changes.
3. Make comments or conclusions about your observations.

### B. Measure Light Intensity with Wheatstone Bridge

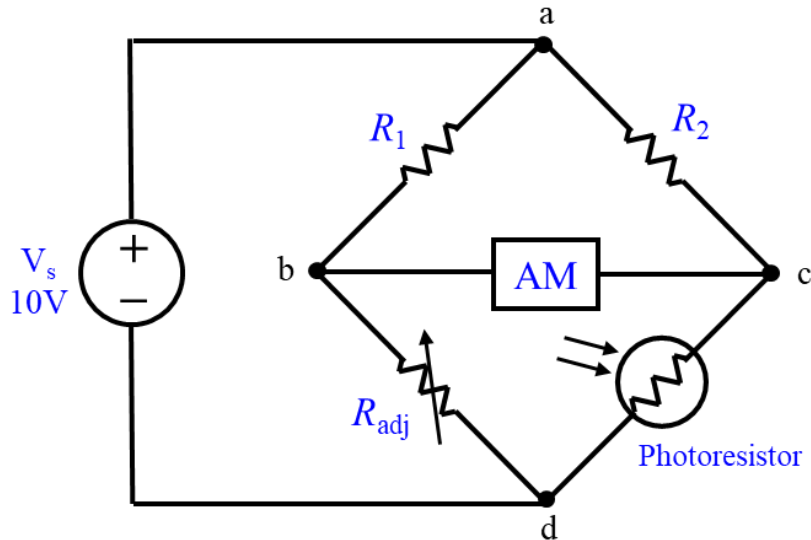

**Figure 5** – Light Measurement with Wheatstone Bridge

1. Replace  $R_x$  with a photoresistor, as in **Figure 5**. Cover the photoresistor and adjust  $R_{adj}$  until the reading of the ammeter is close to zero. It is the setting of low light.
2. Expose the photoresistor to different light settings and see how the reading of the ammeter changes.
3. Make comments or conclusions about your observations.

*Make sure to check off with the TA before leaving the lab section.*

## **VII. Laboratory Report:**

Include the measurements, computations, and answers to questions from the laboratory procedure. Clearly label all steps.