

SANTA CLARA UNIVERSITY	ELEN 115 Spring 2023	Dr. S. Krishnan
Lab 7: Applications of the MOSFET in analog systems		

I. OBJECTIVES



- To study the MOSFET as a switch in sample and hold systems
- To study a MOS inverting amplifier

II. LAB

Part 1: MOSFET as a switch

A. NMOS switch

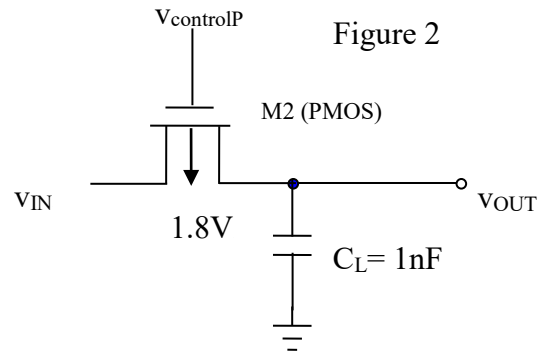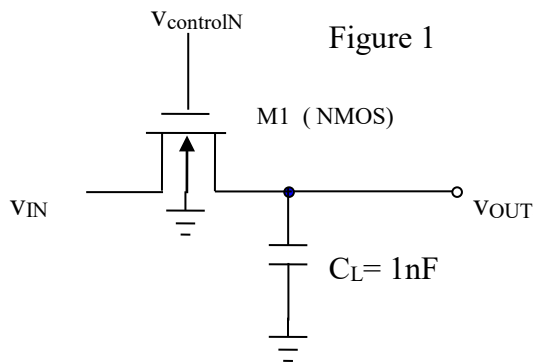- (a) Draw the MOS circuit given in Figure 1 in LTSpice. You will use the NMOS4 component from the library. Connect the bulk terminal to ground.



- (b) Edit the MOSFET model for model parameters $W=100\mu\text{m}$, $L=1\mu\text{m}$.
(c) The sinusoidal input to v_{IN} has a DC Offset of 0.9V and peak voltage 0.9V at a frequency of 100Hz.
(d) Connect a pulse to the gate voltage $v_{controlN}$ which switches from 0V to 1.8V with a time period of 1msec and pulse width of 0.5msec. Keep the rise and fall times at 1ns.
(e) The capacitor is 10nF.
(f) Run a transient simulation and plot input and output on one screen shot.
(g) Observe the voltage on the capacitor and explain the behavior.

B. PMOS switch

- (a) Draw the MOS circuit given in Figure 2 in LTSpice. You will use the PMOS4 component from the library. Connect the bulk terminal to $V_{dd}=1.8\text{V}$.
(b) Edit the MOSFET model for model parameters $W=100\mu\text{m}$, $L=1\mu\text{m}$.
(c) The sinusoidal input to v_{IN} has a DC Offset of 0.9V and peak voltage 0.9V at a frequency of 100Hz.
(d) Connect a pulse to the gate voltage $v_{controlP}$ which switches from 1.8V to 0V with a time period of 1msec and pulse width of 0.5msec. Keep the rise and fall times at 1ns. The signal should be the complement of $v_{controlN}$.
(e) The capacitor is 10nF.
(f) Run a transient simulation and plot input and output on one screen shot.


(g) Observe the voltage on the capacitor and explain the behavior.

C. Transmission gate

- (a) Connect the NMOS and PMOS in parallel for this third circuit.
- (b) Run a transient simulation and plot input and output on one screen shot.
- (c) Observe the voltage on the capacitor and explain the behavior.

Part 2: MOS inverting amplifier

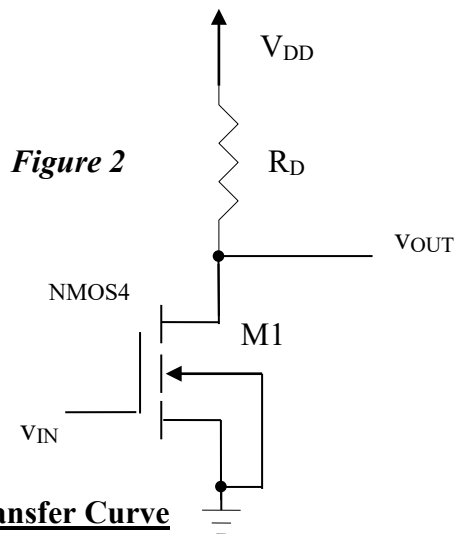- (a) Draw the amplifier circuit in Figure 2.
- (b) For the circuit and MOSFET use the following parameters:
 $V_{DD} = 2.5V$, $V_{to} = 1V$, $k' = 30\mu A/V^2$, $\lambda = 0$, $W/L = 100\mu m/1\mu m$, $R_D = 150K\Omega$
- (c) Edit the MOSFET model to provide the model parameters as used in the prelab.
You can do this by including a command
.MODEL MYNMOS NMOS VTO=?? KP=?? LAMBDA=?? GAMMA=??



(d) Voltage Transfer Curve

Perform a DC sweep at the input v_{IN} from 0 to 5V in steps of 50 mV.

Observe the voltage transfer curve (VTC) by plotting v_{OUT} vs. v_{IN} .

Copy this plot and use this for the following observations.

Clearly indicate on the VTC, the regions of operation of the MOSFET.

(e) MOS as an analog amplifier

- a. On your plot indicate for what portion the MOS transfer curve is linear.
- b. Indicate what would be an optimal BIAS point for use of this circuit as an analog amplifier.
- c. What is the gain at this point? Hint: Find the slope.
- d. What is the input signal that can be given to satisfy the small signal approximation?
- e. Give an input to this amplifier with the DC bias from (b) and signal input from (d).

- f. Run a transient analysis with the input you obtain from ϵ and observe the output signal. Note the DC and signal values.

(f) MOS as a Logic Inverter

- a. Mark the portions of the curve that help you use the device as an inverter.
- b. Find and note the values V_{OH} and V_{OL} from the VTC.
- c. Run a transient analysis giving a pulse signal as logic input to this inverter and see the logic output. What do you observe for the high and low values at the output?
- d. Find the current drawn from V_{dd} . Observe the values during the flat portions of the pulse and during the transitions from low to high and high to low. What do you observe for power consumed?
- e. Increase R_D to $500\text{ K}\Omega$ and rerun part (c). What do you observe? What can you comment on the ideal load value for a perfect inverter.

IV. REPORT

Prepare a detailed report that includes all simulation results. The lab report should contain the following:

Schematic printout of the circuits.

Printout of simulation results.

Answers to questions in the prelab and laboratory procedure.