

Group Number: 9

NAMES (FIRST AND LAST NAME): Harrison Goss  
Mulia Widjaja  
Jonathan Jim

### In-Class Assignment 2

ELEN 21/COEN 21 – Fall 2022

Instructor: Maria Kyrarini

Date: 10/18/2022

Time: 1 hour and 30 minutes

Number of Problems: 4

#### Important Notes:

- Be sure to read all the problems carefully and answer all questions.
- Be sure to answer all parts of each question.
- **Submit only one answer for each question.**
- Multiple solutions for one question will not be graded.
- **Clearly SHOW and EXPLAIN all the steps of your work.**
- **Answers without detailed explanations will NOT be graded (excluding Problem 1).**
- The Engineering School Honor Code applies.

1	20
2	39
3	17
4	12
Total	88

inf. altans

## Boolean Algebra Properties

5a. $x \cdot 0 = 0$	10a. $x \cdot y = y \cdot x$	Commutative
5b. $x + 1 = 1$	10b. $x + y = y + x$	
6a. $x \cdot 1 = x$	11a. $x \cdot (y \cdot z) = (x \cdot y) \cdot z$	Associative
6b. $x + 0 = x$	11b. $x + (y + z) = (x + y) + z$	
7a. $x \cdot x = x$	12a. $x \cdot (y + z) = x \cdot y + x \cdot z$	Distributive
7b. $x + x = x$	12b. $x + y \cdot z = (x + y) \cdot (x + z)$	
8a. $x \cdot \bar{x} = 0$	13a. $x + x \cdot y = x$	Absorption
8b. $x + \bar{x} = 1$	13b. $x \cdot (x + y) = x$	
9. $\bar{\bar{x}} = x$	14a. $x \cdot y + x \cdot \bar{y} = x$	Combining
	14b. $(x + y) \cdot (x + \bar{y}) = x$	
	15a. $\overline{x \cdot y} = \bar{x} + \bar{y}$	DeMorgan's theorem
	15b. $\overline{x + y} = \bar{x} \cdot \bar{y}$	
	16a. $x + \bar{x} \cdot y = x + y$	
	16b. $x \cdot (\bar{x} + y) = x \cdot y$	
	17a. $x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$	Consensus
	17b. $(x + y) \cdot (y + z) \cdot (\bar{x} + z) = (x + y) \cdot (\bar{x} + z)$	

D	$Q(t+1)$
0	0
1	1

T	$Q(t+1)$
0	$Q(t)$
1	$\overline{Q(t)}$

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

$Q_t$	$Q_{t+1}$	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

Handwritten text at the top of the page, possibly a title or header, is mostly illegible due to blurring.

$(1+z)Q$	T
$(+z)Q$	0
$(+z)Q$	1

$(1+z)Q$	D
0	0
1	1

$(1+z)Q$	z	k
$(+z)Q$	0	0
0	0	1
1	1	0
$(+z)Q$	1	1

## Problem 1 (20 points)

True/False questions – Circle the correct answer (no explanation is needed).

- |  |            |
|--|------------|
| i. The decimal value of the following 2's complement number 10010011 is -115.                        | True/False |
| ii. Latch is an edge-sensitive device, while Flip-flop is a level-sensitive device.                  | True/False |
| iii. An arithmetic logic unit (ALU) is a digital circuit used to perform only arithmetic operations. | True/False |
| iv. A D-flip flop and a NOT gate are only needed to implement a T-flip flop.                         | True/False |
| v. We wrote our full names and our group number on page 1.   | True/False |


20

## Problem 2 (40 points)

For the following sequential circuit, do the following:

- Write the truth table. [10 points]
- Redesign this circuit by replacing the  $T_1$  Flip-Flop with negative edge D Flip-Flop, the  $T_0$  Flip-Flop with negative edge JK Flip-Flop and a minimal AND-OR-NOT-XOR gate network. [20 points]
- Draw the circuit you have redesigned. [10 points]


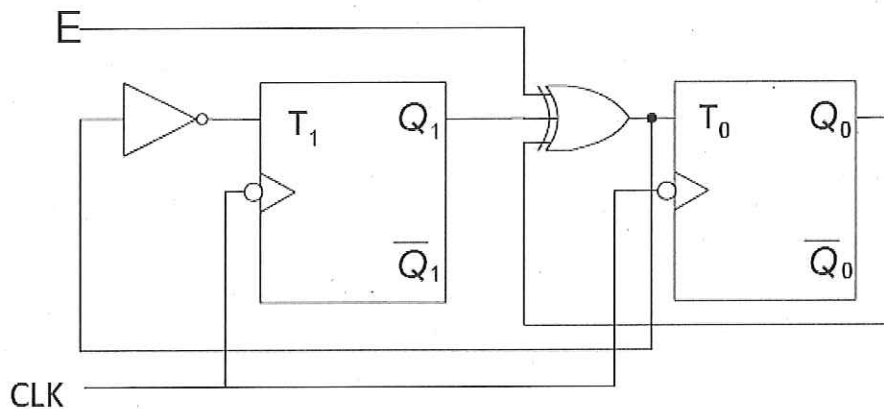
**Reminder:**  $x \oplus y = \bar{x} \cdot \bar{y} + x \cdot y$




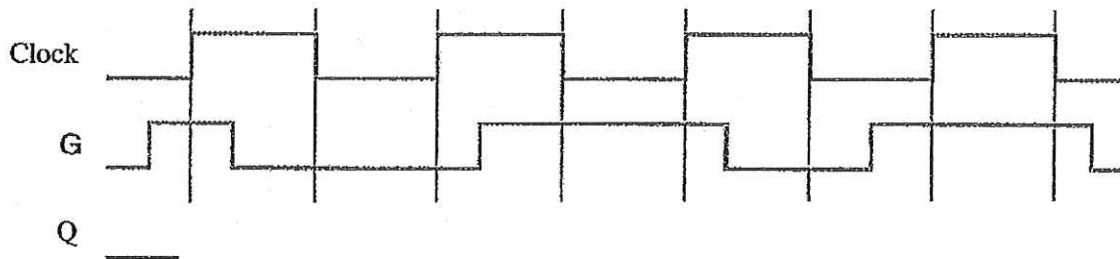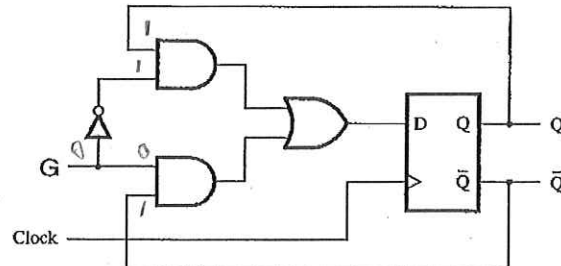
### Problem 3 (20 points)

- Draw the timing diagram of the output Q of the following circuit. Consider that initially  $Q = 0$ . (15 points)
- What circuit is this? (5 points)



### Problem 4 (20 points)

The following two signed 2's complement numbers are given:  $A = 1001\ 0111\ 0101$  and  $B = 1100\ 1001\ 0110$ .

- Subtract number A from number B and show the result. DO NOT use decimal equivalents. [10 points]
- Is the result correct? Explain your answer. [10 points]





②

it would be good to explain\*

a) present states    input    next states

$Q_1(t)$	$Q_0(t)$	$E$	$Q_1(t+1)$	$Q_0(t+1)$	$J_0$	$K_0$	$D_1$	$T_1$	$T_0$
0	0	0	1	0	0	d	1	1	0
0	0	1	0	1	1	d	0	0	1
0	1	0	0	0	d	1	0	0	1
0	1	1	1	1	d	0	1	1	0
1	0	0	1	1	1	d	0	0	1
1	0	1	0	0	0	d	0	1	0
1	1	0	0	1	d	0	0	1	0
1	1	1	0	0	d	1	1	0	1

NXOR

10

b)  $T_1 = E \oplus Q_1(t) \oplus Q_0(t)$      $T_0 = E \oplus Q_1(t) \oplus Q_0(t)$

$Q_1, Q_0$      $J_0$

$E$	00	01	11	10
0	0	d	d	1
1	1	d	d	1

$J_0 = Q_1 + E$

$Q_1, Q_0$

$E$	00	01	11	10
0	0	0	1	1
1	0	0	0	1

$D_1 = Q_1 + \bar{E} \cdot \bar{Q}_0$

$D_1 = Q_1 \cdot \bar{E} + \bar{E} \cdot \bar{Q}_0 + Q_1 \cdot \bar{Q}_0$

$D_1 = Q_1 \bar{Q}_0 + \bar{E} + Q_1$

$D_1 = \bar{Q}_0 \oplus E$  ✓

$Q_1, Q_0$      $K_0$

$E$	00	01	11	10
0	0	1	1	d
1	d	1	0	d

$K_0 = \bar{E} + \bar{Q}_1$

$Q_1, Q_0$      $J_0$

$E$	00	01	11	10
0	0	d	d	1
1	1	d	d	0

$J_0 = Q_1 \bar{E} + \bar{Q}_1 E$

$J_0 = Q_1 \oplus E$  ✓

$Q_1, Q_0$      $K_0$

$E$	00	01	11	10
0	d	1	0	d
1	d	0	1	d

$K_0 = \bar{E} \bar{Q}_1 + E Q_1$

$K_0 = \bar{E} \oplus Q_1$  ✓

①  $10010011$


$$-128 + \overset{0}{16} + 0 + 16 + 2 \times 1$$

$$\begin{array}{cc} 0 & 0 \\ 1 & 1 \end{array}$$

$$-128 + 19 = -109$$

2

C

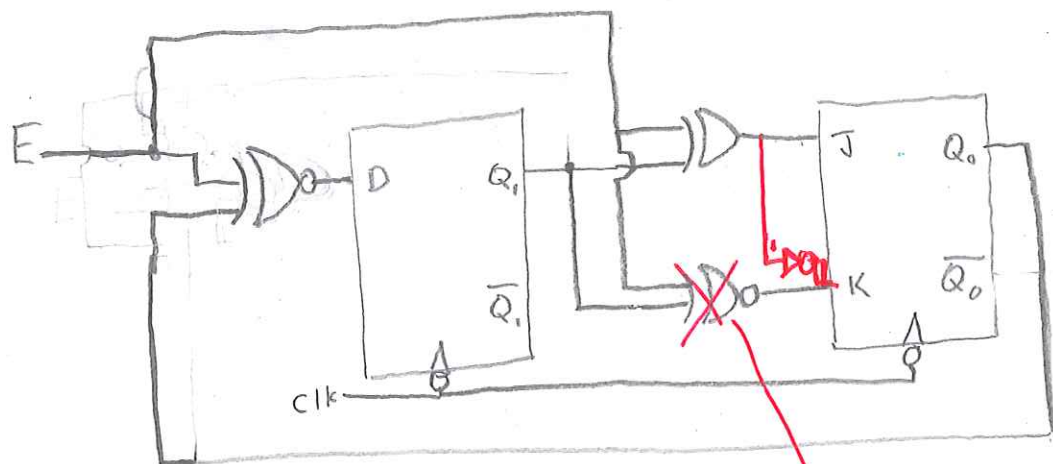

9


\* XOR explanation

$Q_1$	$Q_0$	$E$	$Q_1 \oplus Q_0$	$Q_1 \oplus Q_0 \oplus E = T_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1

you can reuse the XOR



③ a)

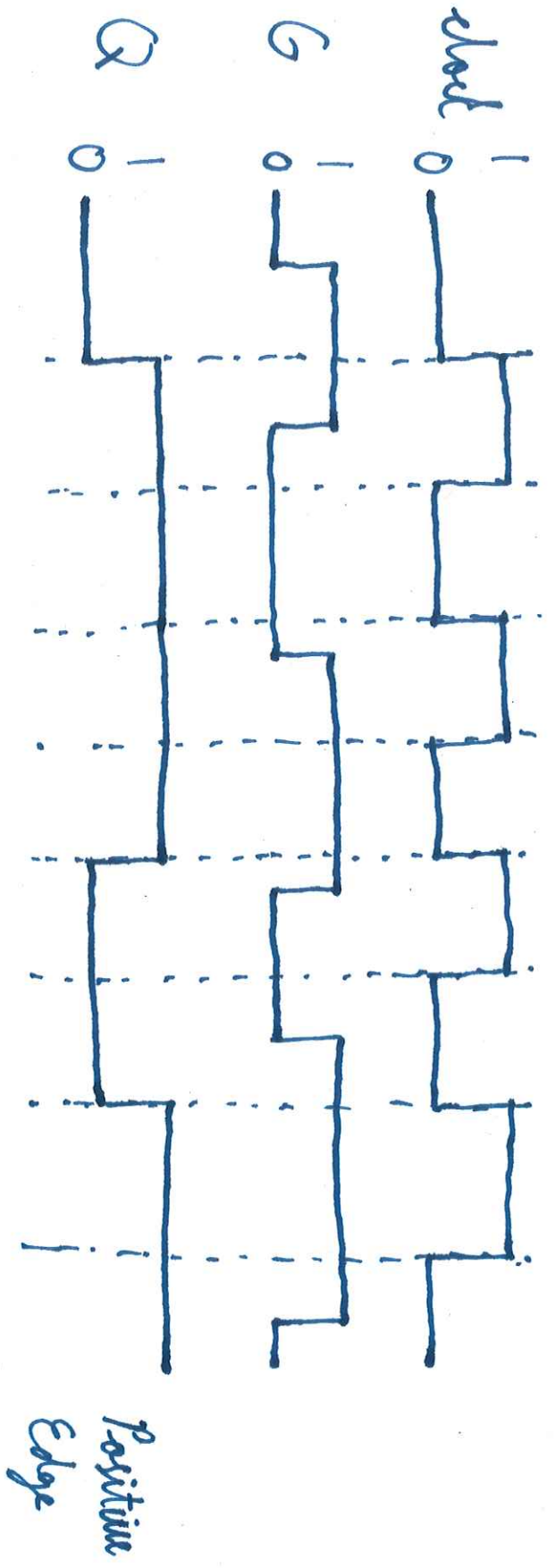


Q changes when  $G=1$  and  $check=0 \rightarrow 1$

$$D = Q(t) + \bar{G} + G(Q(t))$$

where is  $Q(t+1)$ ?


①

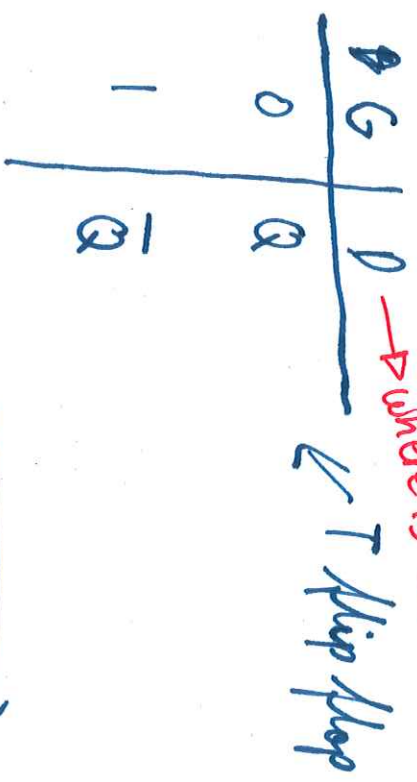

②

b) This is a T flip flop why?

3) a)  $Q$

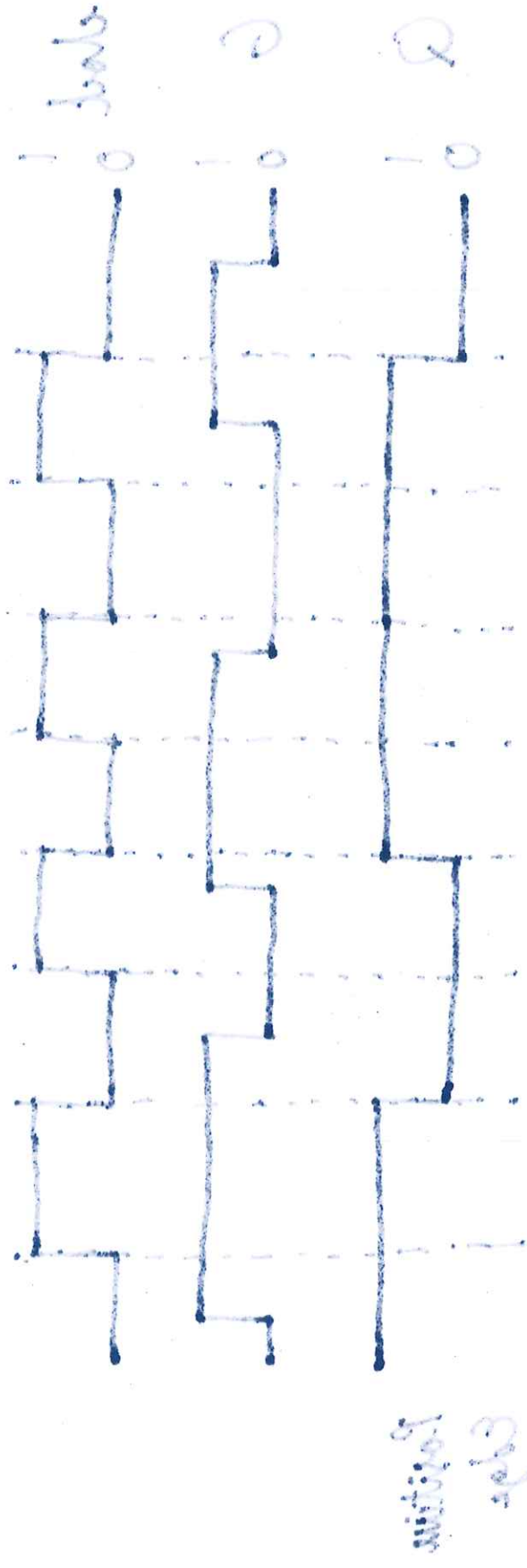

$Q$  starts at 0,  $C$  starts at 1,  $D$  starts at 0

$$D = Q(t) + \overline{C(t)} + C(\overline{Q(t)})$$

$$\begin{array}{c|c} Q & C \\ \hline 0 & 0 \\ 0 & 1 \\ 1 & 0 \\ 1 & 1 \end{array}$$

Truth table for  $D = Q(t) + \overline{C(t)} + C(\overline{Q(t)})$

d) This is a 1-bit full adder

# In-Class Assignment #2

Group 9  
(10/18/2022)

4. a. Flip A: from:  $A = 1001 \ 011 \ 0101$   
to:  $-A = 0110 \ 1000 \ 1010$

$$B - A = B + (-A)$$

$  \begin{array}{r}  \textcircled{12} \leftarrow C_{11} \\  \begin{array}{r}  11 \\  1100 \\  + 0110 \\  \hline  0011  \end{array}  \end{array}  $	$\rightarrow$	$  \begin{array}{r}  \textcircled{10} \\  B \\  + (-A) \\  \hline  B - A  \end{array}  $
--	---------------	--

b. Two leftmost carries are equal  
Meaning: They are accurate.

↓  
The carries??

②

$C_{11} \oplus C_{12} = 1 \oplus 1 = 0 \rightarrow$  no overflow  $\rightarrow$  the result is correct.

