

NAMES:

Group Number:

In-Class Assignment 4

ELEN 21/COEN 21 – Fall 2022

Instructor: Maria Kyrarini

Date: 11/29/2022

Time: 1 hour and 20 minutes

Number of pages: 3

Important Notes:

- Be sure to read all the problems carefully and answer all questions.
- Be sure to answer all parts of each question.
- **Submit only one answer for each question.**
- Multiple solutions for one question will not be graded.
- **Clearly show all the steps of your work.**
- **Answers without explanation will not be graded.**
- The Engineering School Honor Code applies.

Problem 1 (35 points)


Implement the circuit that accepts two binary numbers A and B and performs the operation A^B using two 2-to-4 decoders with enable and a minimum network of OR, NOT, AND gates. The number A consists of 2 bits ($A = a_1a_0$) and B consists of 1 bit ($B = b_0$)

Reminder 1: $0^0 = 1$.

Reminder 2: Truth table and graphic symbol for 2-to-4 decoder with enable:

En	w ₁	w ₀	y ₀	y ₁	y ₂	y ₃
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

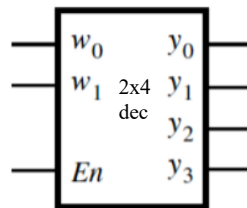


(b) Graphical symbol

Problem 2 (30 points)

A Mealy-style state machine has an input w and an output z. The machine is a sequence detector that produces $z = 1$ when it detects 1101; otherwise $z = 0$. Derive a circuit that realizes this state machine using one-hot encoding approach, T flip-flops and a network of AND-OR-NOT gates. **Note:** You do not need to draw the circuit – Show the Boolean expressions for the simplified circuit.

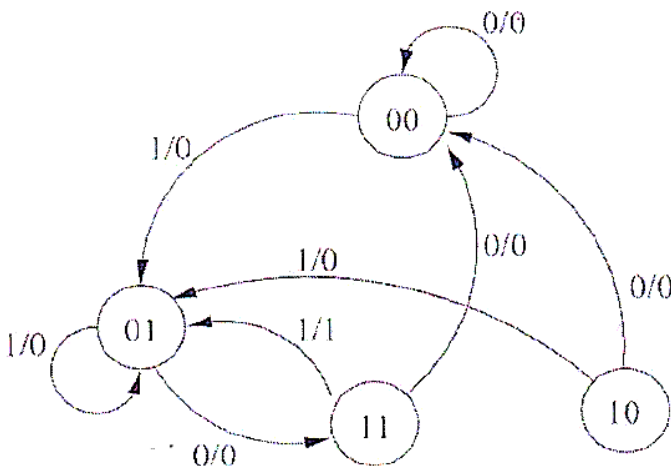Problem 3 (35 points)

Consider the following state diagram for a circuit with one input X and one output Z. Draw the circuit implementation of this state diagram using JK positive-edge flip-flop (state Q_0), T positive-edge flip-flop (state Q_1), and a minimal AND-OR-NOT-XOR network. The states are in the form Q_1Q_0 .



Boolean Algebra Properties

5a.	$x \cdot 0 = 0$	10a.	$x \cdot y = y \cdot x$	<i>Commutative</i>
5b.	$x + 1 = 1$	10b.	$x + y = y + x$	
6a.	$x \cdot 1 = x$	11a.	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	<i>Associative</i>
6b.	$x + 0 = x$	11b.	$x + (y + z) = (x + y) + z$	
7a.	$x \cdot x = x$	12a.	$x \cdot (y + z) = x \cdot y + x \cdot z$	<i>Distributive</i>
7b.	$x + x = x$	12b.	$x + y \cdot z = (x + y) \cdot (x + z)$	
8a.	$x \cdot \bar{x} = 0$	13a.	$x + x \cdot y = x$	<i>Absorption</i>
8b.	$x + \bar{x} = 1$	13b.	$x \cdot (x + y) = x$	
9.	$\bar{\bar{x}} = x$	14a.	$x \cdot y + x \cdot \bar{y} = x$	<i>Combining</i>
		14b.	$(x + y) \cdot (x + \bar{y}) = x$	
		15a.	$\overline{x \cdot y} = \bar{x} + \bar{y}$	<i>DeMorgan's theorem</i>
		15b.	$\overline{x + y} = \bar{x} \cdot \bar{y}$	
		16a.	$x + \bar{x} \cdot y = x + y$	
		16b.	$x \cdot (\bar{x} + y) = x \cdot y$	
		17a.	$x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$	<i>Consensus</i>
		17b.	$(x + y) \cdot (y + z) \cdot (\bar{x} + z) = (x + y) \cdot (\bar{x} + z)$	