

# Electric Circuits I


## Laboratory 8 – Operational Amplifier Circuits

### Objective:

- Design and implement standard OpAmp circuits.
- Design and implement cascaded OpAmp circuits.

### I. Equipment:

- DC Power Supply (Keysight EDU36311A)
- Digital Multimeter (Keysight EDU34450A)
- Waveform Generator (Keysight EDU33221A)
- Digital Oscilloscope (Keysight EDUX1052G)
- Breadboard for connecting resistors
- 5 resistors between  $1\text{k}\Omega$  to  $30\text{k}\Omega$ .
- Resistance Decade  $R_{\text{dec}}$ .
- 1 Operational Amplifier ( $\mu 741$ ).

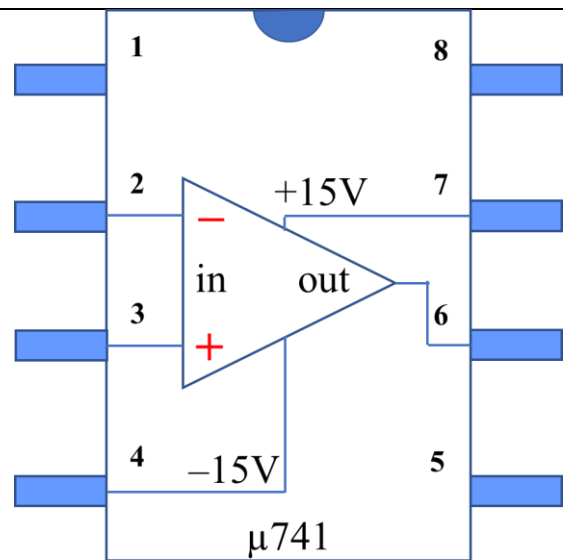


**Figure 1** – Operational Amplifier Diagram

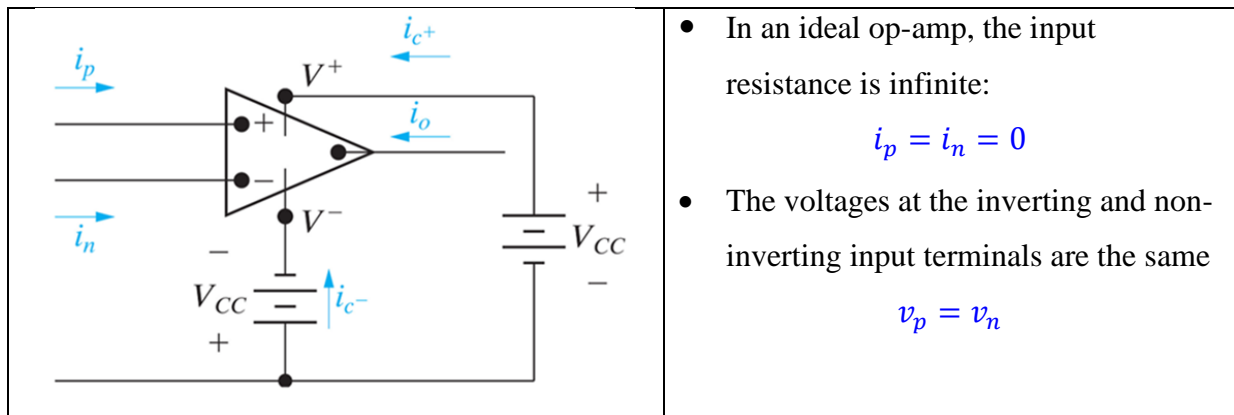
### II. Background & Theory

An *operational amplifier* (OpAmp) is an integrated circuit that can amplify weak electric

signals. Each OpAmp has two inputs and one output. It also has two input pins for the DC power supply. The primary role of OpAmp is to amplify the voltage difference between the two inputs and produce a result at the output pin. Three of the most common applications of OpAmp are inverting amplifiers, non-inverting amplifiers, and voltage followers. Ideally, the input impedance for plus and minus terminals is infinite, and the output impedance is 0. However, for a practical  $\mu 741$  OpAmp, the input impedance is large ( $\sim 2\text{M}\Omega$ ), and the output impedance is about  $75\Omega$ . The function of the voltage follower is to overcome the loading effect. In simplifying the analysis process, we assume that OpAmps are ideal, as shown below:




From the ideal condition of OpAmps, we can apply KCL at the  $V^+$  or  $V^-$  terminal of an OpAmp to derive the expressions of the output voltages for inverting and non-inverting amplifiers.

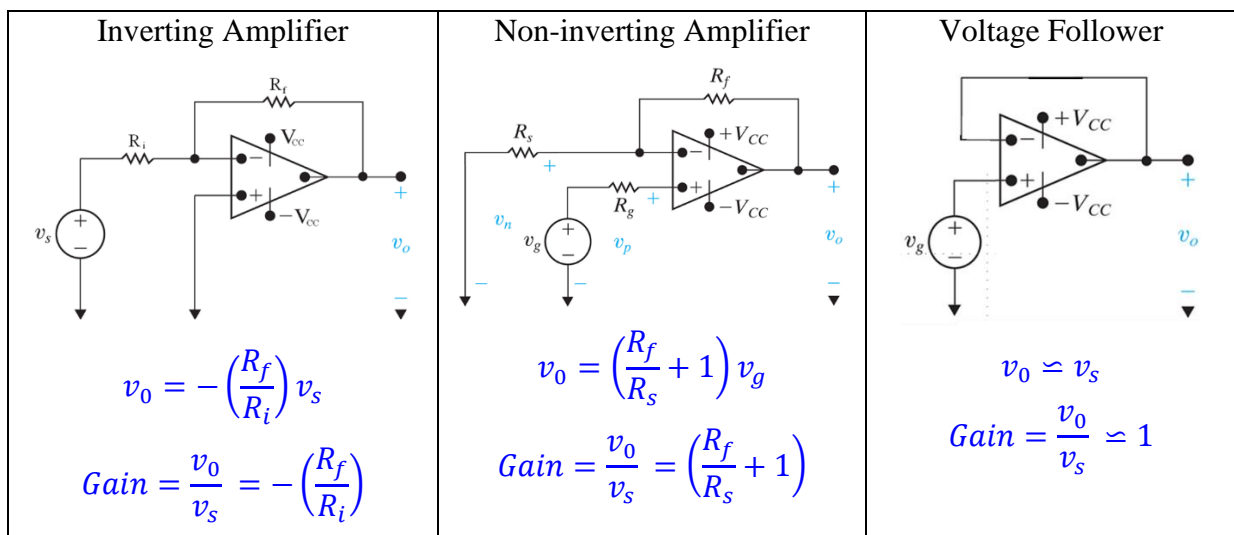

**Figure 2** – Operation Amplifier Applications

In many OpAmp circuits, OpAmps are often connected in stages where the output of an

OpAmp in stage 1 becomes the input for OpAmp 2 in stage 2, shown in **Figure 3**.

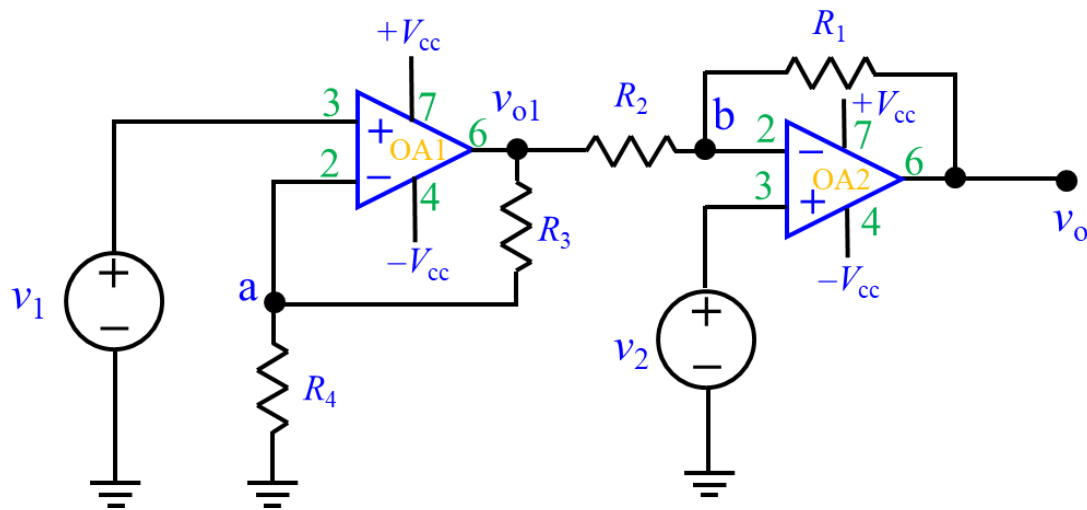

**Figure 3** – Operation Amplifier Circuit

Note that the *green numbers* are the *pin numbers* of OpAmps.

**Table 1** – Standard Resistor Values

(K = x 1,000, M = x 1,000,000)

1.0	5.6	33	160	820	3.9K	20K	100K	510K	2.7M
1.1	6.2	36	180	910	4.3K	22K	110K	560K	3M
1.2	6.8	39	200	1K	4.7K	24K	120K	620K	3.3M
1.3	7.5	43	220	1.1K	5.1K	27K	130K	680K	3.6M
1.5	8.2	47	240	1.2K	5.6K	30K	150K	750K	3.9M
1.6	9.1	51	270	1.3K	6.2K	33K	160K	820K	4.3M
1.8	10	56	300	1.5K	6.6K	36K	180K	910K	4.7M
2.0	11	62	330	1.6K	7.5K	39K	200K	1M	5.1M
2.2	12	68	360	1.8K	8.2K	43K	220K	1.1M	5.6M
2.4	13	75	390	2K	9.1K	47K	240K	1.2M	6.2M
2.7	15	82	430	2.2K	10K	51K	270K	1.3M	6.8M
3.0	16	91	470	2.4K	11K	56K	300K	1.5M	7.5M
3.3	18	100	510	2.7K	12K	62K	330K	1.6M	8.2M
3.6	20	110	560	3K	13K	68K	360K	1.8M	9.1M
3.9	22	120	620	3.2K	15K	75K	390K	2M	10M
4.3	24	130	680	3.3K	16K	82K	430K	2.2M	15M
4.7	27	150	750	3.6K	18K	91K	470K	2.4M	22M
5.1	30								

### III. Prelab Assignment:

*The prelab assignments should be completed and submitted to Camino before the lab.*

Create a MATLAB script, assuming that all OpAmps are ideal,

- Design an inverting amplifier in **Figure 2** for a gain of 2.0 with 2 resistors ( $R_i$  and  $R_{f1}$ ) from the standard resistor values in **Table 1** between  $1\text{k}\Omega$  to  $30\text{k}\Omega$ .
- Design a non-inverting amplifier in **Figure 2** for a gain of 2.5 with 2 resistors ( $R_s$  and  $R_{f2}$ ) from the standard resistor values in **Table 1** between  $1\text{k}\Omega$  to  $30\text{k}\Omega$ .
- Calculate the output voltage  $v_o$  of the OpAmp circuit in **Figure 3** with 4 resistors ( $R_1$  to  $R_4$ ) from the standard resistor values in **Table 1** between  $1\text{k}\Omega$  to  $30\text{k}\Omega$  and  $v_1 = v_2 = 1\text{V}$ .

#### IV. Laboratory

*Verify the results of MATLAB scripts of your prelab assignment with the TA before working on the lab procedures.*

- Use the digital multimeter to measure resistors chosen in the prelab assignments. Record their measured values in **Table 2** below.

**Table 2** – Resistance Values


	$R_i$	$R_{f1}$	$R_s$	$R_{f2}$	
Nominal Values					$\text{k}\Omega$
Measured Values					$\text{k}\Omega$

- With the measured values of  $R_i$ ,  $R_{f1}$ ,  $R_s$ , and  $R_{f2}$  calculate the gains of OpAmp circuits again and record the calculations in **Table 3**.
- Build the inverting circuit in **Figure 2** with  $\pm 15\text{V}$  for  $+V_{cc}$  and  $-V_{cc}$ . The pin numbers are in **Figure 1**. Connect the third power supply output ( $v_s$ ) to the input of the amplifier and set it to  $+1\text{V}$ . Measure  $v_o$ , calculate the gain ( $v_o/v_s$ ), and record the result in **Table 3**.
- Build the non-inverting circuit in **Figure 2** with  $\pm 15\text{V}$  for  $+V_{cc}$  and  $-V_{cc}$ . Connect the third power supply output ( $v_s$ ) to the input of the amplifier and set it to  $+1\text{V}$ . Measure  $v_o$ , calculate the gain ( $v_o/v_s$ ), and record the result in **Table 3**.

**Table 3** – Gain of Operational Amplifier Circuits

	Expected Gain	Measured Gain	% Error
Inverting OpAmp			
Non-inverting OpAmp			

5. Build the voltage follower in **Figure 2** with  $\pm 15\text{V}$  for  $+V_{cc}$  and  $-V_{cc}$ .
6. Set the function generator to produce a sine wave ( $v_g$ ) of 500Hz and 1V amplitude and connect to the input of the voltage follower.
7. Connect CH1 and CH2 of the oscilloscope to the voltage follower's input and output.  
Observe the results.
8. Build a circuit in **Figure 4a** with  $R_s = 1\text{k}\Omega$ . Use CH1 and CH2 of the oscilloscope to measure the amplitudes of  $v_g$  and  $v_{out}$  with different values of  $R_{dec}$ . Record the measurements in **Table 4**. Add a voltage follower as shown in **Figure 4b** and repeat the same process.

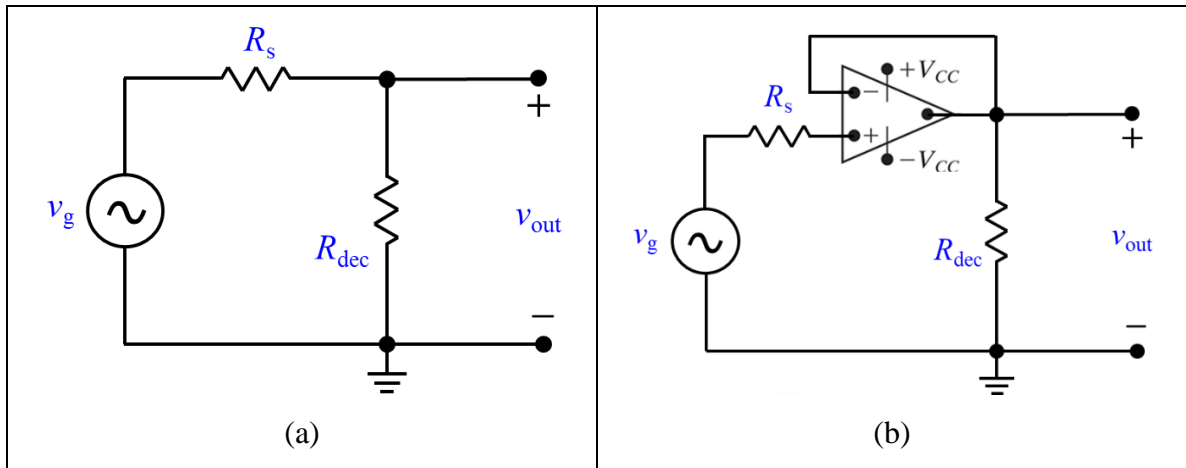

**Figure 4** – Overcoming Loading Effect with Voltage Follower

**Table 4** – Voltage Amplitude

$R_{dec}$ ( $\Omega$ )	$v_g$ (V)	$v_{out}$ (V)	$v_{out}$ with voltage follower (V)
5,000			
3,000			
1,000			
800			
400			
200			
100			
50			

9. Explain the results.
10. Use the digital multimeter to measure resistors chosen in the prelab assignments. Record their measured values in **Table 5** below.

**Table 5** – Resistance Values

	$R_1$	$R_2$	$R_3$	$R_4$	
Nominal Values					k $\Omega$
Measured Values					k $\Omega$

11. Build the OpAmp circuit in **Figure 3** with  $\pm 15\text{V}$  for  $+V_{cc}$  and  $-V_{cc}$ . Notice the plus and minus inputs of the two OpAmps. The **pin numbers** are in **Figure 3**. Set  $v_1 = v_2 = 1\text{V}$ . Use MATLAB to recalculate the theoretical voltages with measured values of resistors. Measure the voltages and record them in **Table 6**.

**Table 6** – Voltages of Operational Amplifier Circuit

	Theoretical (V)	Measured (V)	% Error
$v_a$			
$v_{o1}$			
$v_b$			
$v_o$			

12. If there are any discrepancies, explain them.
13. Derive comments or conclusions from the results.

*Make sure to check off with the TA before leaving the lab section.*

## V. Laboratory Report:

Include the measurements, computations, and answers to questions from the laboratory procedure. Clearly label all steps.