



Noble Huang (Mulia Widjaja)

HW #4: Amplifiers



1. a. $\text{Gain} = \frac{V_o}{i_{in}} = \frac{50 \text{ mV}}{1 \text{ nA}} = \frac{50 \cdot 10^{-3}}{10^{-9}} = 50000 \text{ V/A}$

Input current (i_{in})



Output Voltage (V_o)

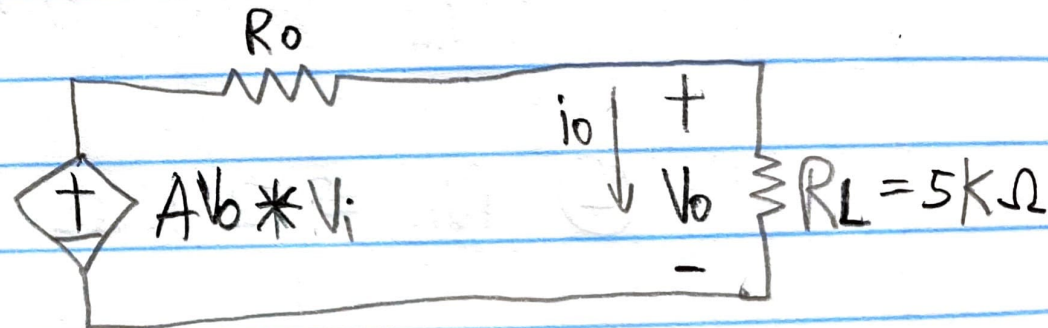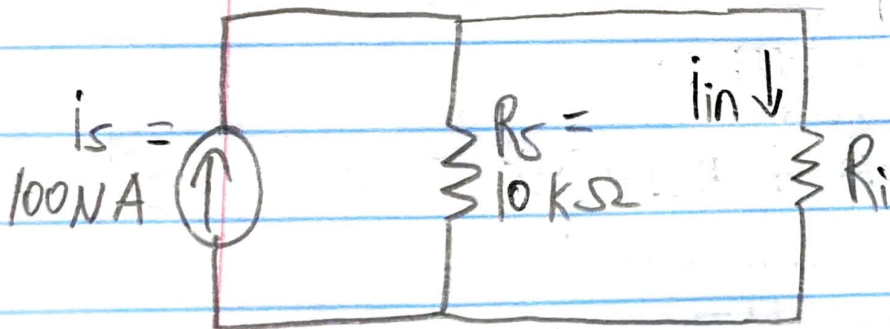

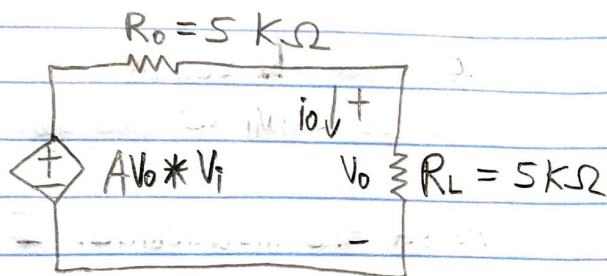
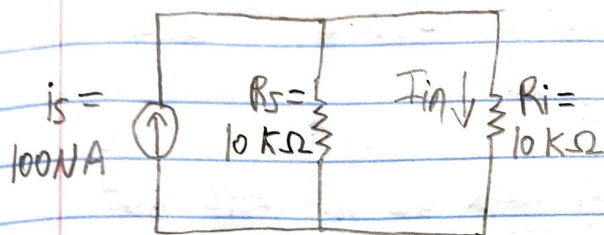
① $R_i = 10\text{ k}\Omega$; $R_o = 5\text{ k}\Omega$



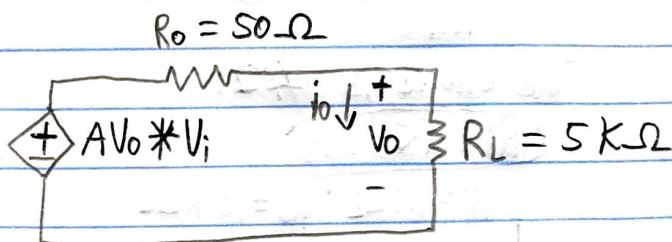
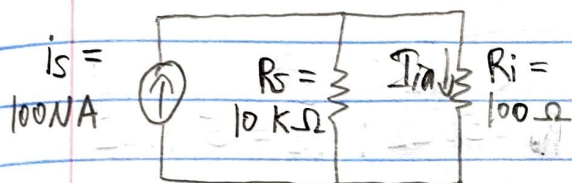
② $R_i = 100\text{ }\Omega$; $R_o = 50\text{ }\Omega$



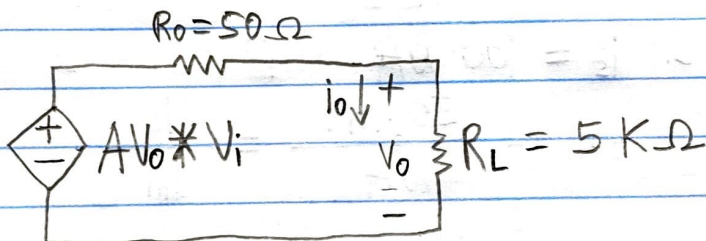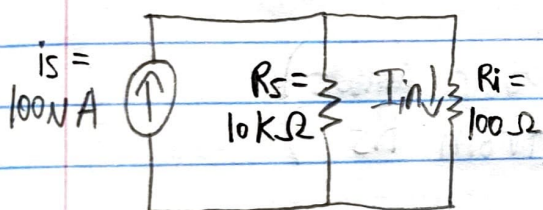③ $R_i = 10\text{ k}\Omega$; $R_o = 50\text{ }\Omega$



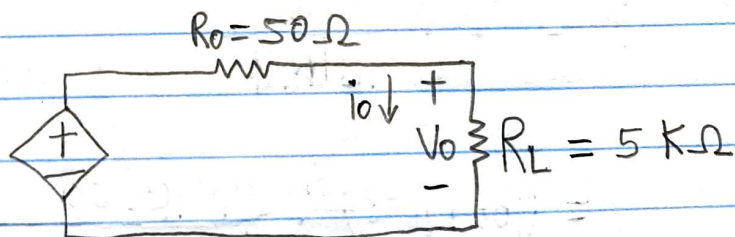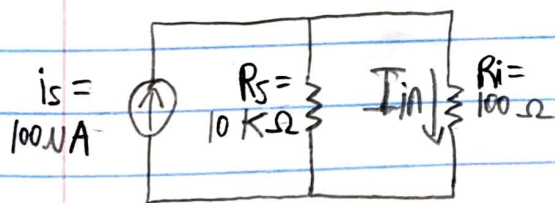④ $R_i = 100\text{ }\Omega$; $R_o = 5\text{ k}\Omega$



b.

$R_i \ll R_S$

$\downarrow R_S = 10\text{ k}\Omega$

$R_i \ll 10\text{ k}\Omega$

$R_o \ll R_L$

$\downarrow R_L = 5\text{ k}\Omega$

$R_o \ll 5\text{ k}\Omega$

We need R_i and R_o below $10\text{ k}\Omega$ and $5\text{ k}\Omega$, respectively, and as small as possible.

As per the instructions, I do NOT work the numbers out for each choice, as it is already apparent what option the designer should choose.

The choice is #2:

$$R_i \ll R_s$$

$$R_i = 100\ \Omega; R_s = 10\text{ k}\Omega$$

$$100 \ll 10\text{ k}$$

$$R_o \ll R_L$$

$$R_o = 50\ \Omega; R_L = 5\text{ k}\Omega$$

$$50 \ll 5\text{ k}$$

C. $i_s = 100\text{ nA}$

$$\text{Gain} = \frac{50\text{ mV}}{1\text{ nA}} = \frac{V_o}{i_{in}} \quad \text{(other values from } R_s \text{)}$$

Current divider:

$$i_{in} = i_s \cdot \frac{R_s}{R_s + R_i}$$

$$= (100 \cdot 10^{-6}) \cdot \frac{10000}{10000 + 100}$$

$$= (100 \cdot 10^{-6}) \cdot \frac{10000}{10100}$$

$$= 9.901 \cdot 10^{-5}\text{ A}$$

$$V_o = \text{Gain} \cdot I_{in}$$

$$= \frac{50 \cdot 10^{-3}}{10^{-6}} \cdot (9.901 \cdot 10^{-8})$$

$$= 4.9505 \text{ V}$$

$$P = \frac{V_o^2}{R_L} = \frac{(4.9505)^2}{5000} = 4.901 \cdot 10^{-3} \text{ W}$$


2. Clipped peaks: $V_o > 8 \text{ V}$

$$V_o < -9 \text{ V}$$

Dual supply: $\pm 10 \text{ V} \rightarrow V_{in}$

$$\text{Gain} = \frac{V_o}{V_{in}} = 2 \text{ V/V}$$


2.

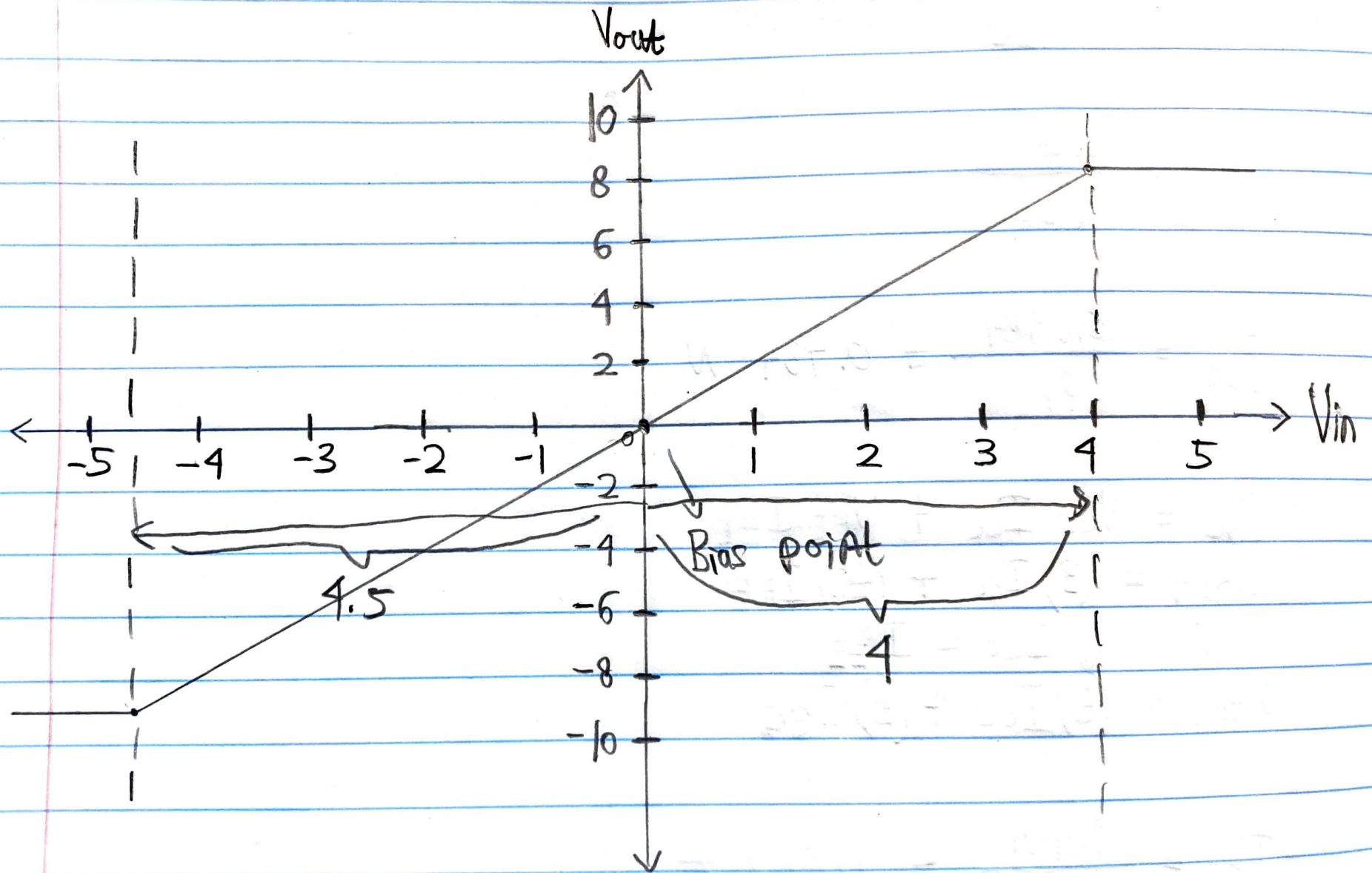

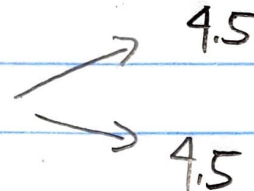i. Highest $\longrightarrow V_{in} = 4$

Lowest $\longrightarrow V_{in} = 1.5$

Expression: $0\text{ V} + 4.5 \sin \omega t$



a. 4.5 V

b. 4 V

ii. $\frac{4 - (-4.5)}{2} = 4.25$

$$4.25 + (-4.5) = -0.5$$

$$V_{in} = 4.25 - 0.5 \sin \omega t$$

Bias point (Max possible undistorted sine wave output):
 4.25 V

3. $V_s = \pm 3 \text{ V} \longrightarrow V_{CC} = 3 \text{ V} ; V_{EE} = -3 \text{ V}$
 $V_o = 2.2 \text{ V}$ (Peak Sine Wave)
 $R_L = 100 \Omega$ (100- Ω load)
 $V_i = 0.2 \text{ V}$ (0.2-V Peak input)
 $i_I = 1 \text{ mA} \longrightarrow$

a. Unknown:

1. Voltage gain
2. Current gain
3. Power gain

1. Voltage gain = A_V

$$= \frac{V_o}{V_i} = \frac{2.2}{0.2} = 11$$

$$\begin{aligned} A_V(\text{dB}) &= 20 \log |A_V| \\ &= 20 \log |11| \\ &= 20.83 \text{ dB} \end{aligned}$$

2. Current gain = A_i

$$i_o = \frac{V_o}{R_L} = \frac{2.2}{100} = 0.022$$

$$A_i = \frac{i_o}{i_I} = \frac{0.022}{10^{-3}} = 22$$

$$\begin{aligned} A_i(\text{dB}) &= 20 \log |A_i| \\ &= 20 \log |22| \\ &= 26.85 \text{ dB} \end{aligned}$$

$$\begin{aligned}
 3. \text{ Power gain} &= A_p \\
 &= A_v \cdot A_i \\
 &= (11)(22) \\
 &= 242
 \end{aligned}$$

$$A_p(\text{dB}) = 23.84 \text{ dB}$$

$$b. P_L = \frac{V_o^2}{R_L} = \frac{(2.2)^2}{100} = 0.0484 \text{ W}$$

$$\eta = \frac{P_L}{P_{dc}} \cdot 100\%$$

$$10\% = \frac{0.0484}{P_{dc}} \cdot 100\%$$

$$0.1 = \frac{0.0484}{P_{dc}}$$

$$P_{dc} = \frac{0.0484}{0.1} = 0.484 \text{ W}$$

$$P_{dc} = V_{cc} I_{cc} + V_{EE} I_{EE}$$

$$0.484 = (3) I_{cc} + (3) I_{EE}$$

$$\downarrow I_{cc} = I_{EE}$$

$$0.484 = (3) I_{cc} + (3) I_{cc}$$

$$I_{cc} = \frac{0.484}{6} = 0.0807 \text{ A}$$

P_I : very small \rightarrow can be ignored $\rightarrow P_I = 0$

$$P_{dc} + P_I = P_L + P_{\text{dissipated}}$$

$\downarrow P_I = 0$

$$P_{dc} = P_L + P_{\text{dissipated}}$$

$$0.484 = 0.0484 + P_{\text{dissipated}}$$

$$P_{\text{dissipated}} = 0.4356 \text{ W}$$

Answers: ① $P_L = 0.0484 \text{ W}$

② $P_{dc} = 0.484 \text{ W}$

③ $P_{\text{dissipated}} = 0.4356 \text{ W}$