

90

Group Number: 5

NAMES (FIRST AND LAST NAME):

Bryce Kelly  
Mulia Widjaja  
Venus Li

### In-Class Assignment 1

ELEN 21/COEN 21 – Fall 2022

Instructor: Maria Kyrarini

Date: 10/4/2022

Time: 1 hour and 20 minutes

Number of Problems: 3

#### Important Notes:

- Be sure to read all the problems carefully and answer all questions.
- Be sure to answer all parts of each question.
- **Submit only one answer for each question.** Multiple solutions for one question will NOT be graded.
- **Clearly show all the steps of your work.**
- **Answers without detailed explanations will NOT be graded.**
- The Engineering School Honor Code applies.

### Problem 1 (30 points)

Implement the following function using only 2-to-1 multiplexers and NOT gates:

$$f = \bar{w}_2 w_3 + \bar{w}_1 w_2 \bar{w}_3 + w_2 \bar{w}_3 w_4 + w_1 \bar{w}_2 \bar{w}_4$$

**Note:** AND, NAND, OR, NOR, XOR gates are not available.

### Problem 2 (35 points)

For the logic function  $f(w,x,y,z) = \prod M(1,7,12,13,14,15) \cdot d(0,2,8,10)$  (**Note:** the  $d$  represents the don't cares):


- Show the truth table. [5 points]
- Draw a completely labeled K-map. [5 points]
- Write the algebraic expression for the minimized Sum of Products (SoP) and minimized Product of Sum (PoS) implementation of this function using the K-map. **Note:** Show the circles on the K-map. [10 points]
- Write a Verilog program using structural code that implements the SoP. [5 points]

### Problem 3 (35 points)

Simplify the following circuit by using Boolean Algebra properties. Assume that you have **only** 2-input and 3-input NAND gates. It is known that  $\bar{x} + \bar{y} + \bar{z} = \bar{x} \cdot \bar{y} \cdot \bar{z}$ . Draw the simplified circuit.

**Note:** NOT, AND, OR, NOR, XOR gates are not available.

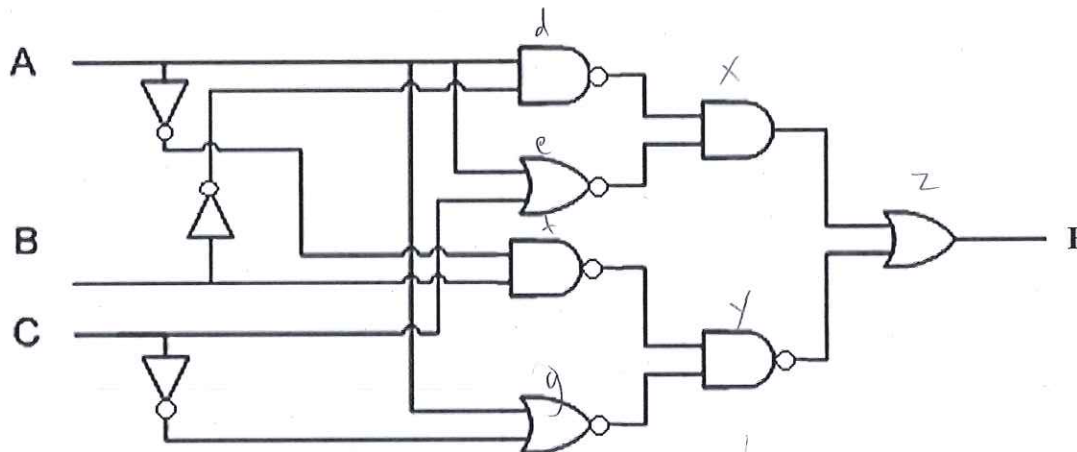**Note:** Simplification by K-maps will NOT be graded.



## Boolean Algebra Properties

5a.	$x \cdot 0 = 0$	10a.	$x \cdot y = y \cdot x$	<i>Commutative</i>
5b.	$x + 1 = 1$	10b.	$x + y = y + x$	
6a.	$x \cdot 1 = x$	11a.	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	<i>Associative</i>
6b.	$x + 0 = x$	11b.	$x + (y + z) = (x + y) + z$	
7a.	$x \cdot x = x$	12a.	$x \cdot (y + z) = x \cdot y + x \cdot z$	<i>Distributive</i>
7b.	$x + x = x$	12b.	$x + y \cdot z = (x + y) \cdot (x + z)$	
8a.	$x \cdot \bar{x} = 0$	13a.	$x + x \cdot y = x$	<i>Absorption</i>
8b.	$x + \bar{x} = 1$	13b.	$x \cdot (x + y) = x$	
9.	$\bar{\bar{x}} = x$	14a.	$x \cdot y + x \cdot \bar{y} = x$	<i>Combining</i>
		14b.	$(x + y) \cdot (x + \bar{y}) = x$	
		15a.	$\overline{x \cdot y} = \bar{x} + \bar{y}$	<i>DeMorgan's theorem</i>
		15b.	$\overline{x + y} = \bar{x} \cdot \bar{y}$	
		16a.	$x + \bar{x} \cdot y = x + y$	
		16b.	$x \cdot (\bar{x} + y) = x \cdot y$	
		17a.	$x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$	<i>Consensus</i>
		17b.	$(x + y) \cdot (y + z) \cdot (\bar{x} + z) = (x + y) \cdot (\bar{x} + z)$	



Problem 1

$$f = \bar{w}_2 w_3 + \bar{w}_1 w_2 \bar{w}_3 + w_2 \bar{w}_3 w_4 + w_1 \bar{w}_2 w_4$$

$$\bar{w}_2 (w_3 + w_1 \bar{w}_4) + w_2 (\bar{w}_1 \bar{w}_3 + \bar{w}_3 w_4)$$

$$\bar{w}_2 (w_3 + w_1 \bar{w}_4) + w_2 (\bar{w}_3 (\bar{w}_1 + w_4))$$

$$d = \bar{w}_3 (\bar{w}_1 + w_4)$$

$$\text{if } \bar{w}_3 = 0; d = \bar{w}_1 + w_4$$

$$\text{if } w_3 = 1; d = 0$$

$$b = \bar{w}_1 + w_4$$

$$\text{if } \bar{w}_1 = 0; b = w_4$$

$$\text{if } w_1 = 1; b = w_4$$

~~Handwritten scribble~~

$$\bar{w}_2 (w_3 + w_1 \bar{w}_4) + w_2 (\bar{w}_3 (\bar{w}_1 + w_4) + w_3(0))$$

$$\bar{w}_2 (w_3 + w_1 \bar{w}_4) + w_2 (\bar{w}_3 (\bar{w}_1(1) + w_1(w_4)) + w_3(0))$$

$$c = w_3 + w_1 \bar{w}_4$$

$$\text{if } \bar{w}_3 = 0; c = w_1 \bar{w}_4$$


$$\text{if } w_3 = 1; c = 1$$

$$d = w_1 \bar{w}_4$$

$$\text{if } \bar{w}_1 = 0; d = 0$$

$$\text{if } w_1 = 1; d = \bar{w}_4$$
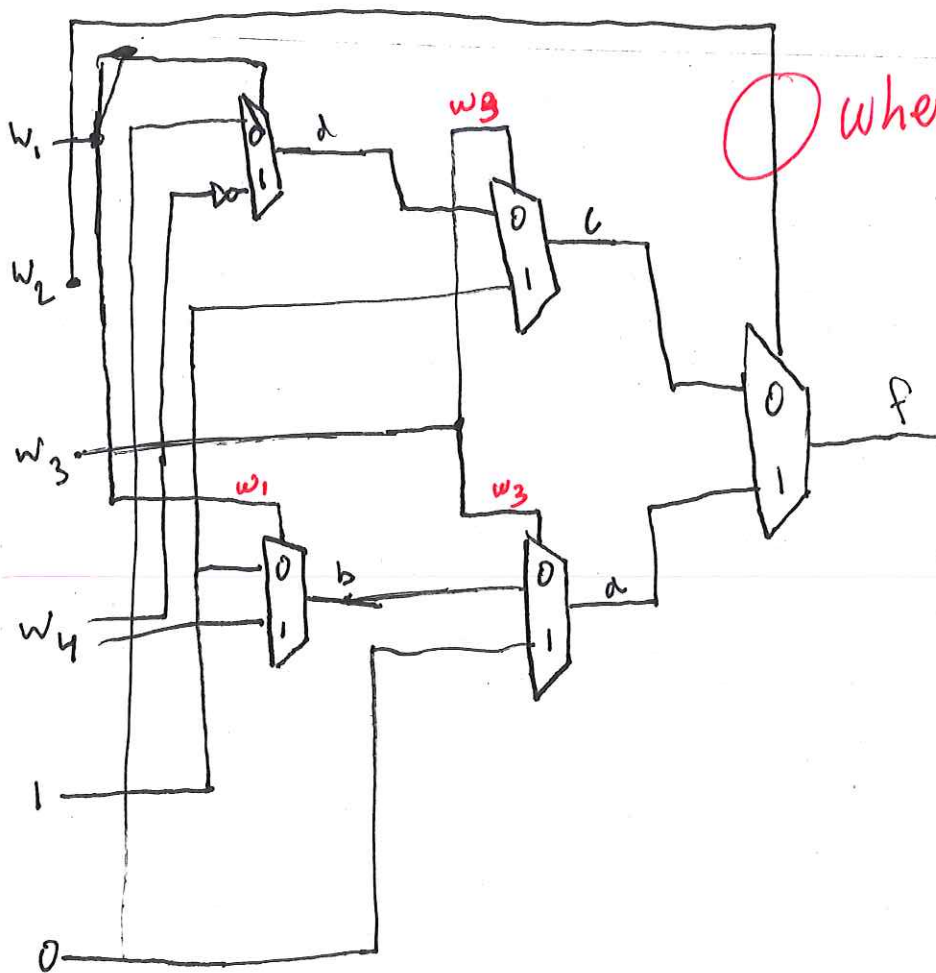
$$\bar{w}_2 (w_3(1) + \bar{w}_3 (w_1(0) + w_1(\bar{w}_4)) + w_2 (\bar{w}_3 (\bar{w}_1(1) + w_1(w_4)) + w_3(0))$$



where is it connected?  
w2 or w1?

30  
complicated explanation



# Problem 2

$$f(w, x, y, z) = \prod M(1, 7, 12, 13, 14, 15)$$

•  $d(0, 2, 8, 10)$

a.

w	x	y	z	f
0	0	0	0	d
0	0	0	1	0
0	0	1	0	d
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	d
1	0	0	1	1
1	0	1	0	d
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

b.

⑤

wx \ yz	00	01	11	10
00	d	1	0	d
01	0	1	0	1
11	1	0 <sup>2</sup>	0	1
10	d	1	0	d

② ④ ③ ①

⑤





# Problem 2

C. SOP:  $f = w \cdot \bar{x} + \bar{x} \cdot y + \bar{w} \cdot \bar{z} + \bar{w} \cdot x \cdot \bar{y}$  (5)

POS:  $f = \cancel{\bar{w} \cdot \bar{x} \cdot \bar{y}} + \cancel{x \cdot y \cdot z} + \cancel{w \cdot x}$

$$= (w + x + y) \cdot (\bar{x} + \bar{y} + \bar{z}) \cdot (\bar{w} + \bar{x})$$

(5)



d. SOP structural Verilog:

```
module problem2d (w, x, y, z, f);
```

```
    input w, x, y, z;
```

```
    output f;
```

```
    not (a, w);
```

//  $a = \overline{w}$

```
    not (b, x);
```

//  $b = \overline{x}$

```
    not (c, y);
```

//  $c = \overline{y}$

```
    not (d, z);
```

//  $d = \overline{z}$

```
    and (h, w, b);
```

```
    and (i, b, y);
```

```
    and (j, a, d);
```

```
    and (k, a, x, c);
```

```
    or (f, h, i, j, k);
```

```
endmodule
```

5

+10



Problem 3:

$$F = (\overline{A\overline{B}} \cdot \overline{A+C}) + \overline{\overline{A}B \cdot A+C}$$

Properties used:

DeMorgan's Theorem:

$$\overline{X \cdot Y} = \overline{X} + \overline{Y}$$

Note:  $X \rightarrow \overline{A}B$

$Y \rightarrow A+C$

(1) Associative property

(2)  $\overline{\overline{X}} = X$

DeMorgan's Theorem:

$$\overline{X+Y} = \overline{X} \cdot \overline{Y}$$

$$\overline{X+Y+Z} = \overline{X} \cdot \overline{Y} \cdot \overline{Z}$$

$$\overline{\overline{X}} = X$$

Commutative property

Factoring/  
Distributive property

Disable Property:

$$X+1=1$$

Enable Property:

$$X \cdot 1 = X$$

Commutative Property

$$X + \overline{X} \cdot Y = X + Y$$

Commutative Property

$$X = \overline{\overline{X}}$$

(1) DeMorgan's Theorem:

$$\overline{X+Y+Z} = \overline{X} \cdot \overline{Y} \cdot \overline{Z}$$

(2)  $\overline{\overline{X}} = X$

$$= \overline{A\overline{B}} + \overline{A+C} + \overline{\overline{A}B + A+C}$$

$$= \overline{A\overline{B}} + \overline{A+C} + \overline{\overline{A}B} + \overline{A+C}$$

THIS IS WRONG  $\downarrow (\overline{A\overline{B}}) \cdot \overline{A} \cdot \overline{C} = (\overline{A}+B) \cdot \overline{A} \cdot \overline{C}$  This is the correct

$$= (\overline{A} + B) \cdot \overline{A} \cdot \overline{C} + \overline{A\overline{B}} + \overline{A+C}$$

$$= (\overline{A} + B) \cdot \overline{A} \cdot \overline{C} + \overline{A\overline{B}} + \overline{A+C}$$

$$= \overline{C} + (\overline{A} + B) \cdot \overline{A} \cdot \overline{C} + \overline{A\overline{B}} + A$$

$$= \overline{C} (1 + (\overline{A} + B) \cdot \overline{A}) + \overline{A\overline{B}} + A$$

$$= \overline{C} \cdot 1 + \overline{A\overline{B}} + A$$

$$= \overline{C} + \overline{A\overline{B}} + A$$

$$= \overline{C} + A + \overline{A}B$$

$$= \overline{C} + A + B$$

$$= A + B + \overline{C}$$

$$= \overline{\overline{A+B+C}}$$

$$= \overline{A \cdot B \cdot C}$$



Continued for Problem 3:


$$F = \overline{A \cdot B \cdot C}$$

$$= \overline{A \cdot 1 \cdot B \cdot 1 \cdot C}$$

Reverse Enable Property:

$$X = X \cdot 1$$

Simplified Circuit:

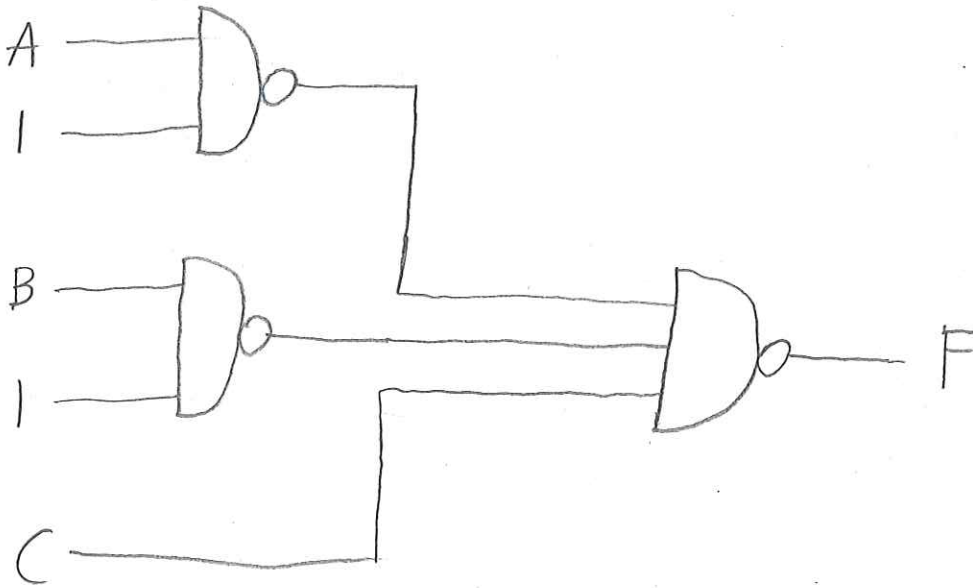

25

//

