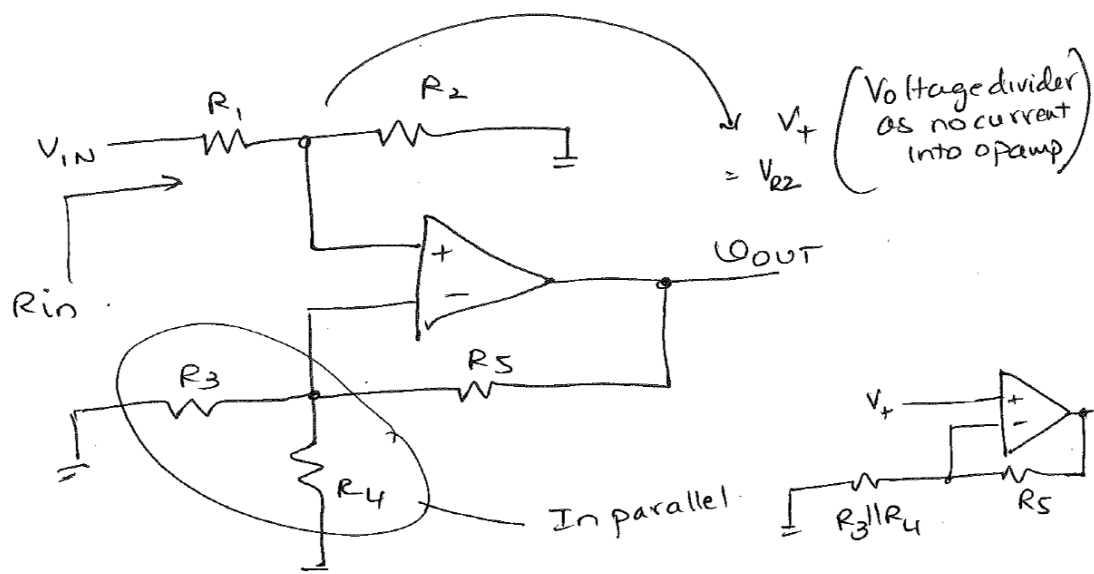


SANTA CLARA UNIVERSITY	ELEN 115 – Spring 2023	S. Krishnan
Homework #3 Solutions		

1.



(a) Noninverting Amplifier.

$$V_+ = V_{IN} * \frac{R_2}{R_1 + R_2}$$

$$V_{OUT} = \left(1 + \frac{R_5}{R_3 || R_4}\right) V_+$$

$$\frac{V_{OUT}}{V_{IN}} = \left(\frac{R_2}{R_1 + R_2}\right) \left(1 + \frac{R_5}{R_3 || R_4}\right)$$

$$R_{in} = R_1 + R_2 \quad \left[\begin{array}{l} \text{Current flow into } R_1 \\ \text{none into opamp all to } R_2 \text{ \& GND} \end{array} \right]$$

(a) Also can solve by doing KCL @ V_+ & V_-

At V_+ $\frac{V_{IN} - V_+}{R_1} = \frac{V_+ - 0}{R_2} \Rightarrow V_+ = V_{IN} * \frac{R_2}{R_1 + R_2}$

At V_- $\frac{0 - V_-}{R_3} + \frac{0 - V_-}{R_4} + \frac{V_{OUT} - V_-}{R_5} = 0$

$V_+ = V_-$ & so get

(b) $R_1 = 5K$ $R_2 = 10K$ $R_3 = 6K$ $R_4 = 3K$ $R_5 = 4K$


$$\frac{V_{OUT}}{V_{IN}} = \frac{10K}{5K + 10K} \left[1 + \frac{4K}{6K || 3K} \right] = \frac{2}{3} [1 + 2] = 2$$


$$V_{IN}(t) = 2 \sin 2\pi t \quad V_{OUT}(t) = 2 * V_{IN} = 4 \sin 2\pi t$$

(c) $V_{OUT} \text{ max} = +10 \text{ min} = -10$

$$V_{IN} = \frac{V_{OUT}}{\text{gain}} = \frac{V_{OUT}}{2} \Rightarrow V_{IN \text{ max}} = \frac{10}{2}$$

$$\Rightarrow V_{IN} = 5 \sin 2\pi t$$

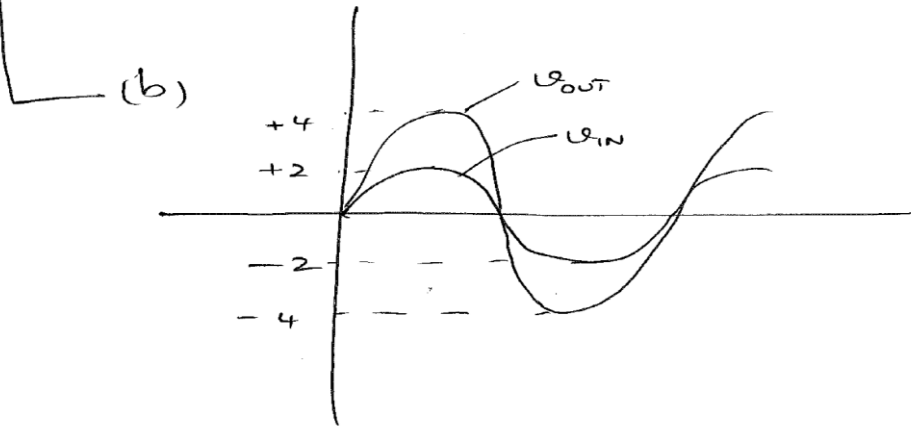

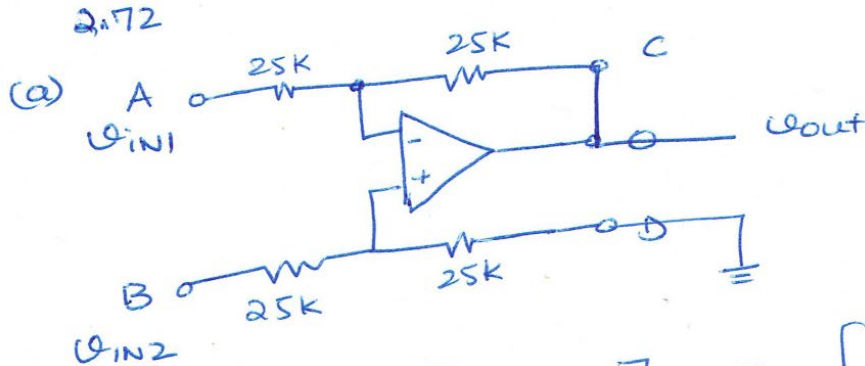


$$V_{out} = V_{in2} \left[\frac{25K}{25K+25K} \right] \left[1 + \frac{25K}{25K} \right] + V_{in1} \left[\frac{-25K}{25K} \right]$$


$$V_{out} = V_{in2} - V_{in1}$$

(b)(i) $-1 \Rightarrow$ inverting amplifier
 $B=0$ $D=0$ V_{in} At A $C \& O$ connected
 $V_{out} = V_{in} \left[\frac{-25K}{25K} \right] \Rightarrow \frac{V_{out}}{V_{in}} = -1$

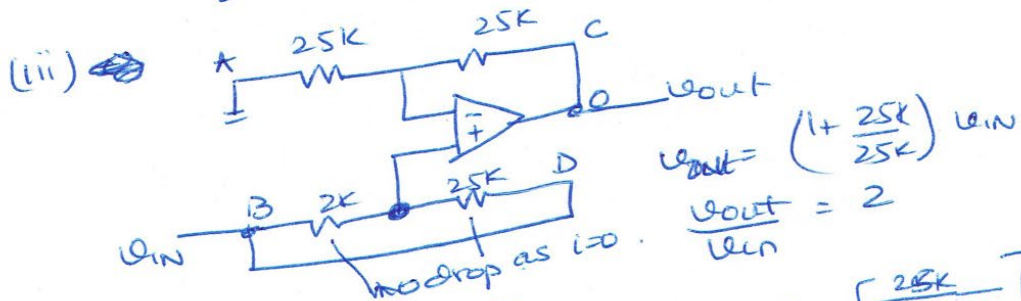(ii) $+1 \Rightarrow$ noninverting amplifier
 $A=0$ $D=0$ $C \& O$ connected V_{in} @ B
 $V_+ = \frac{1}{2} V_{in}$ $V_{out} = \frac{1}{2} V_{in} \left[1 + \frac{25K}{25K} \right] \Rightarrow \frac{V_{out}}{V_{in}} = 1$




(iv)

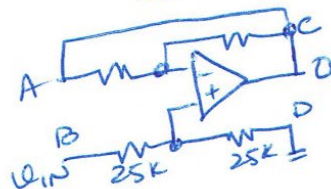


$$V_+ = V_{in} \left[\frac{25K}{25K+25K} \right] = \frac{V_{in}}{2}$$

$$V_o = V_- = V_+ \Rightarrow \frac{V_o}{V_{in}} = \frac{1}{2}$$

3.

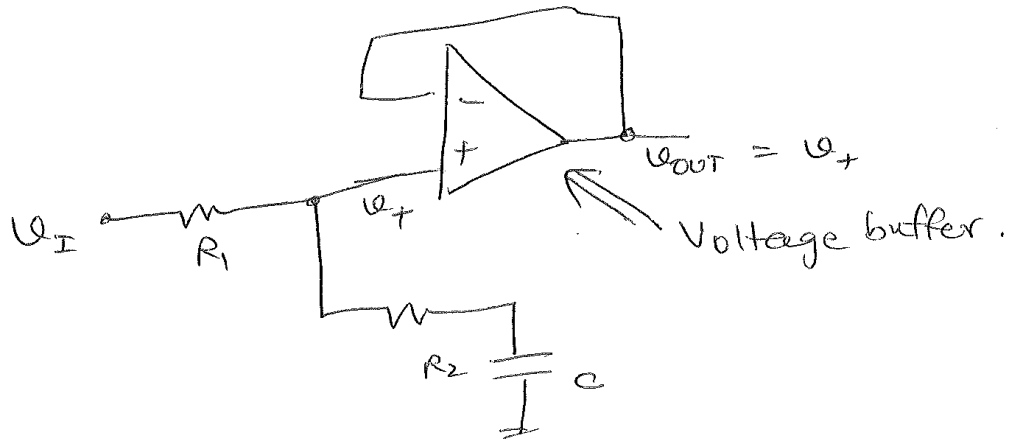

(a) $\omega = 0$ $C = \text{open}$

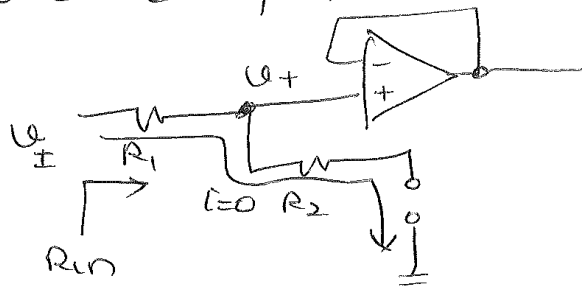


$$i = 0 \Rightarrow R_{in} = \infty$$

$$\Rightarrow u_+ = u_I$$

$$\Rightarrow u_o = u_+ = u_I$$

$$\frac{u_o}{u_I} = 1$$

(b) $\omega = \infty$ $C = \text{short}$

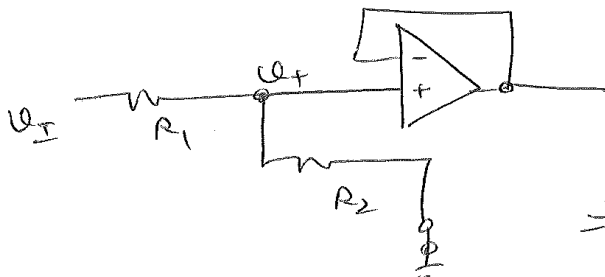


$$i = \frac{u_I - 0}{R_1 + R_2} \Rightarrow R_{in} = R_1 + R_2$$

$$u_+ = \frac{R_2}{R_1 + R_2} u_I$$

$$\Rightarrow u_o = u_I \times \frac{R_2}{R_1 + R_2}$$

(c)

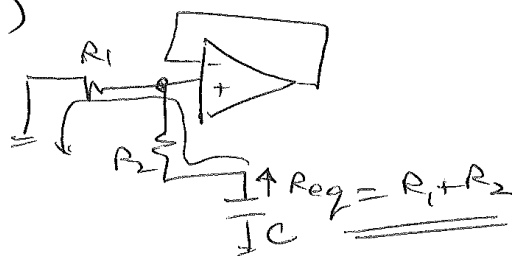

$$\Rightarrow \frac{u_o}{u_I} = \frac{R_2}{R_1 + R_2}$$

$$f_o = \frac{1}{2\pi R_{eq} C} = \frac{1}{2\pi (R_1 + R_2) C}$$

$$R_1 = 1K \quad R_2 = 500\Omega \quad C = 1\mu F \quad \pm 5V \text{ sat voltage.}$$

$$f_0 = \frac{1}{2\pi(1.5K)1\mu F} = 106.10 \text{ Hz}$$

$$\frac{V_0}{V_i} = 1 \quad f < 106.1 \text{ Hz}$$

$$\frac{V_0}{V_i} = \frac{500}{500+1000} = \frac{1}{3} \quad f > 106.1 \text{ Hz}$$


$$(i) \quad V_{in}(t) = 2 + 5 \sin 2\pi t$$

\downarrow $f=0$ \downarrow $f=1 \text{ Hz}$ $\omega=2\pi$ $\omega=2\pi f$

\Rightarrow Both 0 & 1 Hz get multiplied by gain = 1

$\Rightarrow V_{out}(t) = 2 + 5 \sin 2\pi t$

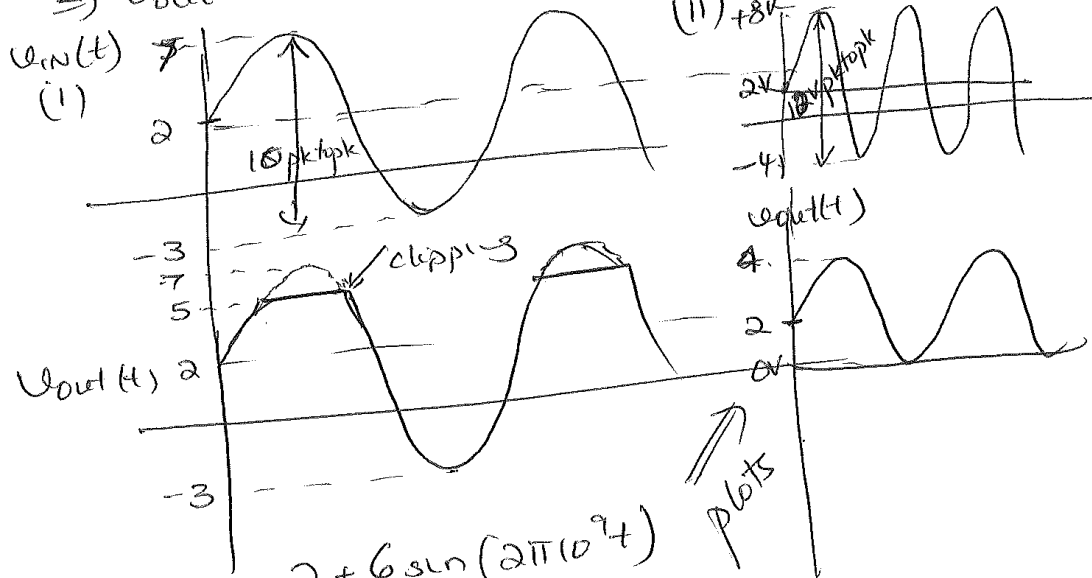max $2+5=7$ will get clipped
min $2-5=-3$ No clipping



$$(ii) \quad V_{in}(t) = 2 + 6 \sin(2\pi 10^9 t)$$

\downarrow $f=0$ \downarrow $f=10^9 \text{ Hz}$

$\times 1$ $\times \frac{1}{3}$

$$V_{out}(t) = 2 + \frac{1}{3} \times 6 \sin 2\pi 10^9 t$$

$$= 2 + 2 \sin 2\pi 10^9 t$$

max $2+2=4$ No clipping
min $2-2=0$ No clipping