

SANTA CLARA UNIVERSITY	ELEN 115 Spring 2023	Shoba Krishnan
Laboratory #5: Diode Rectifiers		


PRE-LAB

1. For the diode circuit shown in Figure 1, consider the diode to be ideal. The input voltage v_I given to the circuit is a sinusoid with a peak value of 10V.

For the circuit

- Derive the expression for the transfer characteristic v_{OUT} versus v_I for the circuit.
- Plot the transfer characteristic v_{OUT} versus v_I indicating the values of all significant points and the values of the slopes of all segments.
- Draw the corresponding output voltage v_{OUT} vs. time for two cycles of the the input v_I
- Find the peak diode current.
- Find the maximum reverse voltage seen by the diode.

Figure 1

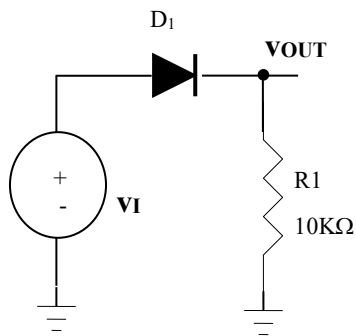

- If a capacitor is connected **instead of** the resistor $R1$ in Figure 1, draw the corresponding output voltage v_{OUT} vs. time for two cycles of the the input v_I .
- If a capacitor is connected **in parallel with** the resistor $R1$ in Figure 1, draw the corresponding output voltage v_{OUT} vs. time for two cycles of the the input v_I .