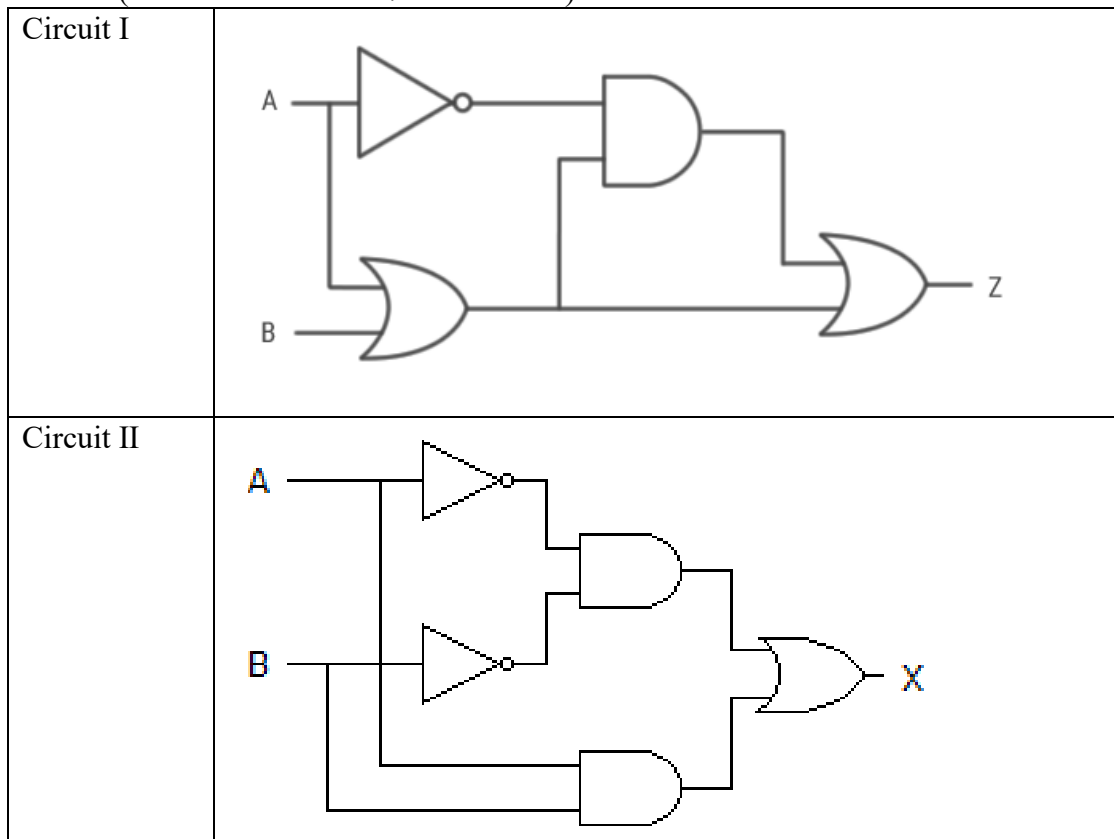


## Homework 1

ELEN 21/COEN 21

Instructor: Maria Kyrarini

- Convert the following binary numbers to their decimal equivalents. Explain your solutions.
  - 001100
  - 11100
  - 000111100
  - 101010
- Draw the logic symbol for a 7-input AND gate. Label the inputs A, B, C, D, E, F, and G and the output Y.
  - Draw the logic symbol for a 5-input OR gate. Label the inputs A, B, C, D, and E, and the output Y.
- Analyze the following circuits by writing the truth table and the timing diagram (hint: Look at slide 27 of Lecture 1):



- Synthesize a simplified circuit for the following truth table by:

- a) Using only properties of Boolean Expressions,  
 b) Using K-maps.  
 Use only AND, OR, and NOT gates.

**Truth table**

Inputs			Output
C	B	A	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

5. Synthesize a simplified circuit for the following truth table by:  
 c) Using only properties of Boolean Expressions,  
 d) Using K-maps.  
 Use only AND, OR, and NOT gates.

**Truth table**

Inputs				Output
D	C	B	A	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1