

Santa Clara University	ELEN 115 Spring 2023	Dr. Shoba Krishnan
Laboratory #2: Single time constant circuits		

I. Objectives

- To construct a simple RC single time constant circuit and do transient analysis in LTSpice.
- To understand frequency behavior and do ac analysis for simple RC circuits.

II. Laboratory Procedure:

Part 1: Schematic Capture

For this part of the lab, please create the single time constant circuit shown in Figure 1 in LTSpice.

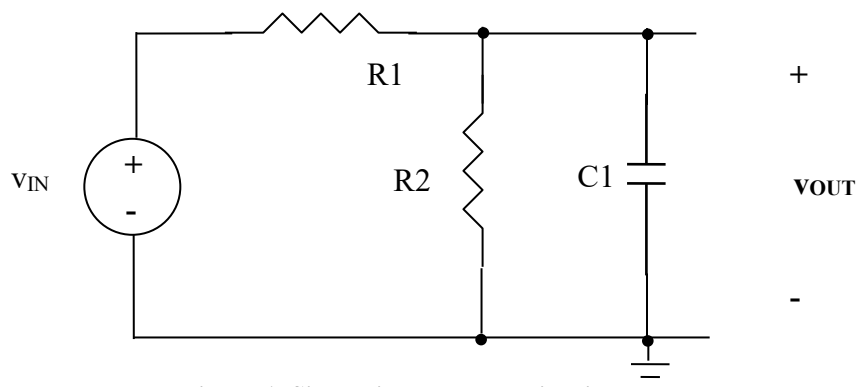


Figure 1. Single time constant circuit

Part 2: Transient Analysis- Pulse Input

- (1) Assign component value for $R1 = 20k\Omega$, $R2 = 20k\Omega$ and $C1 = 0.1\mu F$.
- (2) Make V_{IN} a pulse input that goes from 0V to 10V and has a pulse width of 10msec and period of 20msec. The rise and fall times should both be 1nsec. Set V_{IN} pulse delay time = 0.
- (3) Set the initial condition on the capacitor to be 0V.
To do this, make a SPICE directive with the following text: “.ic V(Vout)=0” where Vout is the name of the output node.
- (4) Run a Transient Analysis for 50ms, using a 10us time step.
- (5) Plot V_{IN} and V_{OUT} as a function of time on the same plot.

Do the results look as expected? Why or why not?

Make sure to take a screen capture of the simulation waveforms.

- (6) Change the V_{IN} pulse width and period (and transient runtime) to produce a full charge/discharge V_{out} wave. How many time constants does it take to reach steady state.
- (7) Plot $C \cdot dV_{out}/dt$ (use: $1e-6 \cdot D(V(Vout))$).
- (8) Plot current i_{OUT} as a function of time.
What does the plot show? Explain its shape. Verify if i_{OUT} is the same as your plot in (6)
Make sure to take a screen capture of the simulation waveforms.
- (9) Modify the initial condition on the capacitor $C1$ to 1V. Rerun the simulations and replot.
How did the waveforms change? Explain why?
Make sure to take a screen capture of the simulation waveforms.
- (10) Modify the value of $C1 = 10\mu F$. Rerun the transient simulations and replot the signals.
How did the waveforms change? Explain why?

Santa Clara University	ELEN 115 Spring 2023	Dr. Shoba Krishnan
Laboratory #2: Single time constant circuits		

Make sure to take a screen capture of the simulation waveforms.

TA Check Point: Complete Part 1 and Part 2 and demo the results to your TA.

Part 3: AC analysis

- (1) Assign component value for $R1 = 20k\Omega$, $R2 = 20k\Omega$ and $C1 = 0.1\mu F$. Initial condition of 0V on the capacitor.
- (2) V_{IN} is a sinusoidal source. Set the small signal AC analysis amplitude to 1.
- (3) Simulate using AC Analysis. Sweep type: Decade.
Number of Points per decade: at least 5. Start frequency: 1Hz. Stop Frequency 100kHz.
Use cursors to measure the slope of the line to verify -20dB/decade
Measure the -3dB frequency to verify the time constant and cutoff frequency.

Screen Capture the Bode plot of magnitude and phase of v_{out}/v_{in} .

TA Check Point: Complete Part 4 and demo the results to your TA.

Physical Circuit Build

Build the circuit in Figure 1 with components $R1 = 20k\Omega$, $R2 = 20k\Omega$ and $C1 = 0.1\mu F$. For the circuit build of Figure 1 we would like to observe its output to input of various frequencies and understand its frequency behavior. The following parts helps us make observations regarding this passive filter.

Part 4: Transient input

- (1) Build the circuit in Figure 1 with components $R1 = 20k\Omega$, $R2 = 20k\Omega$ and $C1 = 0.1\mu F$.
- (2) Connect the signal generator as the voltage source v_{IN} with a sinusoidal input with 1V amplitude and 1Hz frequency. Connect an oscilloscope at the output to monitor the voltage.
- (3) Observe v_{IN} and v_{OUT} on the oscilloscope. Zoom in to see two to three time periods.
Do the results look as expected? Why or why not?
Make sure to take a screen capture of the measured waveforms.
- (5) Make v_{IN} a sinusoidal input with 1V amplitude and 10Hz frequency. Repeat step 3.
- (6) Make v_{IN} a sinusoidal input with with 1V amplitude and 100Hz frequency. Change the transient duration to 10msec. Repeat step 3.
- (7) Make v_{IN} a sinusoidal input with with 1V amplitude and 1kHz frequency. Change the transient duration to 1msec. Repeat step 3.
- (8) What have you observed while doing steps (2) through (7)? What behavior does this RC circuit show?

TA Check Point: Complete Part 3 and demo the results to your TA.

III. REPORT

Write a short laboratory report that details all the work done **and** answer the following questions:

- What is the RC time constant when $R1 = 20k\Omega$, $R2 = 20k\Omega$ and $C1 = 0.1\mu F$?
- From part 2, what did you understand is the relationship between i_{OUT} (current in capacitor) and v_{OUT} (voltage across the capacitor)
- Draw the schematic of a single time constant high pass filter. What will be the value of the R and

Santa Clara University	ELEN 115 Spring 2023	Dr. Shoba Krishnan
Laboratory #2: Single time constant circuits		

- C to obtain a cutoff frequency $1/10^{\text{th}}$ of the low pass filter you created in the lab.
- If we took the output of the high-pass-filter you just designed and made that the input of the low-pass filter of the lab, what sort of behavior do we expect at the output of the combined circuit? Draw a rough bode plot sketch of this behavior.