

SANTA CLARA UNIVERSITY	ELEN 115 Spring 2023	Shoba Krishnan
Project 2: Power Supply Design		

I. OBJECTIVES

- To design of a DC power supply.
- To construct the circuit in the laboratory and record sufficient measurements to establish circuit operation in accordance with design objectives.

II. Analysis

The need exists for a small 5 VDC power source capable of delivering a load current to a 2.5K resistive load.

1. Rectifier Design:

It is decided to use a half-wave rectifier using 1N 4001 diode with a simple capacitor filter as shown in Fig.1.

The input voltage is obtained from a transformer that gives a 120Vrms 60 Hz sinusoid at the primary and a 31.8V peak to peak across the secondary (keeping the center tap floating).

- (1) Find the value of the load current for the given specifications
- (2) Identify the turns ratio of the transformer
- (3) Find the value of the capacitor needed to obtain a peak to peak ripple of 2V.

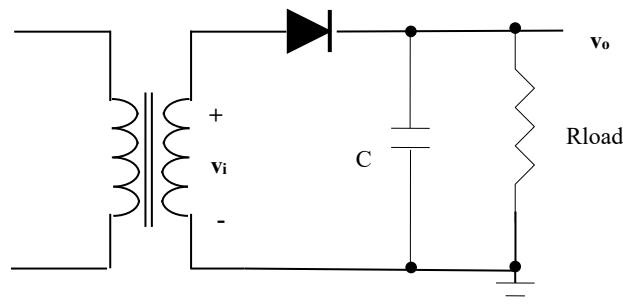


Fig.1: Half Wave Rectifier with Simple Capacitor Filter

2. Regulator:

In order to reduce the ripple voltage applied to the load without increasing the size of the filter capacitor, it is decided to use a 5.1 volt Zener diode (1N751A) with the original design as shown in Fig. 2.

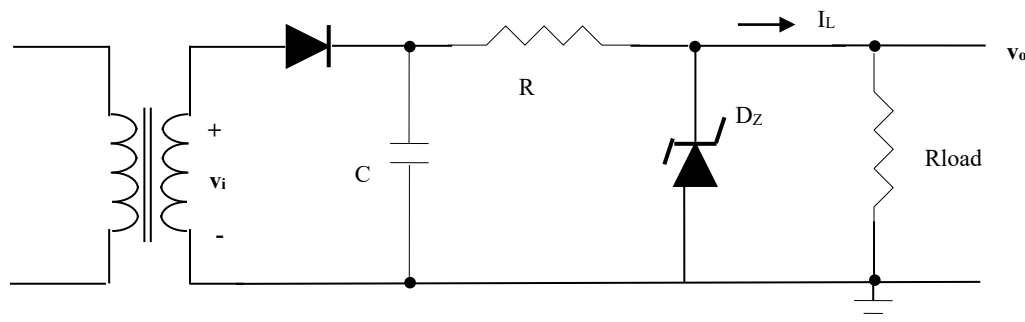


Fig.2: Power supply Design with Zener Regulator

- (1) Look up the Zener diode data sheet to obtain the dynamic zener resistance and test data point.
- (2) Determine a value for R that will supply the maximum required load current of calculated from part 1 to the resistive load and provide a minimum Zener current of 3.5mA.

Hint: Use minimum supply voltage, minimum Zener current and maximum load current when finding the R value.

Develop a test plan by answering the below questions

- (1) How would you ensure that the rectifier action is happening?
- (2) How would you know if the ripple specifications are being met?
- (3) How would you know the load is getting the current it needs?
- (4) How would you measure the output voltage ripple and ensure it has improved after the zener shunt regulator has been added?
- (5) How would you measure load regulation?
- (6) How would you find the maximum load current possible for this power supply?