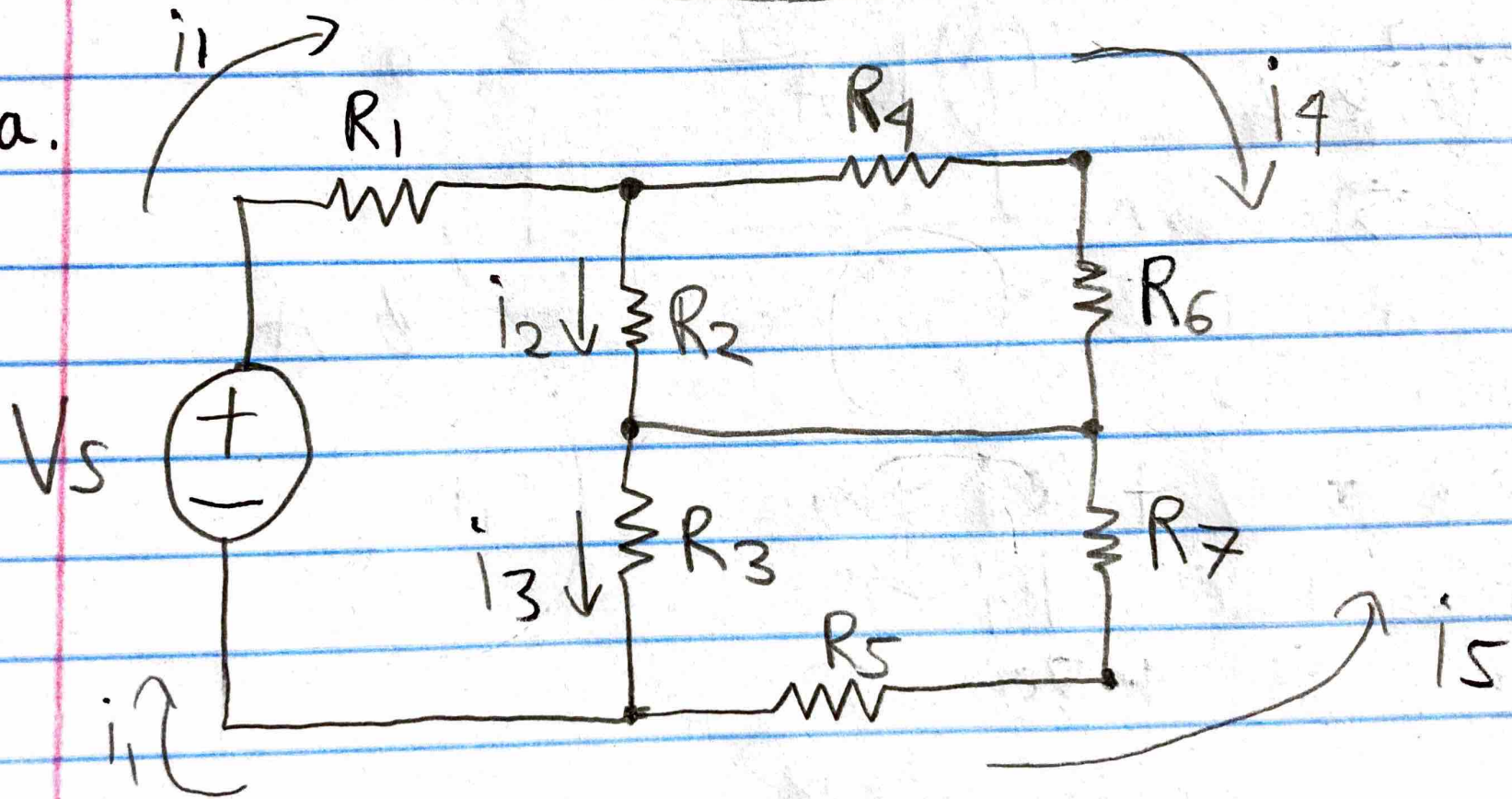


Name: Mulia Widjasa

Homework #4

4.3. a.



There are 5 unknown currents.

b. 4 essential nodes \rightarrow 3 independent equations

$$\left. \begin{aligned} i_1 - i_2 - i_4 &= 0 \\ i_1 - i_2 - i_3 &= 0 \\ -i_1 + i_3 - i_5 &= 0 \end{aligned} \right\} \text{Set of 3 KCL equations}$$


d. 5 Variables need 5 equation to solve.

3 KCL Equations \rightarrow Set up

Also, 2 meshes \rightarrow 2 KVL equations

$$\begin{aligned} \text{e. } -V_s + i_1 R_1 + i_2 R_2 + i_3 R_3 &= 0 \\ -i_2 R_2 + i_4 (R_4 + R_6) &= 0 \\ i_3 R_3 + i_5 (R_5 + R_7) &= 0 \quad // \end{aligned}$$

7.10.

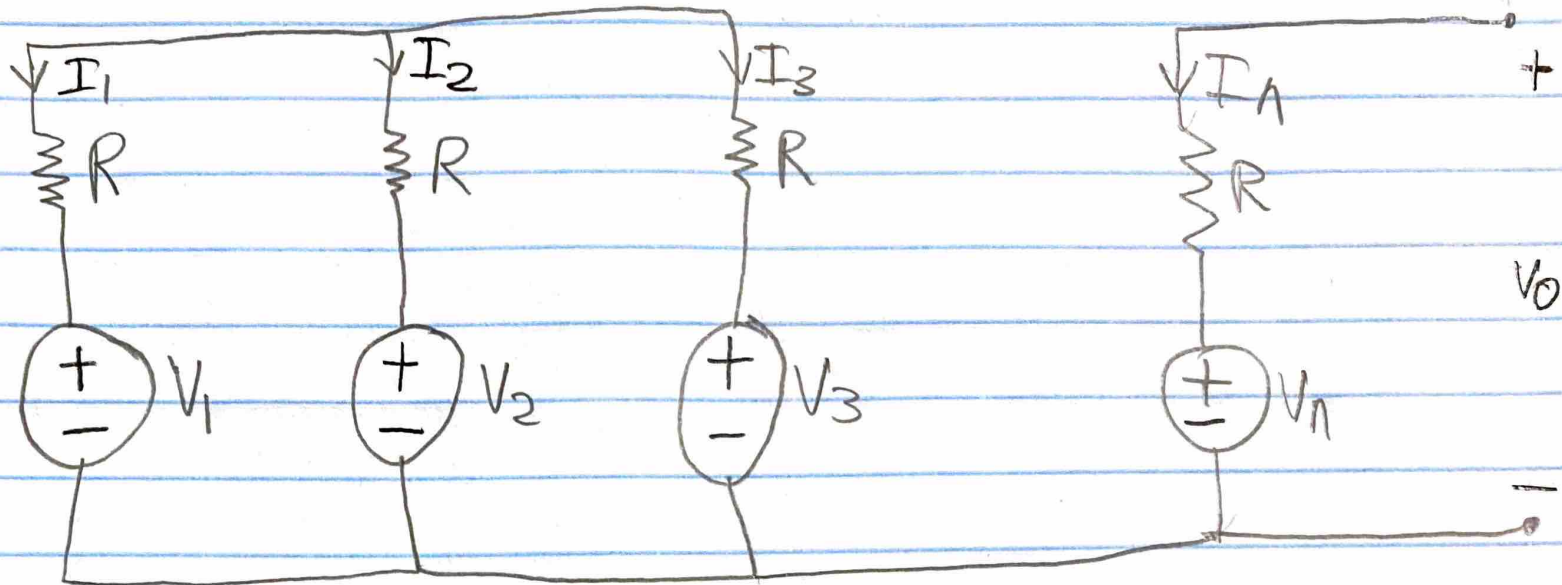

$$a. \frac{V_0 - V_1}{R} + \frac{V_0 - V_2}{R} + \frac{V_0 - V_3}{R} + \dots + \frac{V_0 - V_n}{R} = 0$$

$$V_0 \left(\frac{n}{R} \right) = \frac{V_1 + V_2 + V_3 + \dots + V_n}{R} \cdot \frac{R}{n}$$


$$V_0 = \frac{V_1 + V_2 + V_3 + \dots + V_n}{n} \quad (\text{Demonstrated}) //$$

4.10.

b.

$$V_0 = \frac{100 + 80 - 60}{3} = \textcircled{40 \text{ V}} //$$

4.16.

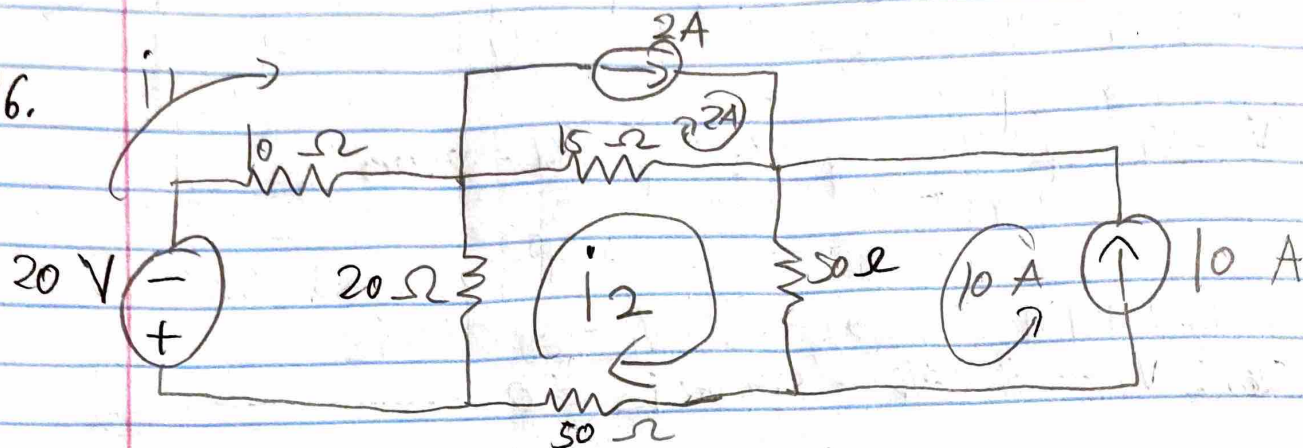

$$-20 + 10i_1 + 20(i_1 + i_2) = 0$$

$$-15(2) + 50(10 + i_2) + 50i_2 = 0$$

$$30i_1 + 20i_2 = 20$$

$$100i_2 = -470$$

$$1.5i_1 + i_2 = 1$$

$$i_2 = -4.7$$

$$1.5i_1 = 5.7 \rightarrow i_1 = 3.8$$

$$30i_1 + 20i_2 = 20$$

$$30(3.8) + 20i_2 = 20$$

$$20i_2 = -94$$

$$i_2 = -4.7 \text{ A}$$

| Power Sources | V | i | P (W) |
|---------------|-----|-----|-------|
| 20 V | 20 | 3.8 | -76 |
| 10 A | 500 | 10 | -5000 |
| 2 A | 30 | 2 | -60 |

Total Power
Dissipated
= 5136 W

$$4.9. a. \frac{V_1 - V_2}{1250} + \frac{V_1}{1000} + 20 \cdot 10^{-3} = 0$$

$$\begin{aligned} V_1 (1 + 1.25) - V_2 &= -25 \\ 2.25 V_1 - V_2 &= -25 \quad \text{--- (1)} \end{aligned}$$

$$\frac{V_2 - V_1}{1250} + \frac{V_2}{4000} + \frac{V_2}{2000} + \frac{V_2 - 2500 i_\Delta}{200} = 0$$

$$\begin{aligned} V_2 (3.2 + 1 + 2 + 20) - 3.2 V_1 - 50000 i_\Delta &= 0 \\ 26.2 V_2 - 3.2 V_1 - 50000 i_\Delta &= 0 \quad \text{--- (2)} \end{aligned}$$

$$i_\Delta = \frac{V_2 - V_1}{1250} \quad \text{--- (3)}$$

Substitute (3) in (2):

$$26.2 V_2 - 3.2 V_1 - 50000 \left(\frac{V_2 - V_1}{1250} \right) = 0$$

$$26.2 V_2 - 3.2 V_1 - 40 V_2 + 40 V_1 = 0$$

$$-13.8 V_2 + 36.8 V_1 = 0$$

$$-V_2 + \frac{36.8}{13.8} V_1 = 0 \quad \text{--- (4)}$$

Subt (4) w (1):

$$2.25 V_1 - \cancel{V_2} = -25$$

$$- \frac{36.8}{13.8} V_1 - \cancel{V_2} = 0$$

$$-0.42 V_1 = -25 \rightarrow V_1 = 60 \text{ V}$$

$$2.25(60) - V_2 = 25 \rightarrow V_2 = 160 \text{ V}$$

$$i_{\Delta} = \frac{V_2 - V_1}{1250} = \frac{160 - 60}{1250} = 0.08 \text{ A}$$

$$\begin{aligned} P_{20\text{mA}} &= V_1 \cdot 20 \cdot 10^{-3} \\ &= 60 \cdot 20 \cdot 10^{-3} \\ &= 1.2 \text{ W} \end{aligned}$$

$$\begin{aligned} P_{2500i_{\Delta}} &= 2500 i_{\Delta} \cdot i \\ &= 2500 i_{\Delta} \cdot \frac{V_2 - 2500 i_{\Delta}}{200} \\ &= -40 \text{ W} \end{aligned}$$

Conclusion:


$$\text{Total power developed} = \boxed{40 \text{ W}}$$

$$\begin{aligned} \text{b. } P_{\text{dissipated}} &= \frac{(V_1)^2}{1000} + 1250(i_{\Delta})^2 + \frac{(V_2)^2}{4000} + \frac{(V_2)^2}{2000} + i^2 \cdot 200 \\ &= \frac{60^2}{1000} + 1250(0.08)^2 + \frac{160^2}{4000} + \frac{160^2}{2000} + (-0.2)^2 \cdot 200 \\ &= 38.8 \text{ W} \end{aligned}$$

$$P_{\text{absorbed}} = P_{\text{dissipated}} + P_{20\text{mA}}$$

$$= 38.8 + 1.2$$
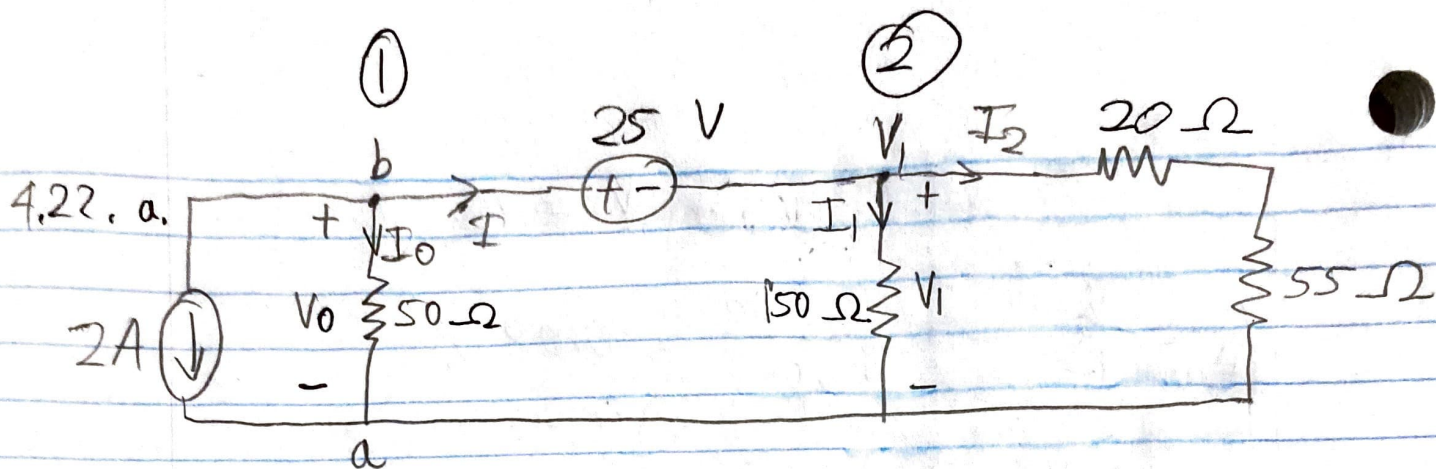
$$= \boxed{40 \text{ W}} \rightarrow \text{Total power absorbed}$$



$$\text{Eq ①: } I_0 = \frac{V_0}{50} \quad || \quad I_1 = \frac{V_1}{150} \quad || \quad I_2 = \frac{V_1}{55+20} = \frac{V_1}{75}$$

$$2 + \frac{V_0}{50} + \frac{V_1}{150} + \frac{V_1}{75} = 0$$

$$2 + \frac{V_0}{50} + \frac{V_1}{50} = 0$$

$$100 + V_0 + V_1 = 0$$

$$\text{Eq ②: } V_1 = V_0 - 25$$

$$\begin{array}{rcl} \cancel{V_0} + V_1 & = & -100 \\ + \cancel{-V_0} + V_1 & = & -25 \\ \hline 2V_1 & = & -125 \\ V_1 & = & -62.5 \text{ V} \end{array}$$

$$100 + V_0 - 62.5 = 0$$

$$V_0 + 37.5 = 0$$

$$V_0 = -37.5 \text{ V}$$

$$P = -2V_0 = -2(-37.5) = 75 \text{ W}$$

$$b. I_0 = \frac{V_a - V_0}{50} = \frac{-V_0}{50}$$

$$I_1 = \frac{V_a - V_1}{150} = \frac{-V_0 - (-25)}{150}$$

$$I_2 = \frac{V_a - V_1}{55 + 20} = \frac{-V_0 - (-25)}{75}$$

$$-2 - \frac{V_0}{50} - \frac{V_0 - 25}{150} - \frac{V_0 - 25}{75} = 0$$

$$-300 - 3V_0 - V_0 + 25 - 2V_0 + 50 = 0$$

$$-6V_0 - 225 = 0$$

$$-6V_0 = 225 \rightarrow V_0 = -37.5 \text{ V}$$

$$P = -2V_0 = -2(-37.5) = 75 \text{ W}$$