

Mulia Widjaja (Noble)  
Amanda Chah

NAMES: Harrison Goss

Group Number: 7

### In-Class Assignment 4

ELEN 21/COEN 21 – Fall 2022

Instructor: Maria Kyrarini

Date: 11/29/2022

Time: 1 hour and 20 minutes

Number of pages: 3

#### Important Notes:

- Be sure to read all the problems carefully and answer all questions.
- Be sure to answer all parts of each question.
- **Submit only one answer for each question.**
- Multiple solutions for one question will not be graded.
- **Clearly show all the steps of your work.**
- **Answers without explanation will not be graded.**
- The Engineering School Honor Code applies.

$$32 + 25 + 32 = 89$$



### Problem 1 (35 points)


Implement the circuit that accepts two binary numbers A and B and performs the operation  $A^B$  using two 2-to-4 decoders with enable and a minimum network of OR, NOT, AND gates. The number A consists of 2 bits ( $A = a_1a_0$ ) and B consists of 1 bit ( $B = b_0$ )

Reminder 1:  $0^0 = 1$ .

Reminder 2: Truth table and graphic symbol for 2-to-4 decoder with enable:

En	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

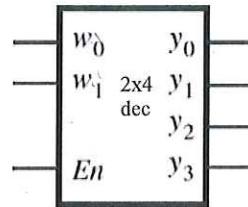


(b) Graphical symbol

### Problem 2 (30 points)

A Mealy-style state machine has an input  $w$  and an output  $z$ . The machine is a sequence detector that produces  $z = 1$  when it detects 1101; otherwise  $z = 0$ . Derive a circuit that realizes this state machine using one-hot encoding approach, T flip-flops and a network of AND-OR-NOT gates. **Note:** You do not need to draw the circuit – Show the Boolean expressions for the simplified circuit.
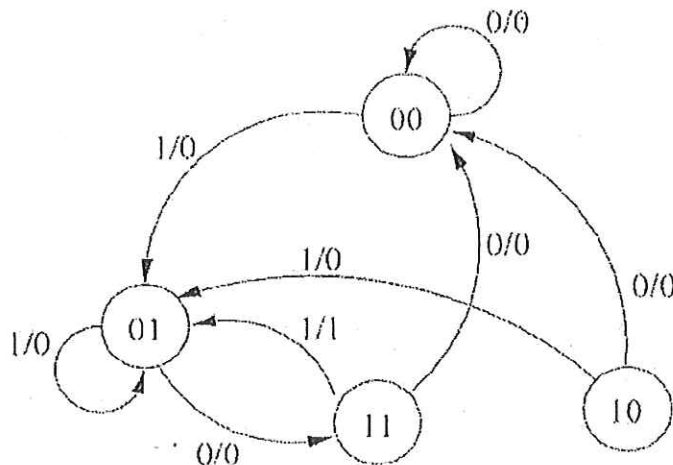
### Problem 3 (35 points)

Consider the following state diagram for a circuit with one input  $X$  and one output  $Z$ . Draw the circuit implementation of this state diagram using JK positive-edge flip-flop (state  $Q_0$ ), T positive-edge flip-flop (state  $Q_1$ ), and a minimal AND-OR-NOT-XOR network. The states are in the form  $Q_1Q_0$ .





## Boolean Algebra Properties

5a.	$x \cdot 0 = 0$	10a.	$x \cdot y = y \cdot x$	<i>Commutative</i>
5b.	$x + 1 = 1$	10b.	$x + y = y + x$	
6a.	$x \cdot 1 = x$	11a.	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	<i>Associative</i>
6b.	$x + 0 = x$	11b.	$x + (y + z) = (x + y) + z$	
7a.	$x \cdot x = x$	12a.	$x \cdot (y + z) = x \cdot y + x \cdot z$	<i>Distributive</i>
7b.	$x + x = x$	12b.	$x + y \cdot z = (x + y) \cdot (x + z)$	
8a.	$x \cdot \bar{x} = 0$	13a.	$x + x \cdot y = x$	<i>Absorption</i>
8b.	$x + \bar{x} = 1$	13b.	$x \cdot (x + y) = x$	
9.	$\bar{\bar{x}} = x$	14a.	$x \cdot y + x \cdot \bar{y} = x$	<i>Combining</i>
		14b.	$(x + y) \cdot (x + \bar{y}) = x$	
		15a.	$\overline{x \cdot y} = \bar{x} + \bar{y}$	<i>DeMorgan's theorem</i>
		15b.	$\overline{x + y} = \bar{x} \cdot \bar{y}$	
		16a.	$x + \bar{x} \cdot y = x + y$	<i>Consensus</i>
		16b.	$x \cdot (\bar{x} + y) = x \cdot y$	
		17a.	$x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$	
		17b.	$(x + y) \cdot (y + z) \cdot (\bar{x} + z) = (x + y) \cdot (\bar{x} + z)$	



# In-class Assignment - Group 7

① 2-to-4 decoder Behavior:

$$Y_0 = \overline{E_n} \overline{W_1} \overline{W_0}$$

$$Y_1 = \overline{E_n} \overline{W_1} W_0$$

$$Y_2 = \overline{E_n} W_1 \overline{W_0}$$

$$Y_3 = \overline{E_n} W_1 W_0$$

A <sup>B</sup> Expr	Inputs			Outputs			
	a <sub>1</sub>	a <sub>0</sub>	b <sub>0</sub>	X <sub>3</sub>	X <sub>2</sub>	X <sub>1</sub>	X <sub>0</sub>
0 <sup>0</sup> = 1	0	0	0	0	0	0	1
0 <sup>1</sup> = 0	0	0	1	0	0	0	0
1 <sup>0</sup> = 1	0	1	0	0	0	0	1
1 <sup>1</sup> = 1	0	1	1	0	0	0	1
2 <sup>0</sup> = 1	1	0	0	0	0	0	1
2 <sup>1</sup> = 2	1	0	1	0	0	1	0
3 <sup>0</sup> = 1	1	1	0	0	0	0	1
3 <sup>1</sup> = 3	1	1	1	0	0	1	1

By observation:  $X_3 = 0$  &  $X_2 = 0$

X<sub>1</sub> K-map:

a <sub>1</sub> a <sub>0</sub>	b <sub>0</sub>			
	00	01	11	10
0	0	0	0	0
1	0	0	1	1

$$X_1 = a_1 b_0$$

X<sub>0</sub> K-map:

a <sub>1</sub> a <sub>0</sub>	b <sub>0</sub>			
	00	01	11	10
0	1	1	1	1
1	0	1	1	0


$$X_0 = \overline{b_0} + a_0$$

Renew k-maps!






Question 1 cont.

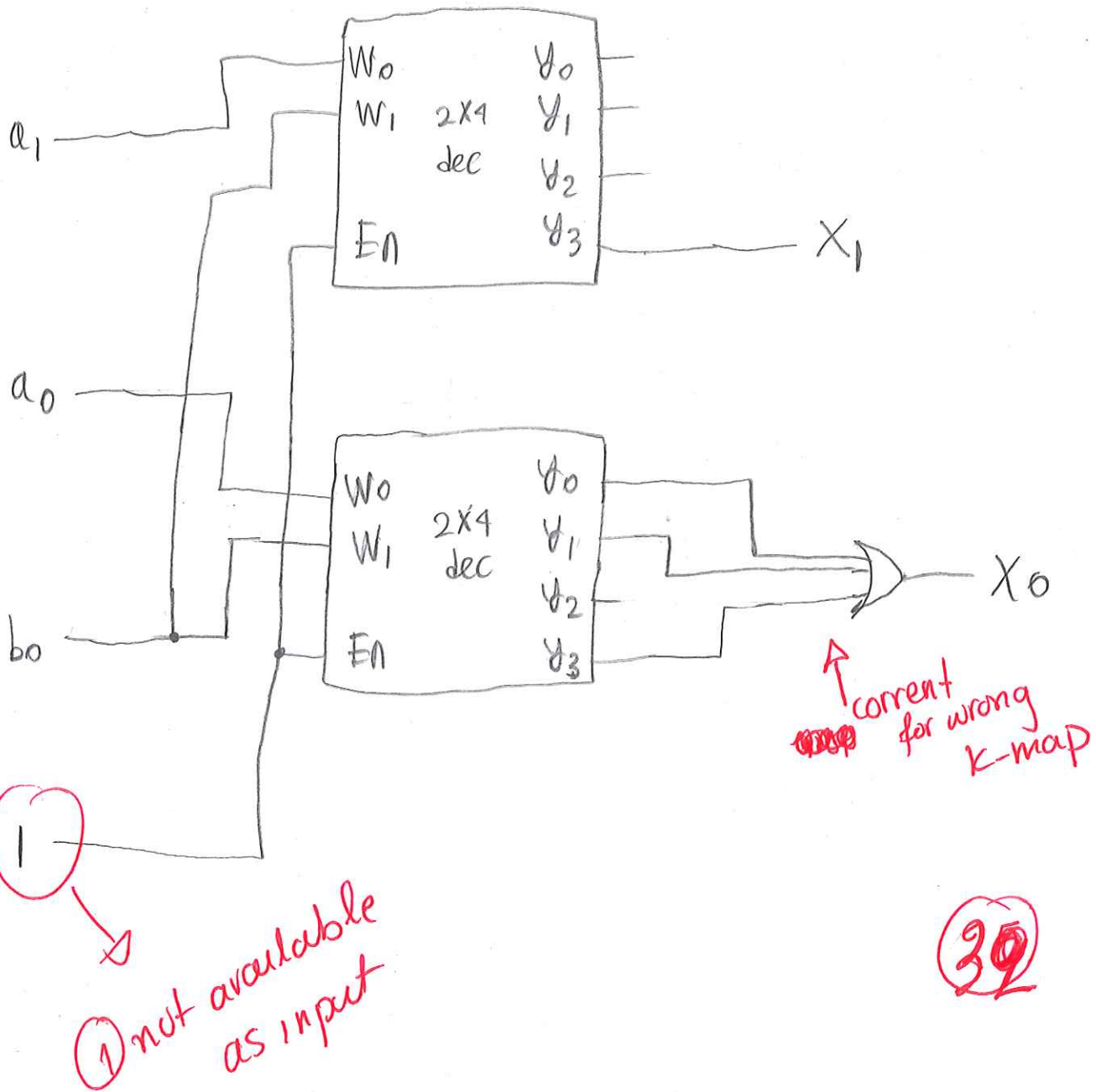



## ② State Diagram

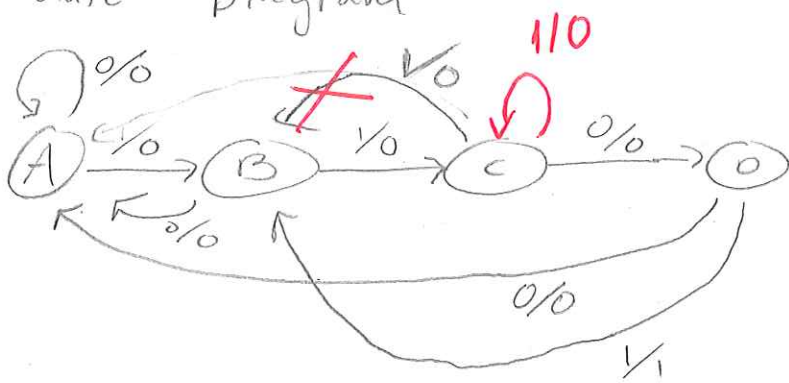

when the state machine is in state "c" it has seen 11. So if it sees one more 1, then it should remain in "c".

### State Assignment Table

	$Q_3 Q_2 Q_1 Q_0$	$w=0$	$w=1$	$z$
A)	1000	1000	0100	0
B)	0100	1000	0010	0
C)	0010	0001	0 <del>1</del> 00	0
	0001	1000	0100	1

	$Q_3 Q_2 Q_1 Q_0$	next state	$T_3$	$T_2$	$T_1$	$T_0$
	1000	1000	0	0	0	0
	0100	1000	1	1	0	0
$w=0$	0010	0001	0	0	1	1
	0001	1000	1	0	0	1
	1000	0100	1	1	0	0
	0100	0010	0	1	1	0
$w=1$	0010	0 <del>1</del> 00	0	<del>1</del> 0	1	0
	0001	0100	0	1	0	1

$$T_3 = (Q_2 + Q_0) \cdot \bar{w} + (Q_3 + Q_1) \cdot w = \cancel{(Q_2 + Q_0)} \oplus w$$

$$T_2 = Q_2 \cdot \bar{w} + Q_1 \cdot w$$

$$T_1 = Q_1 + w \cdot Q_2$$


$$T_0 = Q_0 + \bar{w} \cdot Q_1$$

$$z = Q_0 \cdot w$$

correct for wrong state machine



Circuit

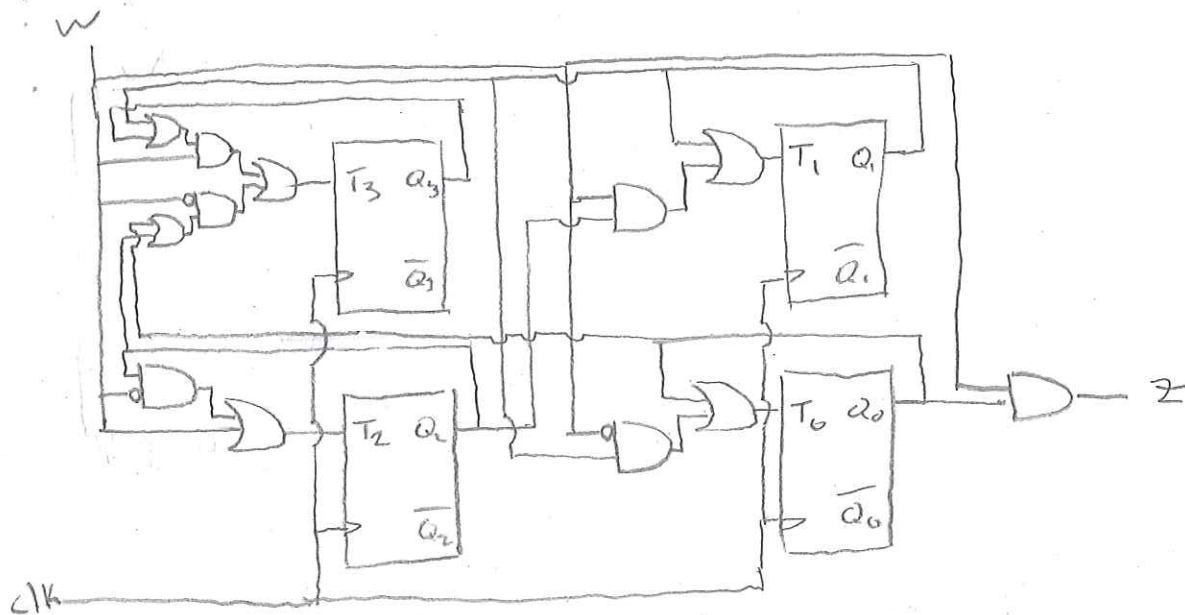



③

present		input	next	output	$T_1$	$J_0$	$K_0$
$q_1$	$q_0$	$x$	$q_1$ $q_0$	$z$			
0	0	0	0 0	0	0	0	d
0	0	1	0 1	0	0	1	d
0	1	0	1 1	0	1	d	0
0	1	1	0 1	0	0	d	0
1	0	0	0 0	0	1	0	d
1	0	1	0 1	0	1	1	d
1	1	0	0 0	0	1	d	1
1	1	1	0 1	1	1	d	0

$q_0$	$q_1$	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

$q_1$	$q_0$	$T_1$
0	0	0
0	1	1
1	0	1
1	1	0

$q_1, q_0$	00	01	11	10
$x$				
0	0	1	1	1
1	0	0	1	1

$q_1, q_0$	00	01	11	10
$x$				
0	0	d	d	0
1	1	d	d	1

$$T_1 = \bar{x}q_0 + q_1 \quad \checkmark$$


$$J_0 = x \quad \checkmark$$

$q_1, q_0$	00	01	11	10
$x$				
0	d	0	1	d
1	d	0	0	d

$$K_0 = \bar{x}q_1 \quad \checkmark$$

$q_1, q_0$	00	01	11	10
$x$				
0	0	0	0	0
1	0	0	1	0

$$z = xq_1q_0 \quad \checkmark$$

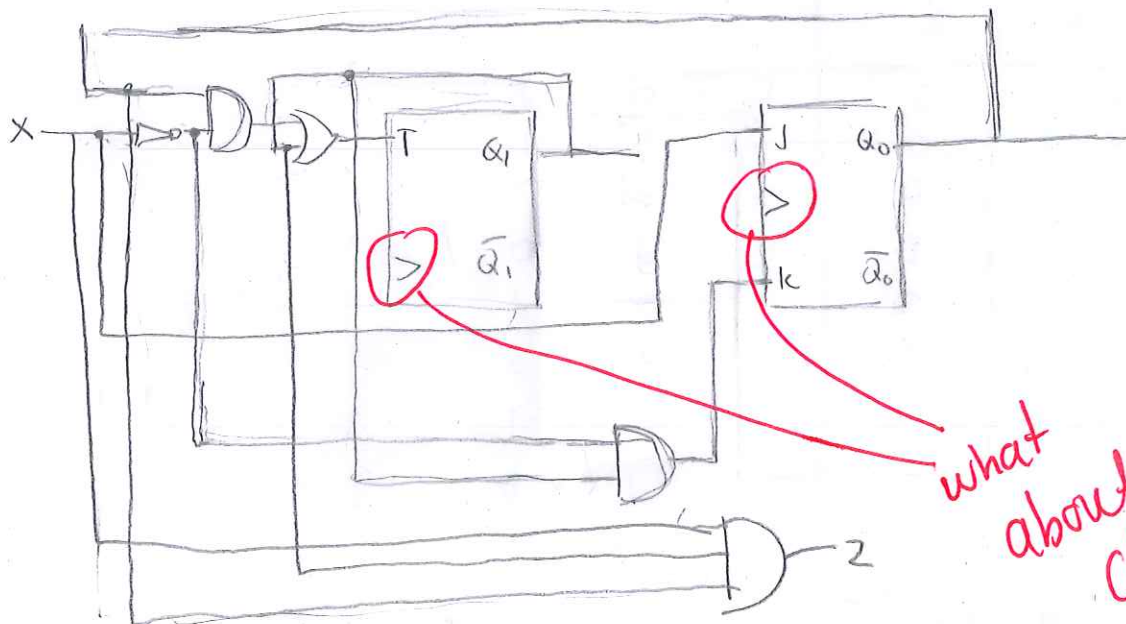

what  
about the  
clock?

32

2

$$T_1 = \bar{X}q_0 + q_1$$

$$J_0 = X$$

$$K_0 = \bar{X}q_1$$

$$Z = Xq_1q_0$$