

Group Number:

NAMES (FIRST AND LAST NAME):

In-Class Assignment 1

ELEN 21/COEN 21 – Fall 2022

Instructor: Maria Kyrarini

Date: 10/4/2022

Time: 1 hour and 20 minutes

Number of Problems: 3

Important Notes:

- Be sure to read all the problems carefully and answer all questions.
- Be sure to answer all parts of each question.
- **Submit only one answer for each question.** Multiple solutions for one question will NOT be graded.
- **Clearly show all the steps of your work.**
- **Answers without detailed explanations will NOT be graded.**
- The Engineering School Honor Code applies.

Problem 1 (30 points)

Implement the following function using only 2-to-1 multiplexers and NOT gates:

$$f = \bar{w}_2 w_3 + \bar{w}_1 w_2 \bar{w}_3 + w_2 \bar{w}_3 w_4 + w_1 \bar{w}_2 \bar{w}_4$$

Note: AND, NAND, OR, NOR, XOR gates are not available.

Problem 2 (35 points)

For the logic function $f(w,x,y,z) = \prod M(1,7,12,13,14,15) \cdot d(0,2,8,10)$ (**Note:** the d represents the don't cares):


- Show the truth table. [5 points]
- Draw a completely labeled K-map. [5 points]
- Write the algebraic expression for the minimized Sum of Products (SoP) and minimized Product of Sum (PoS) implementation of this function using the K-map. **Note:** Show the circles on the K-map. [10 points]
- Write a Verilog program using structural code that implements the SoP. [5 points]

Problem 3 (35 points)

Simplify the following circuit by using Boolean Algebra properties. Assume that you have **only** 2-input and 3-input NAND gates. It is known that $\bar{x} + \bar{y} + \bar{z} = \bar{x} \cdot \bar{y} \cdot \bar{z}$. Draw the simplified circuit.

Note: NOT, AND, OR, NOR, XOR gates are not available.

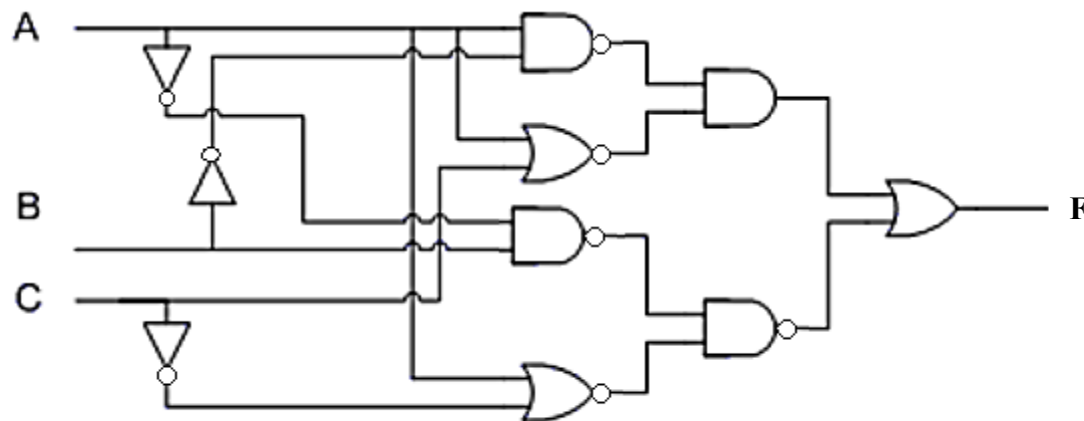Note: Simplification by K-maps will NOT be graded.



Boolean Algebra Properties

5a.	$x \cdot 0 = 0$	10a.	$x \cdot y = y \cdot x$	<i>Commutative</i>
5b.	$x + 1 = 1$	10b.	$x + y = y + x$	
6a.	$x \cdot 1 = x$	11a.	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	<i>Associative</i>
6b.	$x + 0 = x$	11b.	$x + (y + z) = (x + y) + z$	
7a.	$x \cdot x = x$	12a.	$x \cdot (y + z) = x \cdot y + x \cdot z$	<i>Distributive</i>
7b.	$x + x = x$	12b.	$x + y \cdot z = (x + y) \cdot (x + z)$	
8a.	$x \cdot \bar{x} = 0$	13a.	$x + x \cdot y = x$	<i>Absorption</i>
8b.	$x + \bar{x} = 1$	13b.	$x \cdot (x + y) = x$	
9.	$\bar{\bar{x}} = x$	14a.	$x \cdot y + x \cdot \bar{y} = x$	<i>Combining</i>
		14b.	$(x + y) \cdot (x + \bar{y}) = x$	
		15a.	$\overline{x \cdot y} = \bar{x} + \bar{y}$	<i>DeMorgan's theorem</i>
		15b.	$\overline{x + y} = \bar{x} \cdot \bar{y}$	
		16a.	$x + \bar{x} \cdot y = x + y$	
		16b.	$x \cdot (\bar{x} + y) = x \cdot y$	
		17a.	$x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$	<i>Consensus</i>
		17b.	$(x + y) \cdot (y + z) \cdot (\bar{x} + z) = (x + y) \cdot (\bar{x} + z)$	