

SANTA CLARA UNIVERSITY	ELEN 115 Spring 2023	Shoba Krishnan
Laboratory #4: Diode Basics		

PRE-LAB

- (1) **i-v** curve of a pn junction diode
 - (a) Write the equation that relates the current and voltage for a silicon diode.
 - (b) Draw a rough sketch of the i-v curve of the diode in its forward region.
- (2) Switching diodes

For the diode **1N4148**

- (a) Read its data sheet. (online or the pdf posted on Camino)
- (b) Find the maximum ratings for its
 - i. Forward turn-on voltage
 - ii. Forward current
 - iii. Reverse DC blocking voltage
 - iv. Power dissipation
- (3) LEDs: For the LED NSPW500BS
 - (a) Read its data sheet.
 - (b) From the graph determine what is the forward on-voltage for the LED.
- (4) Diode clamping circuits

Figure 2 shows how diodes are used to clamp voltage overshoots at the input of a chip.

- (a) For ideal diodes, what is the range the voltage at point X will be clamped to.
- (b) Clearly show how you arrive at your answer
- (c) When does each diode function as a clamp?

