

SANTA CLARA UNIVERSITY	ELEN 115 Spring 2023	Dr. S. Krishnan
Lab7: Applications of the MOSFET in analog systems		

I. OBJECTIVES

- To study the MOSFET as a switch in sample and hold systems
- To study a MOS inverting amplifier


II. PRE-LAB

Part 1: MOS as a Switch

The MOS transistors in Figure 1 and 2 have the below parameters.

$V_{TN} = 1\text{ V}$, $V_{TP} = -1\text{ V}$, $\lambda = 0$, $k_n' = 20\mu\text{A/V}^2$ and $k_p' = 10\mu\text{A/V}^2$.

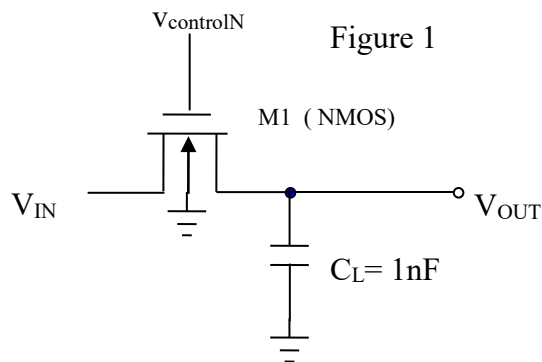All device dimensions are $500\mu\text{m}/10\mu\text{m}$



1. Figure 1 shows an NMOS transistor used as a switch.

(a) Initial voltage condition on capacitor C_L is 0V. V_{IN} is 5V.

The voltage $v_{\text{controlIN}}$ switches from 0V to 5V and stays at 5V till the capacitor settles to its final value. Find the final value of the output voltage V_{OUT}

(b) Initial voltage condition on capacitor C_L is 5V. V_{IN} is 0V.

The voltage $v_{\text{controlIN}}$ switches from 0V to 5V and stays at 5V till the capacitor settles to its final value. Find the final value of the output voltage V_{OUT}

(c) Initial voltage condition on capacitor C_L is 0V. V_{IN} is 2V.

The voltage $v_{\text{controlIN}}$ switches from 0V to 5V and stays at 5V till the capacitor settles to its final value. Find the final value of the output voltage V_{OUT}

Part 2: MOS Inverting Amplifier

- (a) For the amplifier circuit Figure 2, draw a rough voltage transfer curve (VTC) clearly marking the points where the transistor changes its mode of operation. Clearly mark the various regions of operation of the MOSFET on your VTC.
- (b) Mark the portions of the curve that help you use the device as an inverting amplifier.
- (c) Mark the portions of the curve that help you use the device as a logic inverter.
- (d) Find the values at the critical points
 - a. where the transistor changes its mode of operation
 - b. the output high voltage and output low voltage when this circuit acts as an inverter.

For the MOSFET use the following parameters:

$$V_{DD} = 2.5V, V_{to} = 0.6V, k' = 30\mu A/V^2, \lambda = 0, W/L = 100\mu m/1\mu m, R_D = 150K\Omega$$

