


## Homework 8

ELEN 21/COEN 21

Instructor: Maria Kyrarini

### Lecture 12

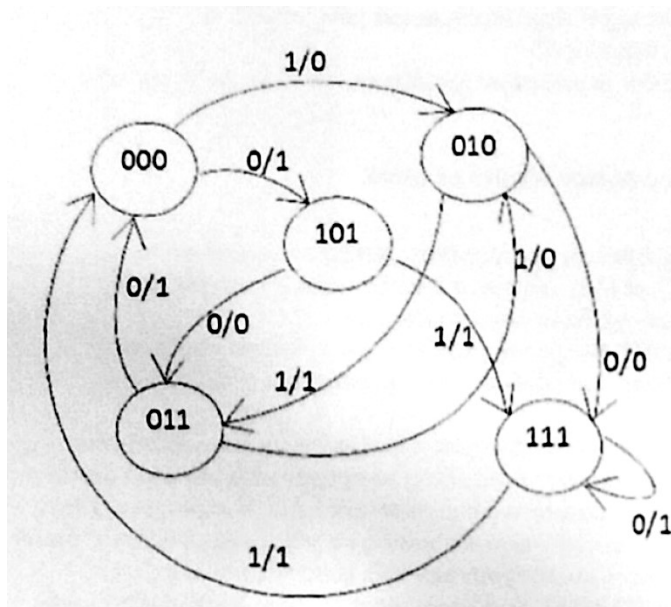1. Derive a minimal state table for a single-input and single-output Mealy-type state machine that produces an output of 1 if in the input sequence it detects either 110 or 101 patterns. Overlapping sequences should be detected.
2. The figure below shows a Mealy-type state machine. The states are presented in the form  $Q_2Q_1Q_0$ . Derive a circuit where the  $Q_2$  is a positive-edge D flip-flop, the  $Q_1$  is a positive-edge JK flip-flop, and the  $Q_0$  is a positive-edge T flip-flop.



3. Draw the state diagram for the table below that describes a state machine that has one input  $x$  and one output  $z$ .

Present State	Next State		Output (z)	
	x = 0	x = 1	x = 0	x = 1
A	A	E	1	0
B	C	F	0	0
C	B	H	0	1
D	E	F	0	0
E	D	A	0	1
F	B	F	1	1
G	D	H	0	1
H	H	G	1	0

**Lecture 13**

4. Implement the following circuit  $F(a,b,c,d) = \Sigma m(4,6,7,8,10,11,12,14,15)$  using only 2-to-4 decoders (without enable).
5. Implement a full adder by using a decoder and a network of OR-AND-NOT gates.