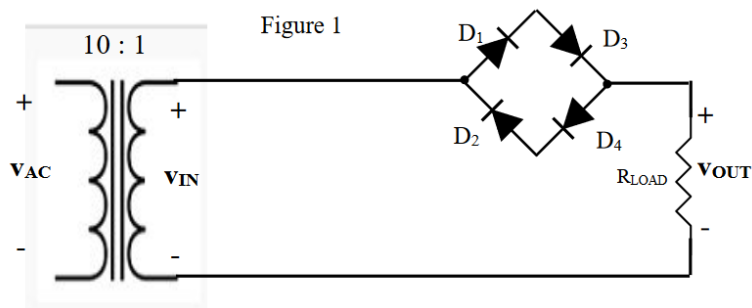


Exam 2 (Spring 2022)


1. A design engineer tries the configuration in Figure 1 for a rectifier circuit. He uses identical diodes D_1, D_2, D_3, D_4 that can be modeled with a constant voltage drop model with $V_{D0} = 0.5V$.

The sinusoidal input signal at v_{AC} is $120V_{rms}$ at $60Hz$. $R_{LOAD} = 5K\Omega$



For his design

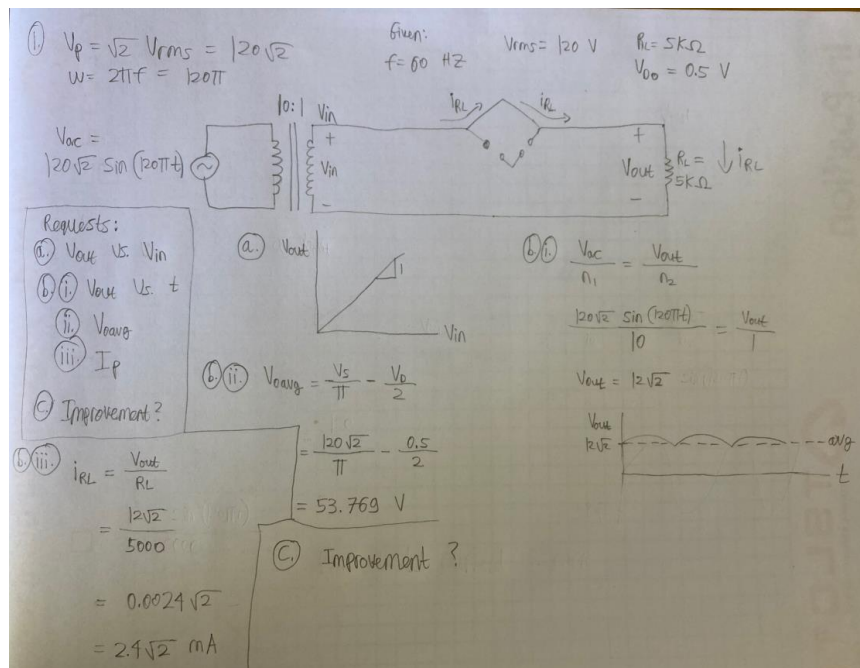- (a) Plot the v_{OUT} vs. v_{IN} for the circuit. Clearly indicate the values of all significant points and slopes of all segments. Label all axes. [20 points]
- (b) For the given input [15 points]
- (i) Draw the corresponding output voltage v_{OUT} vs. time.
 - (ii) Find the average value of the output voltage v_{OUT} .
 - (iii) Find the peak diode current in each diode.
- (c) What change can he do to his design to improve its performance. Explain your answer clearly. [5 points]




2. A designer has to build a regulator circuit as shown in Figure 2 using one of two types of diodes.

Given that **both types of diodes** have a voltage of 0.9V at 1mA current. For the diode of **TYPE A** the voltage changes by 0.1V/decade change in current while for the diode of **TYPE B** the voltage changes by 0.1V when the current through it doubles.

Do not assume the value for V_T .

The regulator needs to provide an output voltage v_{OUT} of 12V and be designed to have good performance for a load current range from no load to 8 mA.

- Which type of diode should the designer pick for building a regulator that has good performance? Clearly explain the reasons for your choice and what performance you were optimizing for. [8]
- How many diodes of the type chosen in (i) would be in the string to obtain the required v_{OUT} at nominal I_{supply} and no-load condition. [10]
- Draw the i - v curve of the diode chosen in (i). Mark the operating point at nominal supply and no load. Clearly label all axes and critical points on the graph. [8]
- What is the percentage change in the output when a 8mA load current is drawn from the regulator. [10]

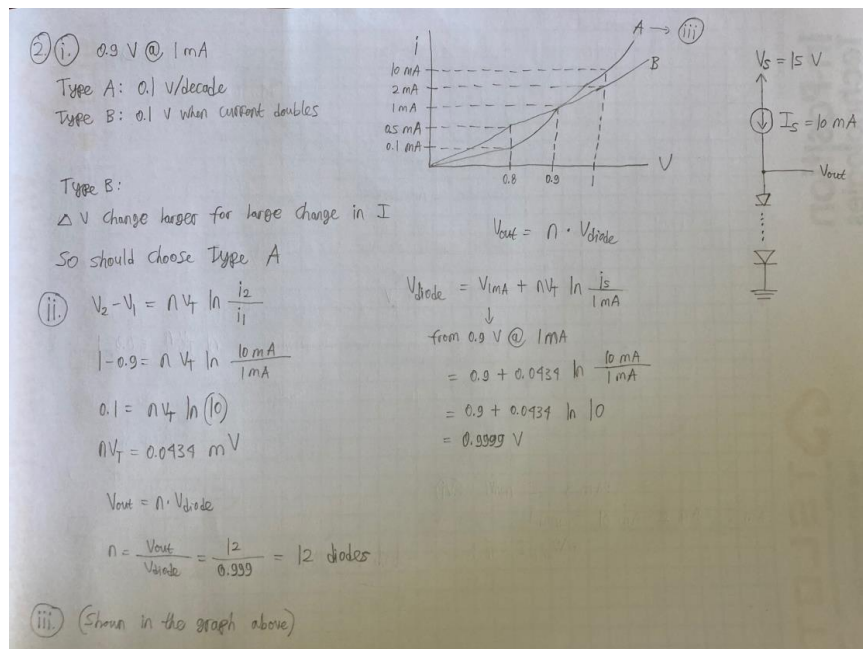

Diode Rectifiers

1. A center-tapped transformer is used to configure a rectifier as shown in Figure 1 where identical diodes D_1 , D_2 , D_3 and D_4 are used. Assume that these diodes are **ideal**. The input v_{IN} is a sinusoidal input.

For each half cycle of the input (positive half (Fig. 1(a)) and negative half (Fig. 1(b))): (i) Find and indicate the state (ON or OFF) of the diodes. (ii)


Clearly mark the current flow in the circuit and clearly indicate the direction of the current **in the diodes and load resistors** $RL1$ and $RL2$.

(iii) If the input $v_{IN} = 170 \sin 2\pi 60t$ is given to the circuit, draw the input v_{IN} and the corresponding outputs v_{OUT1} and v_{OUT2} across the loads.

(iv) What is the average value of v_{OUT1} and v_{OUT2} .

(v) What is the peak diode current in each diode

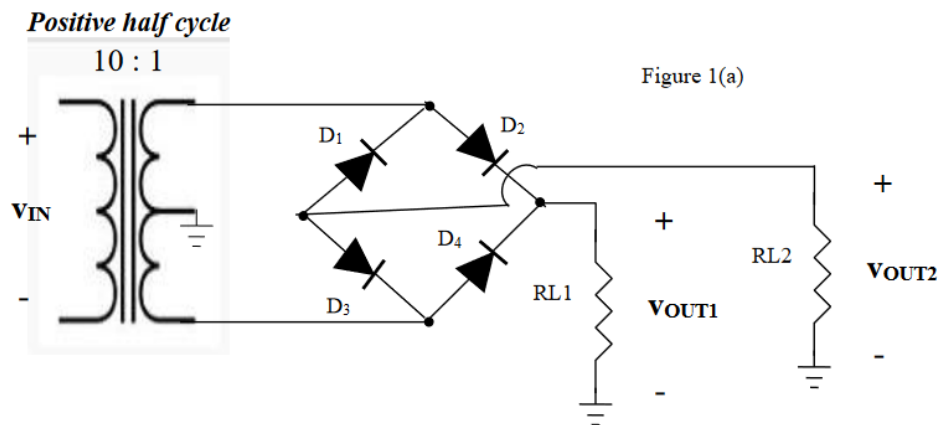(vi) what is the maximum reverse voltage seen by each diode.



Negative half cycle

10 : 1



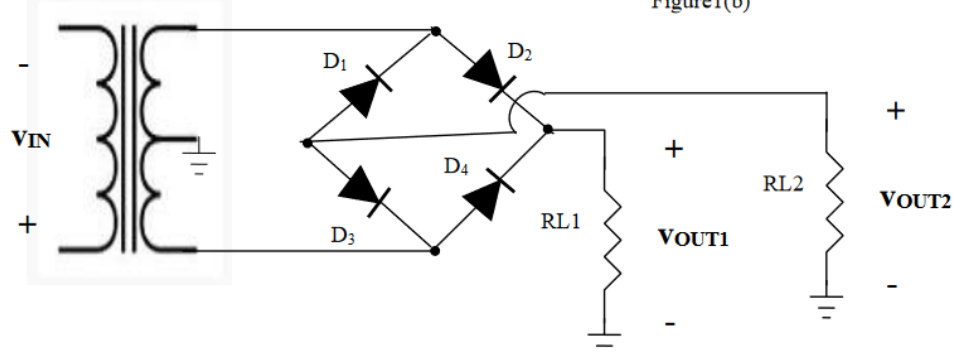


Figure1(b)

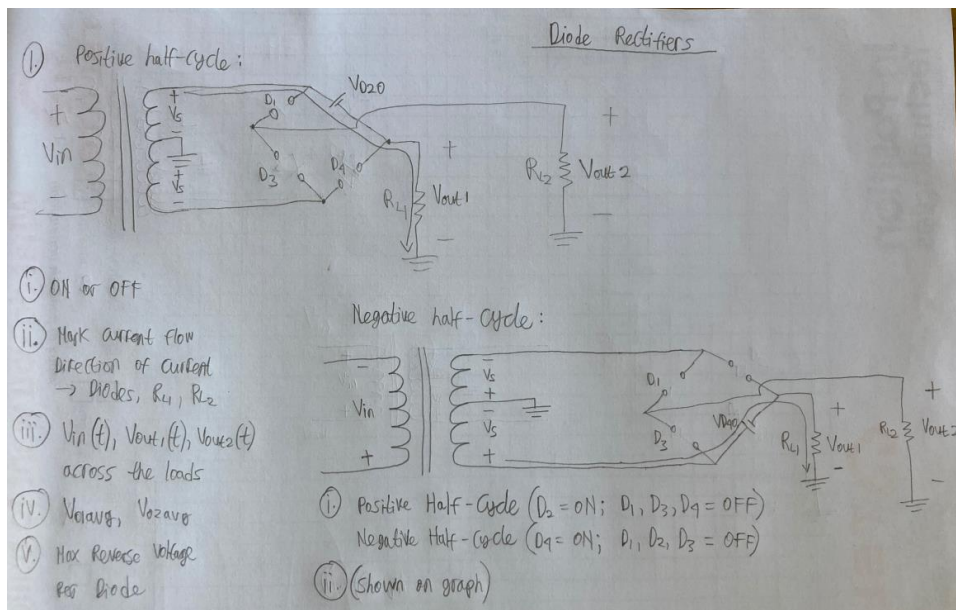

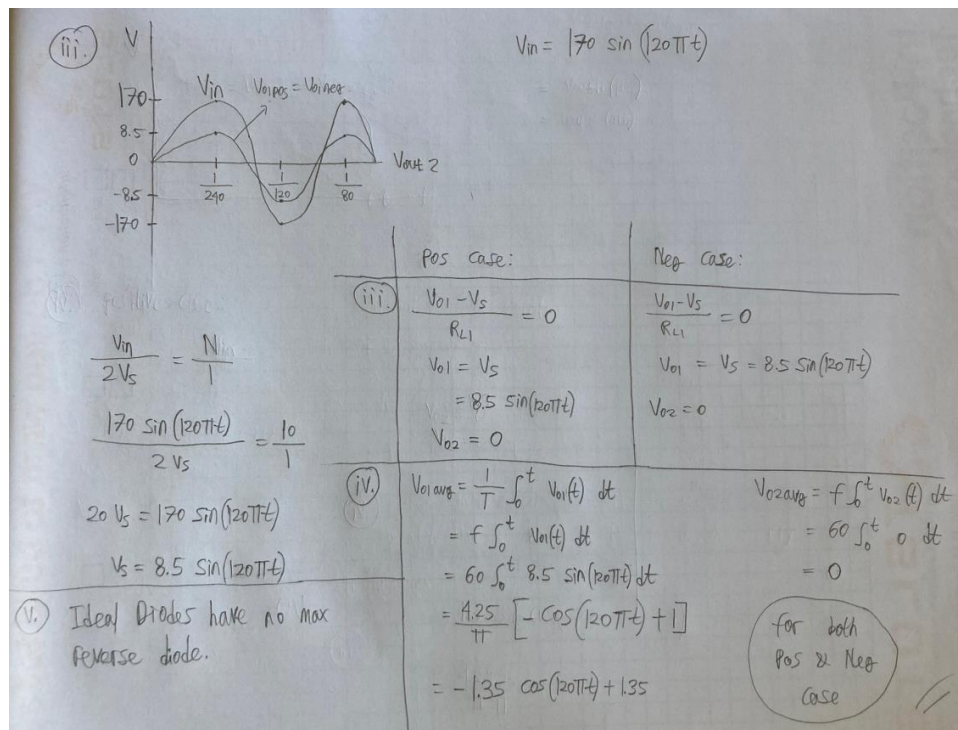



Diode Regulator

1. A voltage regulator is shown in Figure 1 A supply current of $I_{IN} = 10\text{mA}$ is provided.


The diodes D_{1a} , D_{1b} , D_{1c} , and D_{1d} have a 0.65V drop at a current of 1mA and their voltage changes by 0.1V/decade change in current.

- Draw the i-v curve for the diodes D_{1a} . Label axes and all relevant points. Clearly mark the operating points of the diodes on the graph.
- What is the output voltage V_{OUT} obtained for the designs under no load conditions? **Clearly show the steps of your work.**
- What is the load regulation ($\Delta V_{OUT}/\Delta I_L$) for a load current variation of 0mA to 4mA .

What is the percentage change in V_{OUT}

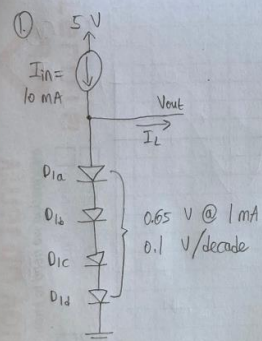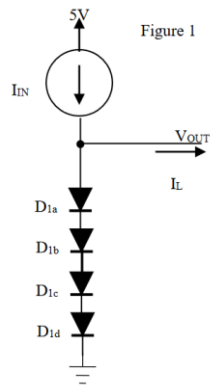

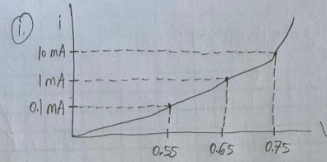- ① i-V curve for D_{1a}
② V_{out} obtained
③ $\Delta V_{out}/\Delta I_L$
for I_L variation
from $0mA$ to $4mA$
↓
Have to find
 $V_{D1(a to d)}$ @ $0mA$
 $4mA$



Diode Regulator

② $V_{D1a} = V_{D1b} = V_{D1c} = V_{D1d} = V_{D1(a to d)}$
 $V_{D1(a to d)} = 0.75$ due to $I_{IN} = 10mA$
 $V_{out} = n \cdot V_{D1(a to d)}$
 $= 4 \cdot 0.75$
 $= 3V$

③ $V_2 - V_1 = n V_T \log \left(\frac{i_2}{i_1} \right)$
 $0.75 - 0.65 = n V_T \log \left(\frac{10mA}{1mA} \right)$
 $0.1 = n V_T \cdot 1$
 $n V_T = 0.1$
 $V_{D1(a to d)} = V_{D1a} + n V_T \ln \left(\frac{4mA}{1mA} \right)$