

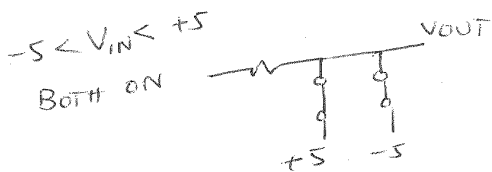
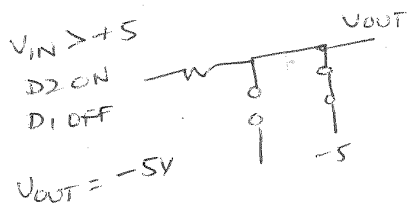
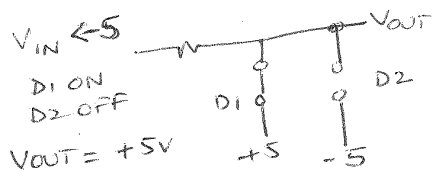
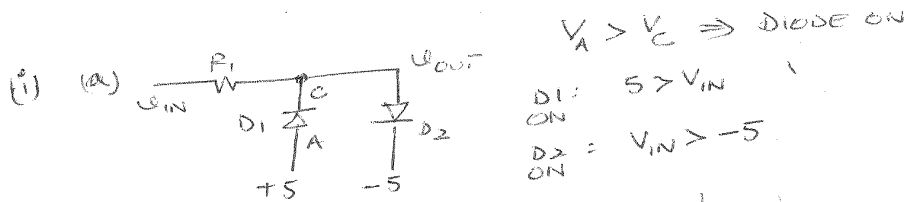
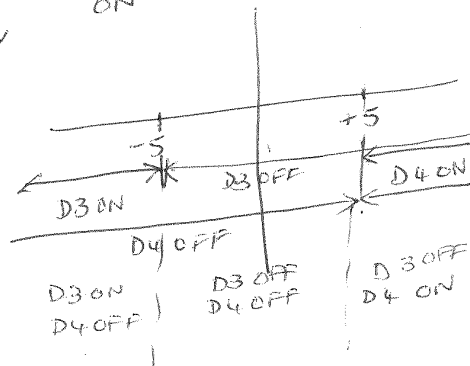
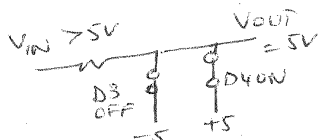
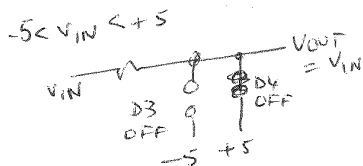
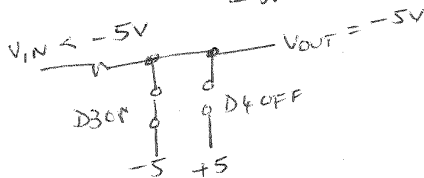


SANTA CLARA UNIVERSITY	ELEN 115 – Spring 2023	S. Krishnan
Homework #6 Solutions		

1.

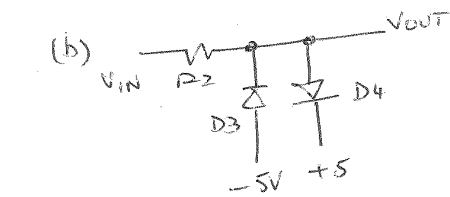


Not a good scenario.
Short $+5$ & -5

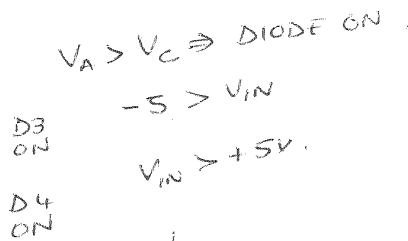

- (ii) (b) functions as a clamp -
as V_{out} stays below +5 & above -5
& ~~for the~~ in between range $V_{out} = V_{in}$.
- (iii) (a) Does NOT function as a clamp
as it shorts out the +5V & -5V for some
input conditions.

2.

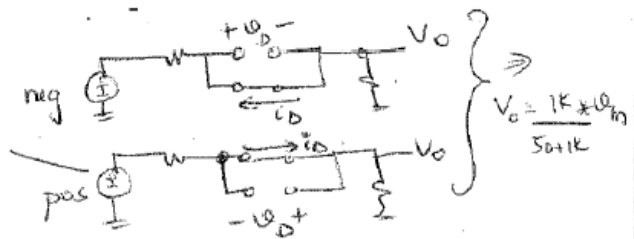- (i) $V_{in} < 0$ D_b turns on
 $V_{in} > 0$ D_a turn on




$$V_o = \frac{1K \times V_{in}}{50 + 1K}$$

(ii) $V_{out} = \frac{1000}{1050} \times V_{in} \approx V_{in}$

(iii) $V_{avg} = 0$

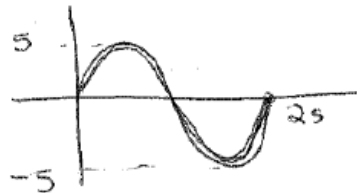
(iv) Not an efficient rectifier
as get zero average.




$$\hat{I}_{D_a} = \frac{5V}{1050} \quad \hat{I}_{D_b} = \frac{0 - (-5)}{1050} \Rightarrow \hat{I}_{D_a} = \hat{I}_{D_b} = \frac{5}{1050}$$

(v) each diode sees the other diode
shorted across its terminals \Rightarrow PIV = 0V


3. 4.74

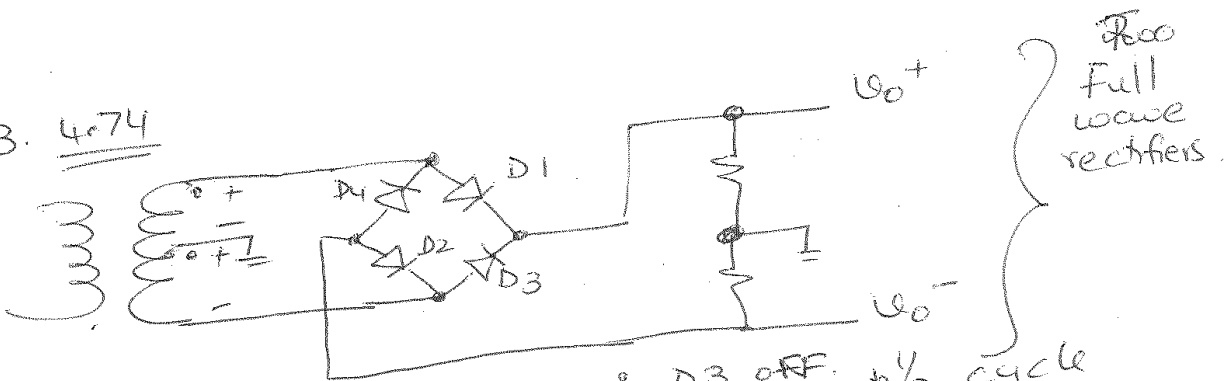

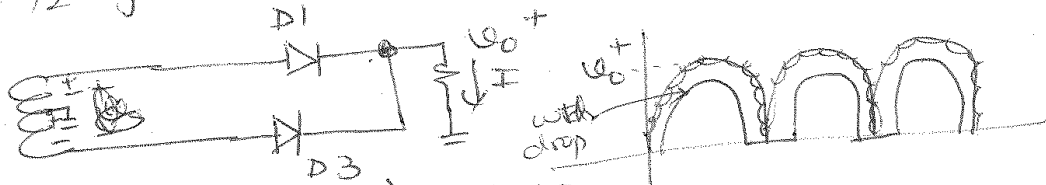positive $\frac{1}{2}$ cycle $D1$ ON & $D3$ OFF. $D1$ OFF $D3$ ON.
 negative $\frac{1}{2}$ cycle



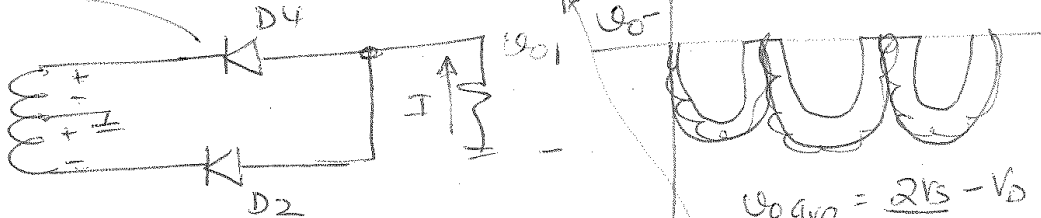PIV $V_S - V_0 = V_S + (V_S - 0.7) = 2V_S - 0.7 = 39.2V$




positive $\frac{1}{2}$ cycle $D2$ ON, $D4$ OFF
 negative $\frac{1}{2}$ cycle $D2$ OFF, $D4$ ON

$$V_{o,avg} = \frac{2V_S - V_0}{\pi}$$

$$12V = \frac{2V_S - 0.7}{\pi}$$


$$V_S = 19.95V //$$

4.

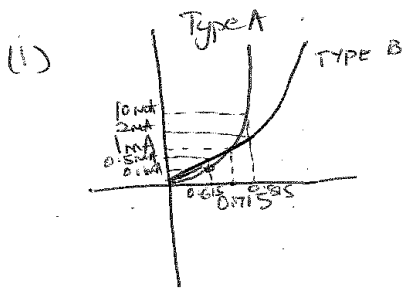

Type B
 ΔV change larger
 for large change in I .

So should
 choose Type A.

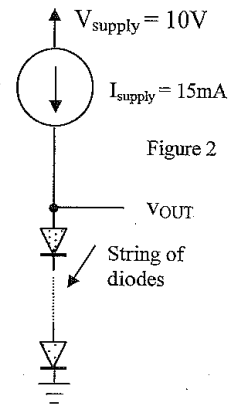

(ii) $V_2 = V_1 + nV_T \ln \frac{I_2}{I_1}$

$$0.1\text{V} = nV_T \ln \frac{10\text{mA}}{1\text{mA}}$$

$$nV_T = 0.0434\text{mV}$$

$$V_2 = 0.715 + 0.0434 \ln \frac{15\text{mA}}{1\text{mA}} = 0.8326\text{V} = V_{\text{diode}}$$

To get 5V $N \times 0.8326 = 5 \Rightarrow N = 6.005 \approx 6 \text{ diodes}$

$$V_{\text{out}} = N \times V_{\text{diode}}$$



(iii) when $I_L = 5\text{mA} \Rightarrow I_{\text{diode}} = 15\text{mA} - 5\text{mA} = 10\text{mA}$

$$\Rightarrow V_{\text{diode}} = 0.815 \text{ as seen in graph}$$

$$V_{\text{out}} = 6 \times 0.815 = 4.89\text{V}$$


$$\% \text{ change} = \frac{4.89 - 5}{5} \times 100 \approx -2.2\%$$

5.

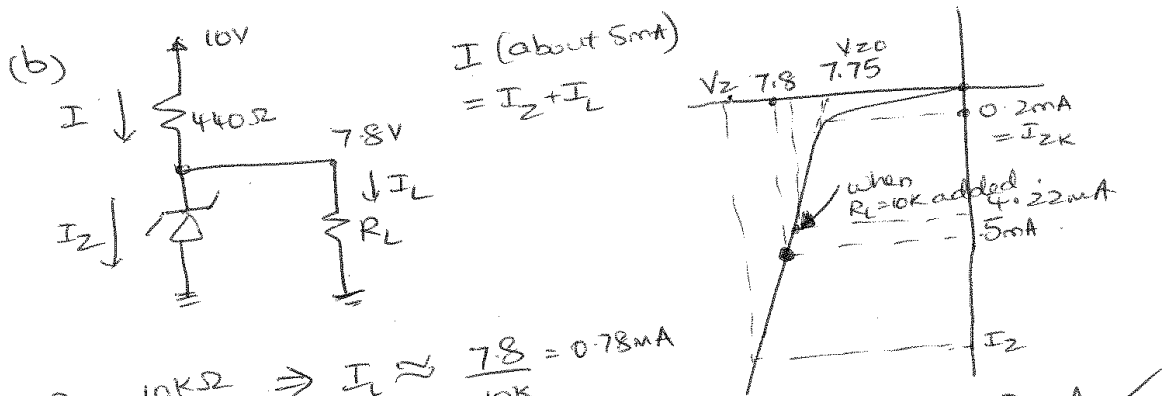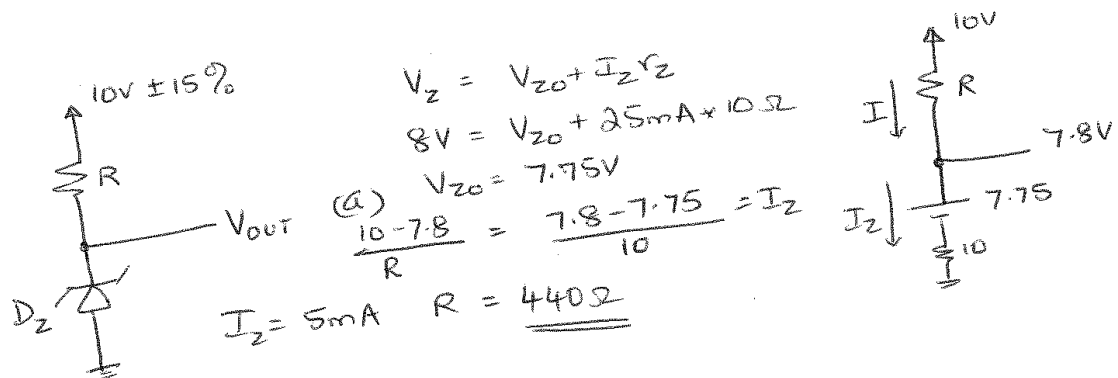

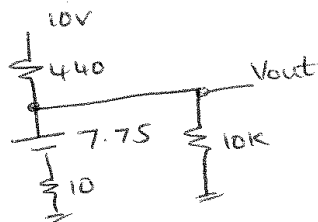(i) $R_L = 10K\Omega \Rightarrow I_L \approx \frac{7.8}{10K} = 0.78mA$

So If R_L added I_z drops $\approx 5 - 0.78$ to $4.22mA$ ✓




$\frac{10 - V_{out}}{440} = \frac{V_{out} - 7.75}{10} + \frac{V_{out}}{10K}$
 $V_{out} \approx 7.8$
sightly lesser

(ii) $R_L = 1k\Omega$

$I_L \approx \frac{7.8V}{1K} = 7.8mA$. So I_Z drops very low below I_{ZK} (2)

I from supply cannot be sufficient & keep zener biased & keep V_{out} @ 7.8V

\Rightarrow Zener turns off

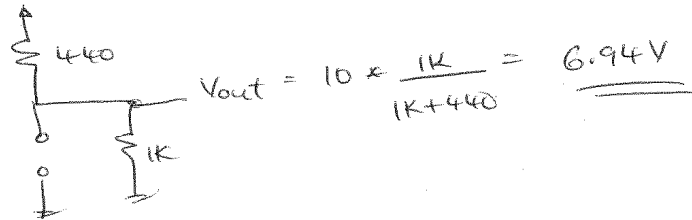

$$V_{out} = 10 \times \frac{1K}{1K + 440} = \underline{\underline{6.94V}}$$