

ELEN 115L Lab Report 1: Circuit Analysis using LTSpice

Matt Tognotti

Mulia Widjaja


5 April 2023

ELEN 115L Section Wednesday 2:15 pm

Lab objectives

- Become familiar with LTSpice
- Use LTSpice to simulate and analyze a voltage and current divider
- Construct a voltage divider and take measurements


Part 1: Schematic

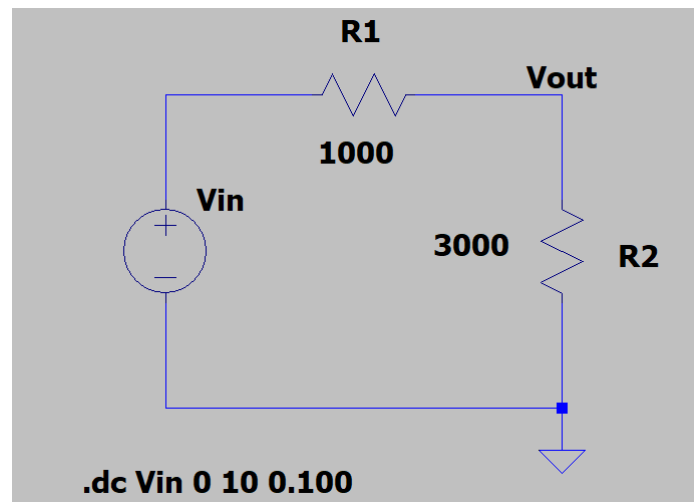

Voltage Divider

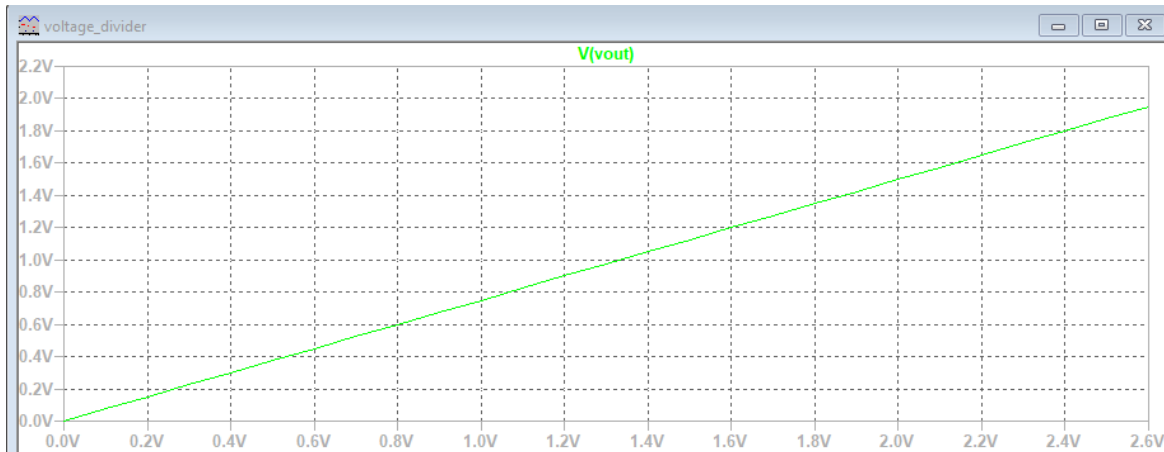
Part 2: DC Analysis

- DC Sweep simulation on V_{in} from 0V to 10V in 100mV increments shown below.
- The plot is of V_{in} on the x-axis and V_{out} on the y-axis




V_{in} vs V_{out} for voltage divider

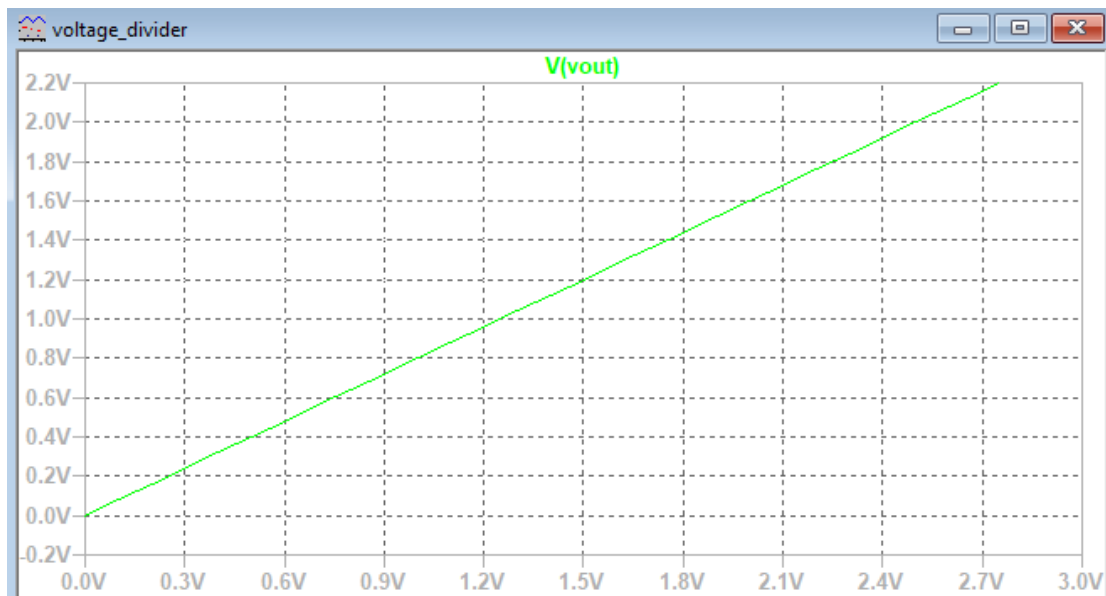- $V_{out} = (R_2/(R_1+R_2)) * V_{in}$ is the equation for the voltage across resistor 2.
- Therefore the slope is $(R_2/(R_1+R_2)) = 3000/4000 = 0.75$
- This is a linear relationship as expected
- Now changing R_2 to 4000 ohms the slope will slightly increase to $(R_2/(R_1+R_2)) = 4000/5000 = 0.8$, using the voltage divider equation. The plot is shown below.



V_{in} vs V_{out} for voltage divider with R_2 increased

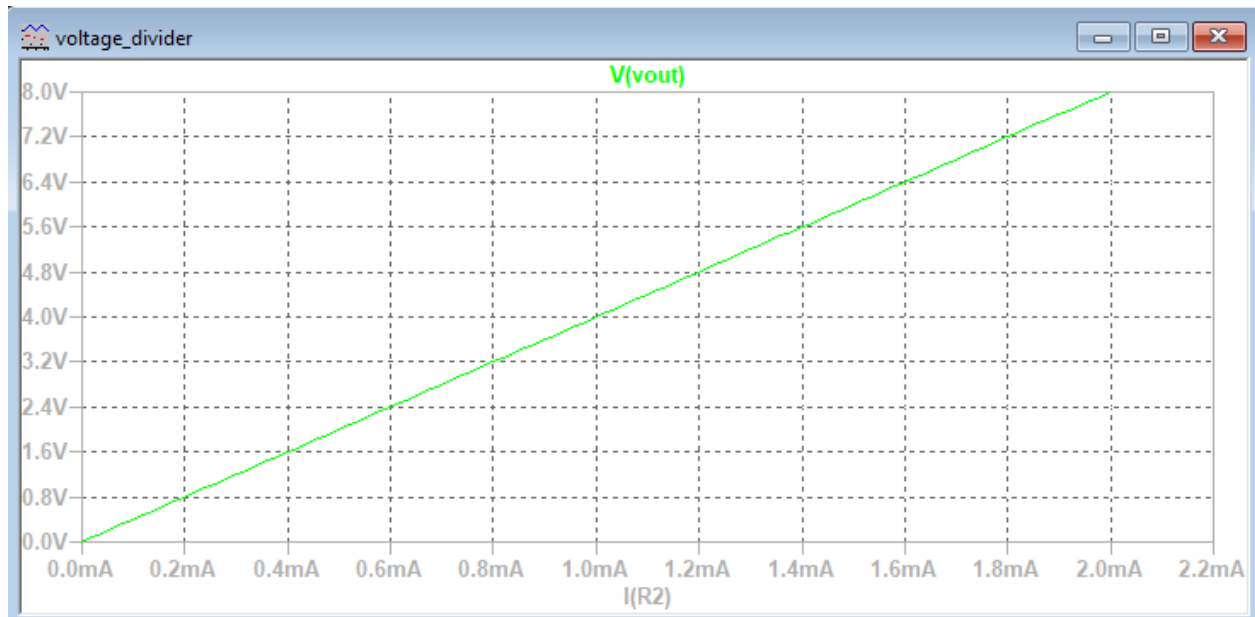- Now plotting V_{out} vs I_{out} for the same voltage divider




V_{out} vs I_{out} for Voltage divider

- This plot makes sense because as the voltage increases as the current increases ($V=IR$)

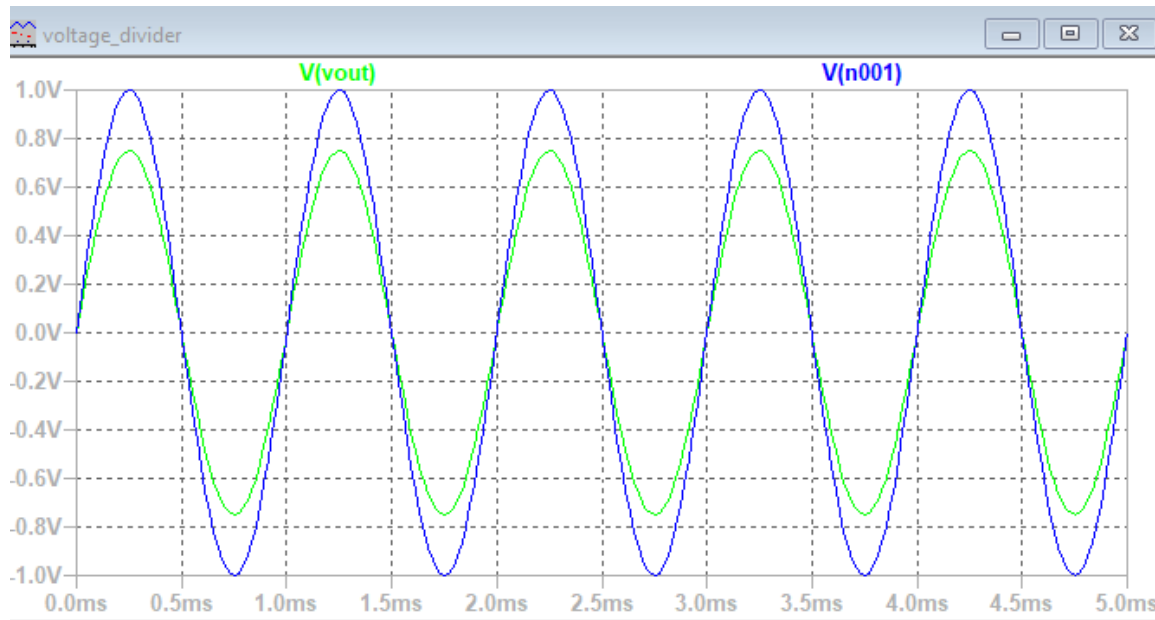Part 3: Transient Analysis


- Now we plot V_{out} and V_{in} as a function of time for a sinusoidal source with the same voltage divider with $R1 = 1k\ \Omega$ and $R2 = 3k\ \Omega$
- We use a sinusoidal source with 1V amplitude and 1kHz frequency
- We run a transient analysis for 5ms, using 10us time steps
- Below, we plot V_{in} and V_{out} as a function of time



V_{in} and V_{out} as a function of time for voltage divider


- The result looks as expected, since the voltage amplitude is smaller due to the voltage divider (voltage was reduced).
- The voltage at the two nodes have the same frequency, as expected. However, their voltage amplitudes are different.

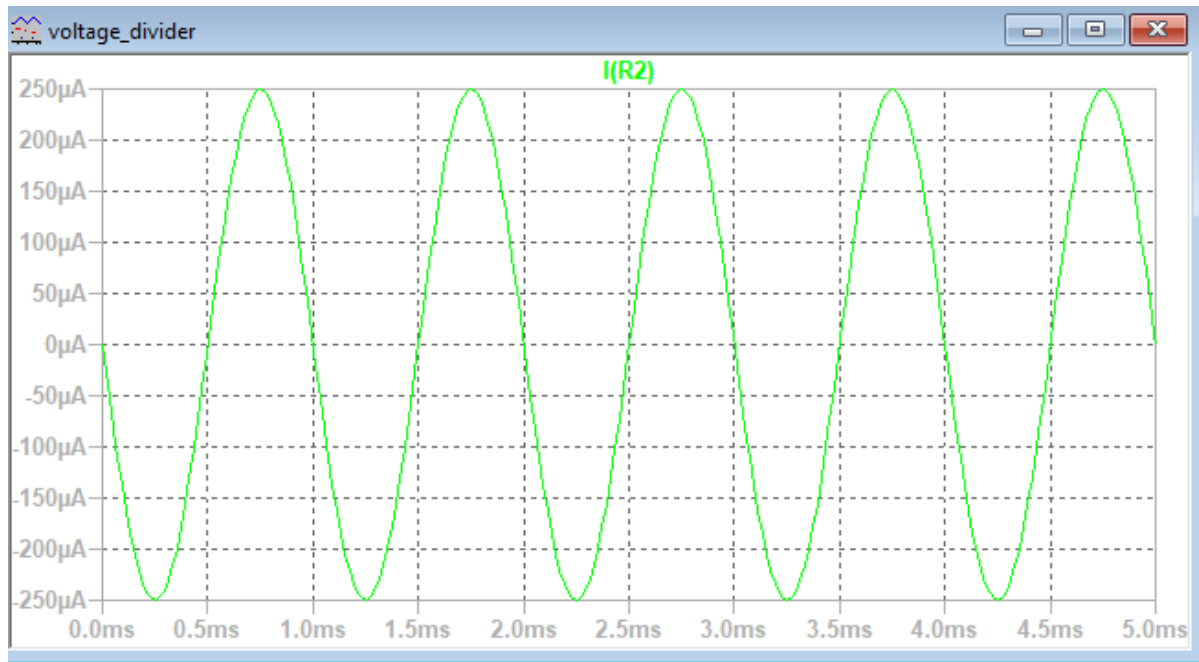- Now we plot the current i_{out} as a function of time as shown below for the same circuit (voltage divider)



i_{out} as a function of time for voltage divider

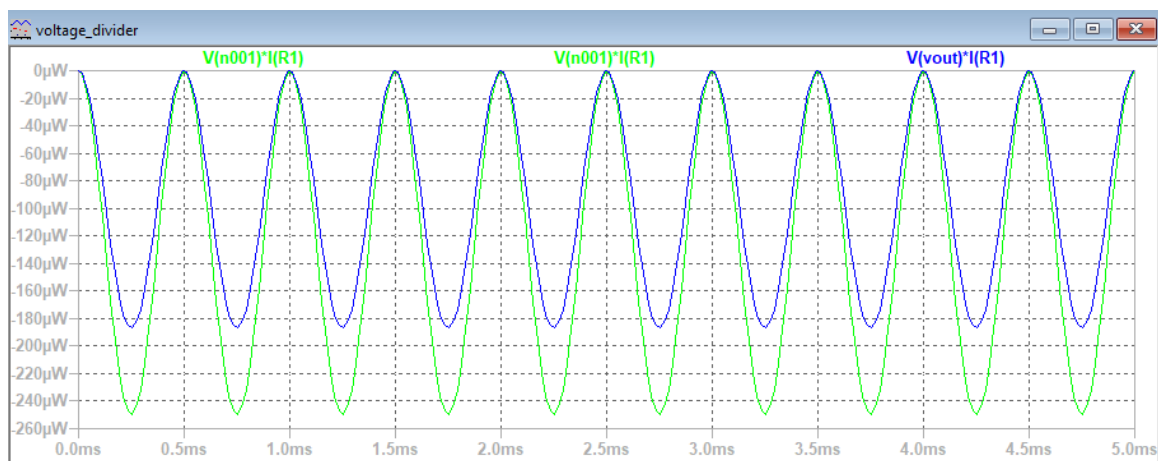
- The plot shows the current changing direction as expected for a sinusoidal source.
- Now we plot the power delivered by V_{in} and power delivered to $R2$ as a function of time



Power delivered by V_{in} and Power delivered to $R2$ as a function of time for the voltage divider


Now we change R2 to 4000 ohms

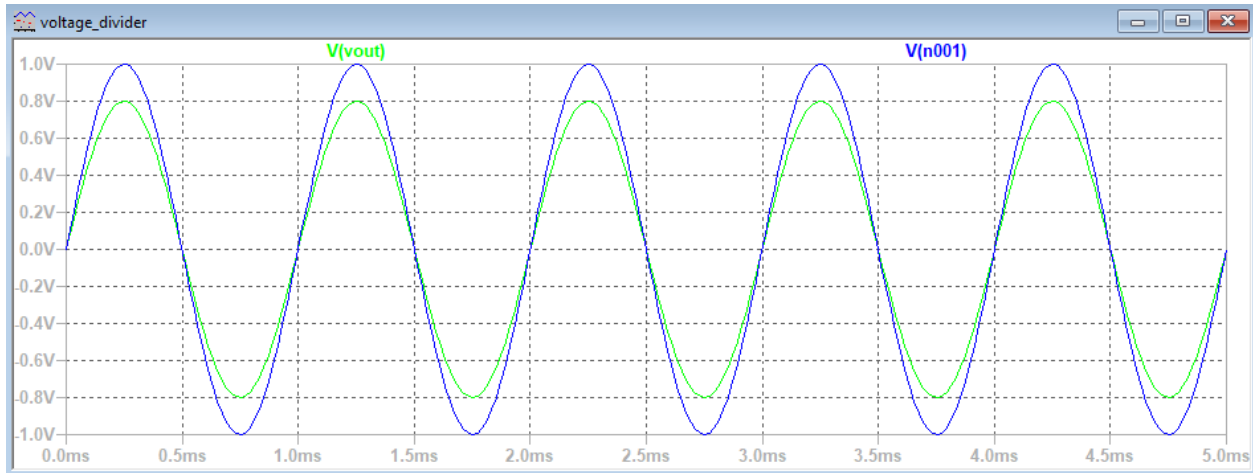- We plot V_{in} and V_{out} as a function of time with the new R2 value of 4000 ohms




V_{in} and V_{out} as a function of time for voltage divider

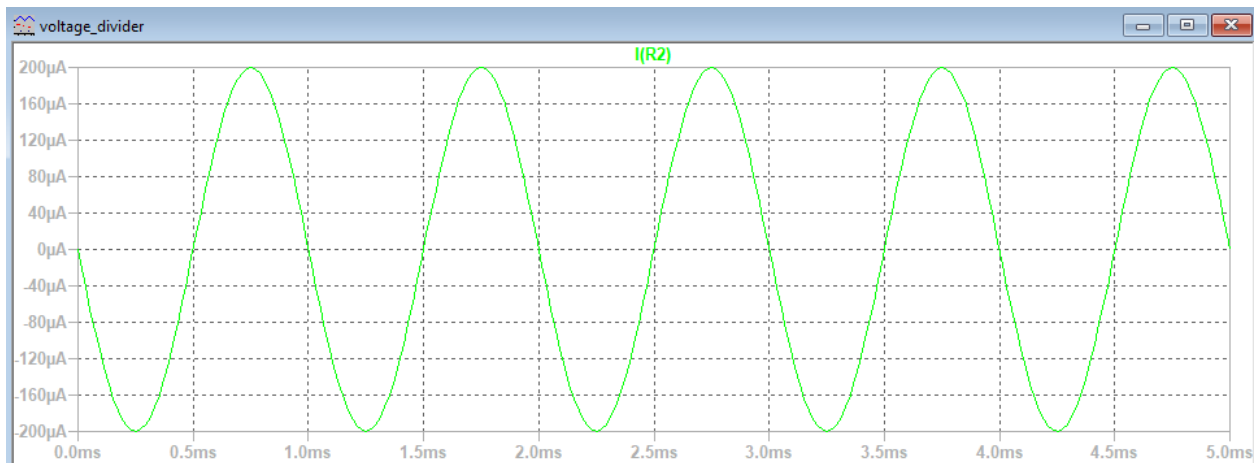- Next, we plot I_{out} as a function of time shown below with the new R2



I_{out} as a function of time for the voltage divider

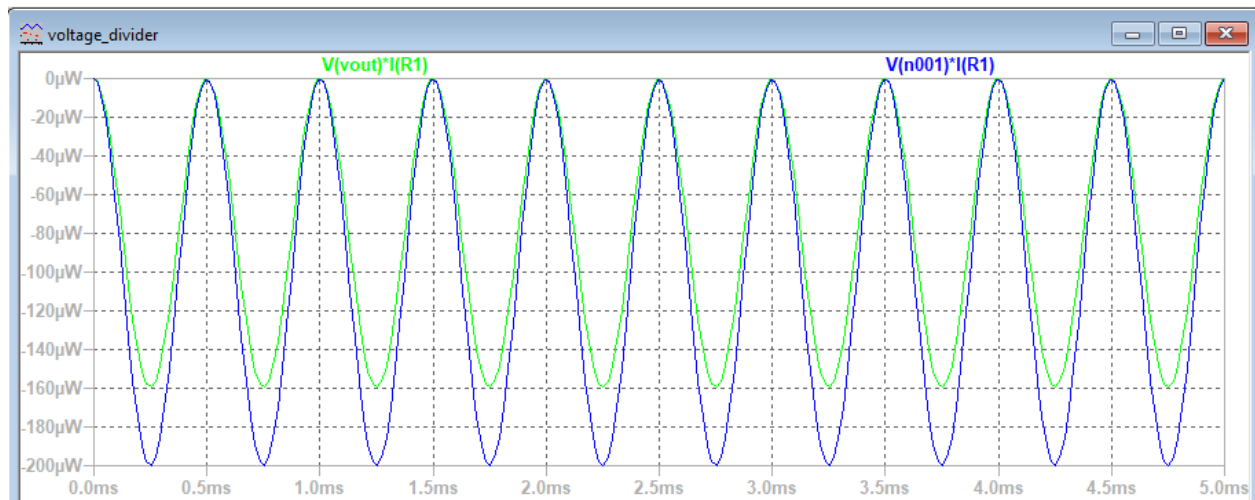- Next, we plot the power delivered by V_{in} and power delivered, with now $R_2 = 4000$ ohms, as a function of time.




Power delivered by V_{in} and Power delivered to R_2 as a function of time for the voltage divider

How did the waveforms change after R_2 was increased?

- The output voltage increased when we changed R_2 to 4000 ohms, as expected per the voltage divider equation
- Additionally, the output current through R_2 decreased to a peak-to-peak of 200 μA (250 μA before with 3000 ohms resistor), which checks out with ohms law.
- The power delivered to R_2 was decreased when we increased the resistor to 4000 ohms.

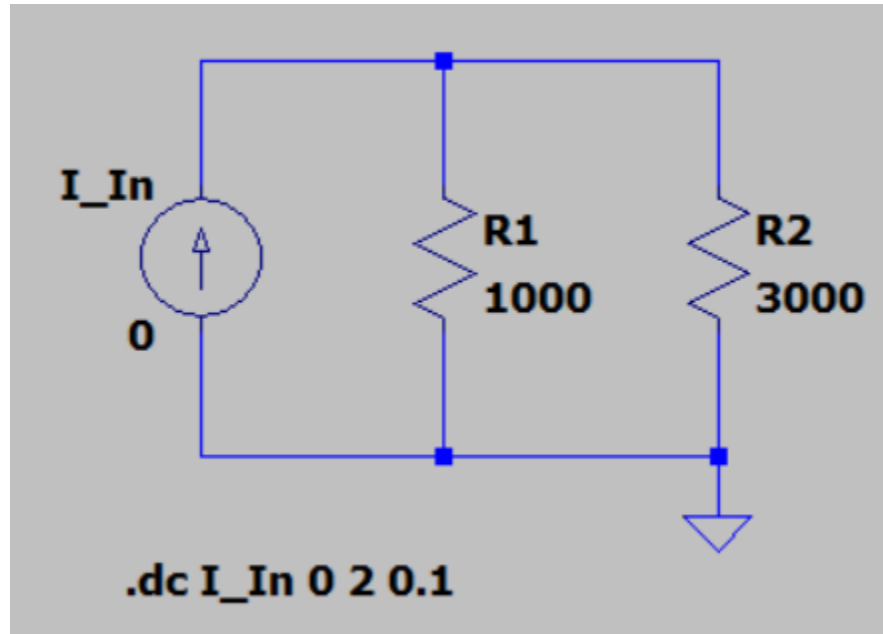
Part 4: Parallel Circuit

- Now we build a current divider as shown below



Current divider

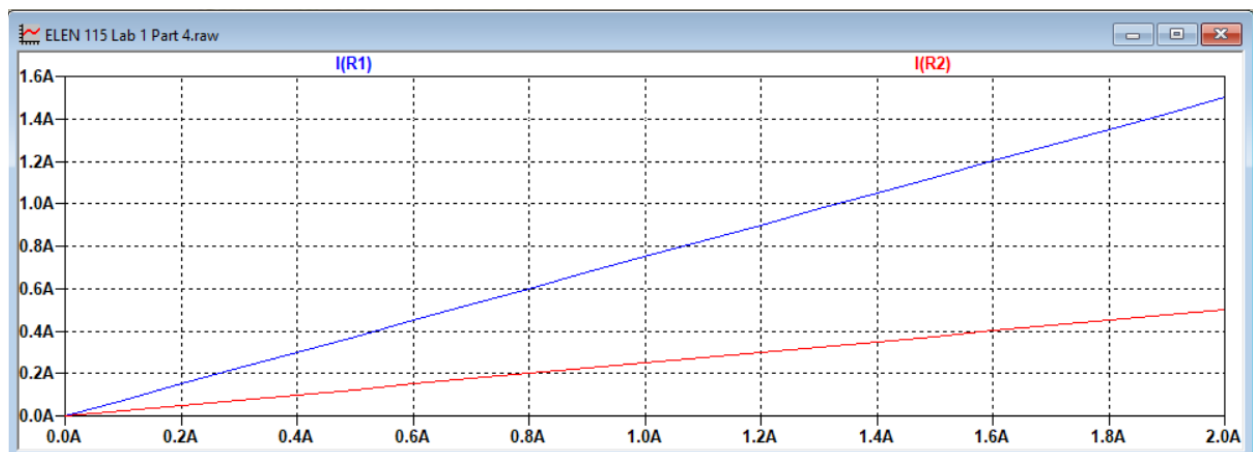- We run a DC sweep simulation on lin from 0A to 2A in 100mA increments.
- We plot IR1 and IR2 with lin on the x-axis as shown below




IR1 and IR2 with lin on the x-axis for current divider

Using the current divider equations:

- The slope for IR1 is $R_2/(R_1+R_2) = \frac{3}{4} = 0.75$

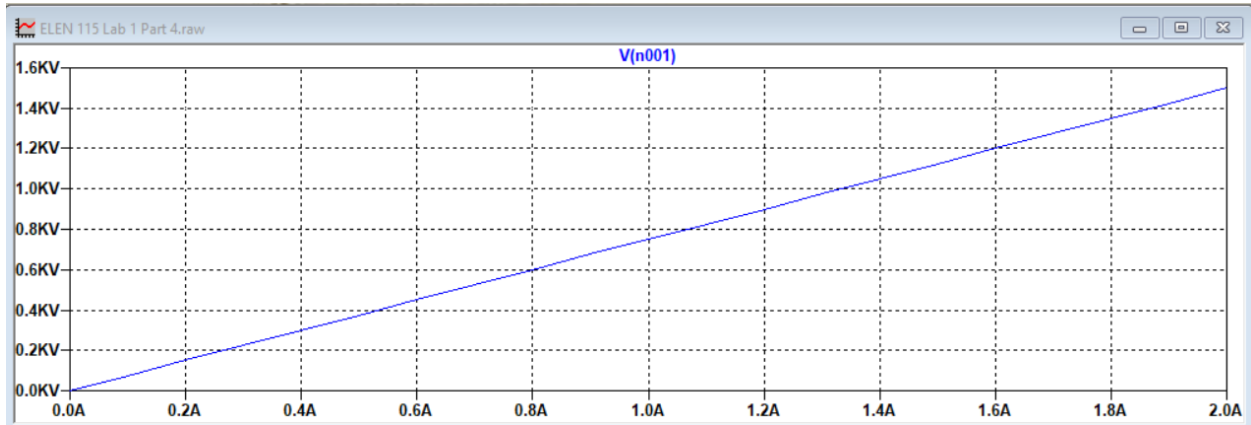- The slope for I_{R2} is $R_1/(R_1+R_2) = 1/4 = 0.2$
- Now we plot V_{out}
- $V_{out} = I * (R_1 \parallel R_2)$ therefore the slope is $(R_1 \parallel R_2) = 750$



Vout vs Iout for current divider

- This represents the voltage and current direct proportionality. As the current increases the voltage increases ($V = IR$).


Part 5: Circuit Build

Now we build the voltage divider from part 1


Vin (V)	Vout (V)
2	1.507
4	3.015
6	4.522
8	6.031
10	7.538

The slope is about 0.75 just like the simulation.

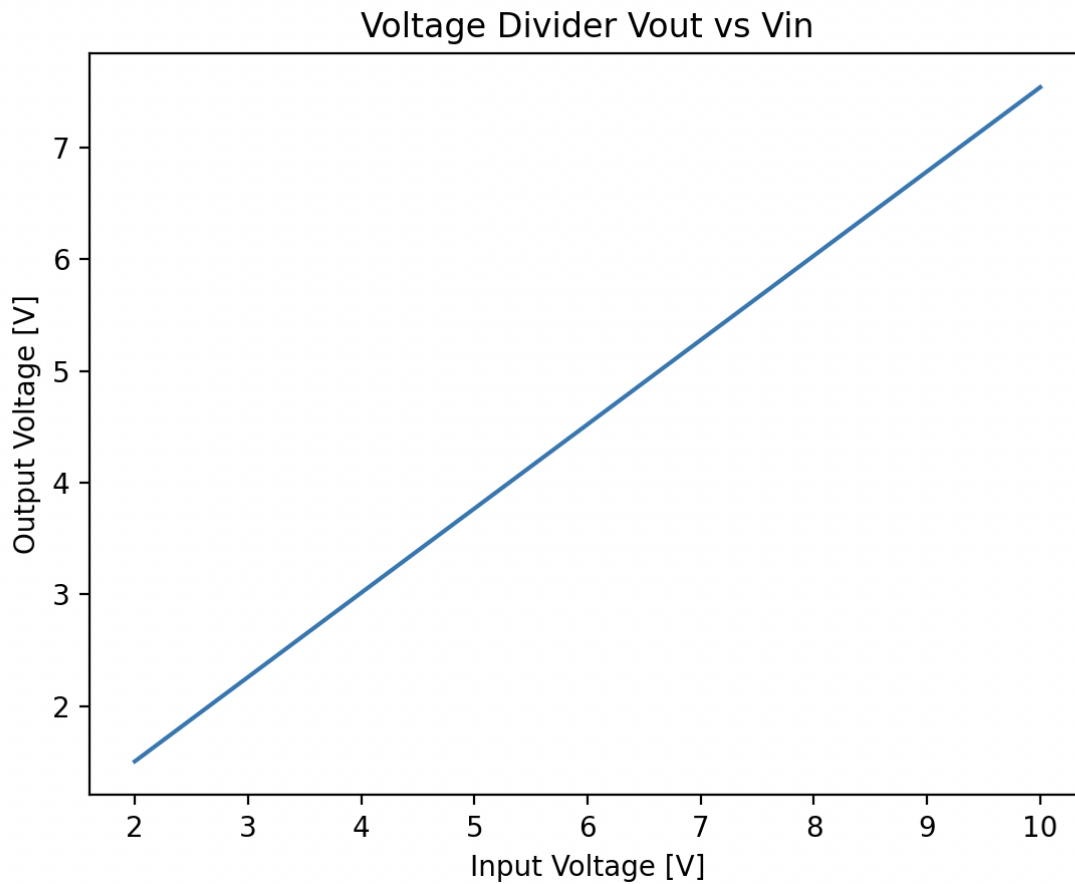We plot the data from the circuit build below.



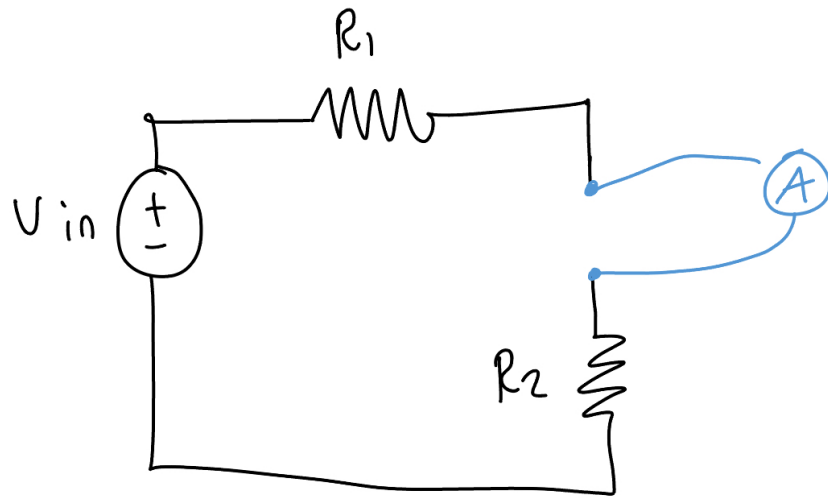- We place the ammeter in series with the resistor R_2 to measure the current through R_2 .




Measuring the current through R_2


Part 6 Lab Extension

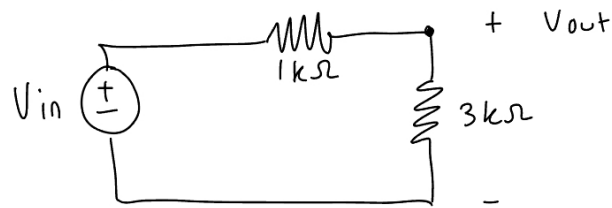1.

Adding a resistor in Parallel to Voltage divider



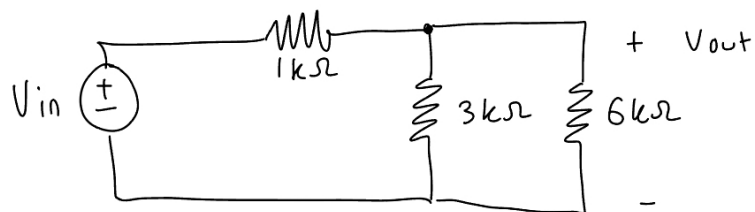
$$V_{out} = V_{in} \times \frac{3k}{1k+3k} = \frac{3}{4} V_{in} = \boxed{0.75 V_{in}}$$



$$6k \parallel 3k = 2k\Omega$$
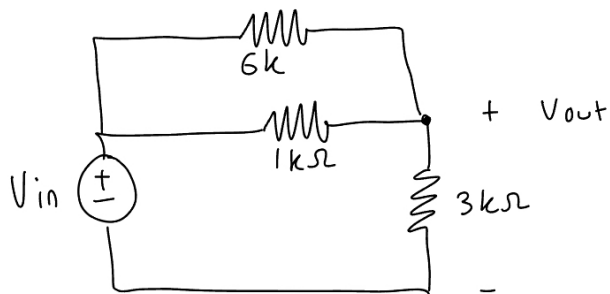
$$V_{out} = V_{in} \frac{2k}{2k+1k} = \frac{2}{3} V_{in} = \boxed{0.66 V_{in}}$$




$$6k \parallel 1k = 857\Omega$$

$$V_{out} = \frac{3k}{3k+857} V_{in} = \boxed{0.77 V_{in}}$$

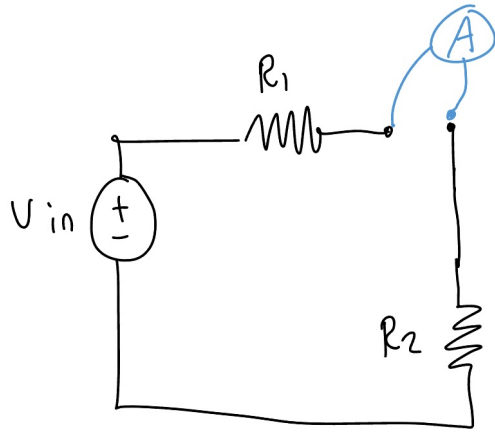2.

To measure current through R_1
add ammeter in series



Conclusion

We became more familiar with constructing and analyzing circuits in LTSpice. We collected data from a current divider and a voltage divider. For the voltage divider, we built the circuit physically and compared our results. They were very similar.