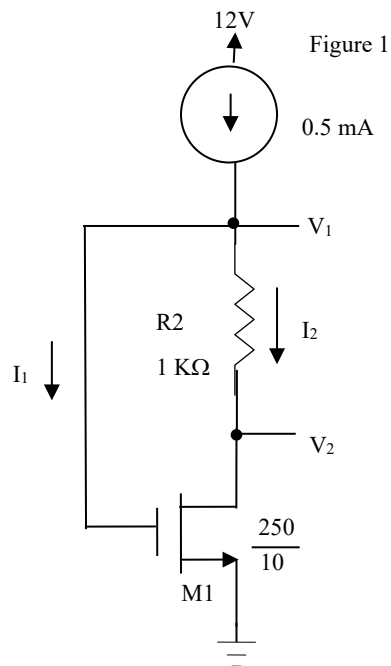


SANTA CLARA UNIVERSITY	ELEN 115 – Spring 2023	S. Krishnan
<b>Homework #8</b>		

- Assume the MOS transistor in Figure 1 has  $V_{TN} = 2\text{ V}$ ,  $V_{TP} = -2\text{ V}$ ,  $\lambda = 0$ .  
Given  $k_n' = 40\mu\text{A/V}^2$  and  $k_p' = 20\mu\text{A/V}^2$ . All device dimensions are in  $\mu\text{m}$   
Find the value of labeled currents and voltages. [10]  
What is the region of operation of the transistor? [10]  
Clearly show how you arrive at your answer.  
If the value of the resistor is halved will it change the mode of operation of M1 ? [5]  
If the value of the resistor is doubled will it change the mode of operation of M1 ? [5]



2. The DC biasing circuit in Figure 2 has MOS transistors with  
 $V_{TN} = 1.3 \text{ V}$ ,  $V_{TP} = -1.5 \text{ V}$ ,  $\lambda = 0$ ,  $k_n' = 25\mu\text{A/V}^2$  and  $k_p' = 15\mu\text{A/V}^2$ .  
 All device dimensions are in  $\mu\text{m}$ .

- (a) Find the value of the DC voltages  $V_1$ ,  $V_2$ , and  $V_3$  [20]  
 Find the value of the DC currents  $I_1$ ,  $I_2$ ,  $I_3$  and  $I_4$  [20]  
 Clearly identify DC biasing topologies in this circuit [10]  
 Justify any assumptions you make. [10]  
*Clearly show how you arrive at your answers.*
- (b) Determine the region of operation of M8? Explain how you arrive at your answer. Clearly show your work. [10]

