

5. A sequential circuit with two D Flip-Flops, A and B; two inputs, x and y; and one output, z, is specified by the following next-state and output equations:

$$A(t + 1) = \overline{x(t)} \cdot y(t) + x(t) \cdot A(t)$$

$$B(t + 1) = \overline{x(t)} \cdot B(t) + x(t) \cdot A(t)$$

$$z(t) = B(t)$$

- i) Draw the logic diagram of the circuit.
- ii) List the truth table for the sequential circuit.