

# Lab 8

Operation Amplifier

ELEN 50 Lab: Electric Circuits I

Course Number: 51310

Section: Monday 2:15 pm

Fall 2022

Submitted

At



By:

Cole Heider, Mulia Widjaja

11/14/2022

**Table 2 - Resistance Values**

	Ri	Rf1	Rs	Rf2	
Nom Values	2.7	5.6	1.2	3.8	kOhm
Meas Values	2.692	5.586	1.195	3.830	kOhm

**Table 3 - Gain of Operational Amplifier Circuits**

	Expected Gain	Measured Gain	% Error
Inverting OpAmp	-2.075	-2.066	0.43%
Non-Inverting OpAmp	4.2050	4.181	0.57%

**Table 4 - Voltage Amplitude**

Rdec (Ohm)	Vg (V)	Vout (mV)	Vout with voltage follower (V)
5000	1.05	0.84	0.99
3000	1.05	0.75	0.99
1000	1.05	0.49	0.94
800	1.05	0.43	0.93
400	1.05	0.29	0.88
200	1.05	0.19	0.83
100	1.05	0.14	0.81
50	1.05	0.60	0.80

Without the voltage follower, the Vout is being affected with the Rdec so that the voltage decreases. The voltage follower aids in maintaining the voltage in order to prevent it from dropping more than without the voltage follower.

**Table 5 - Resistance Values**

	R1	R2	R3	R4	
Nom Values	1.2	2.2	2.7	3.8	kOhm

Meas Values	1.192	2.1912	2.694	3.826	kOhm
-------------	-------	--------	-------	-------	------

**Table 6 - Voltages of Operation Amplifier Circuit**

	Theoretical (V)	Measured (V)	Percent Error
Va	1	1	0.00%
Vo1	1.704	1.694	0.59%
Vb	1	1	0.00%
Vo	0.617	0.620	-0.49%

There are practically no discrepancies, since the percent error all are showing insignificant percent errors.