

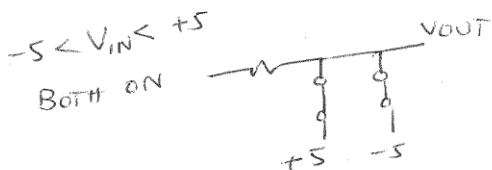
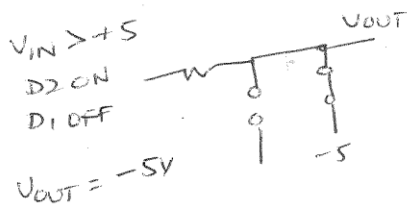
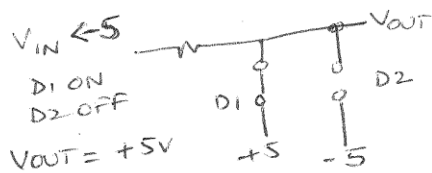
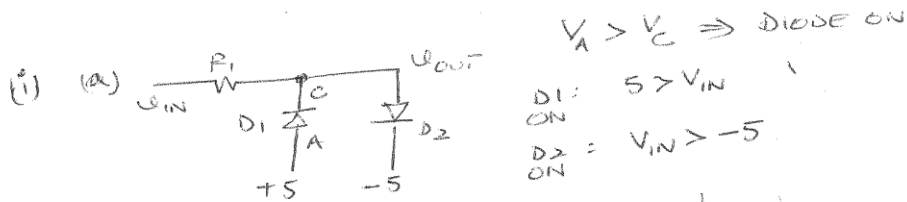
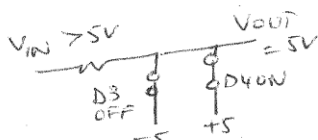
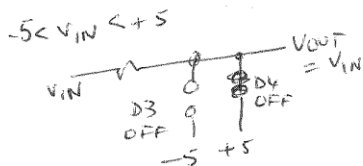


SANTA CLARA UNIVERSITY	ELEN 115 – Spring 2023	S. Krishnan
Homework #6 Solutions		


1.

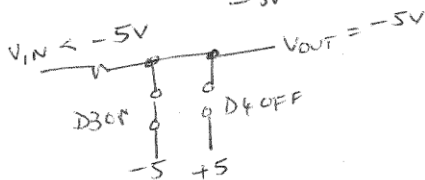

Not a good scenario.
Short +5 & -5

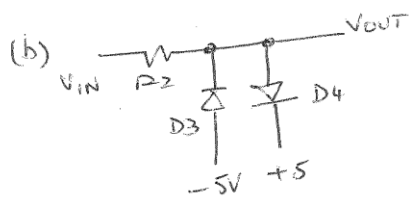

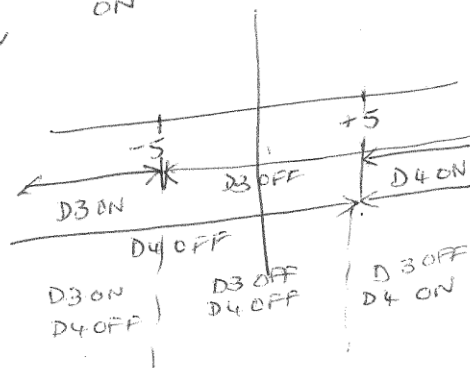
$V_A > V_C \Rightarrow$ DIODE ON
 $-5 > V_{IN}$
 $D3$ ON
 $V_{IN} > +5V$
 $D4$ ON



- (ii) (b) functions as a clamp.
as V_{out} stays below +5 & above -5
if the ~~in~~ between range $V_{out} = V_{in}$.
- (iii) (a) Does NOT function as a clamp
as it shorts out the +5V & -5V for some
input conditions.

2.

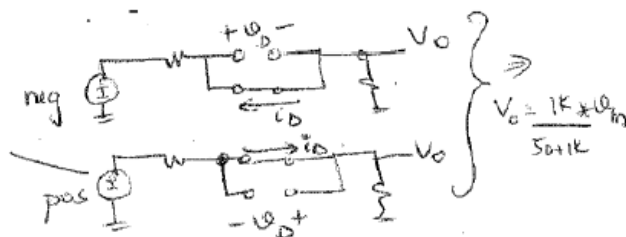
- (i) $V_{in} < 0$ D_b turns on
 $V_{in} > 0$ D_a turn on



(ii) $V_{out} = \frac{1000}{1050} \times V_{in} \approx V_{in}$

(iii) $V_{avg} = 0$

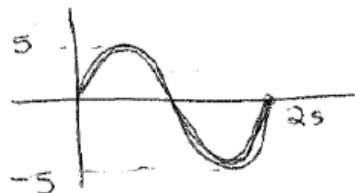
(iv) Not an efficient rectifier
as get zero average.




$\hat{I}_{D_a} = \frac{5V}{1050}$ $\hat{I}_{D_b} = \frac{0 - (-5)}{1050} \Rightarrow \hat{I}_{D_a} = \hat{I}_{D_b} = \frac{5}{1050}$

(v) each diode sees the other diode
shorted across its terminals \Rightarrow PIV = 0V


3. 4r74

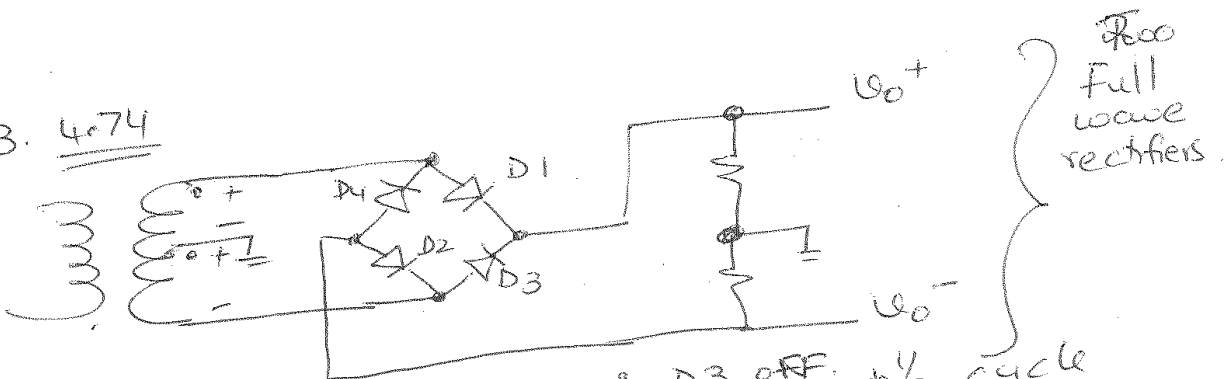

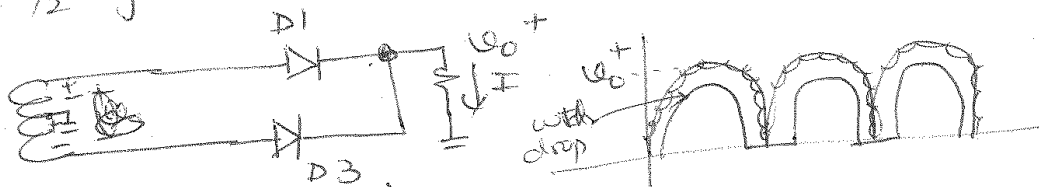positive $\frac{1}{2}$ cycle $D1$ ON & $D3$ OFF. $D1$ OFF $D3$ ON.
 negative $\frac{1}{2}$ cycle



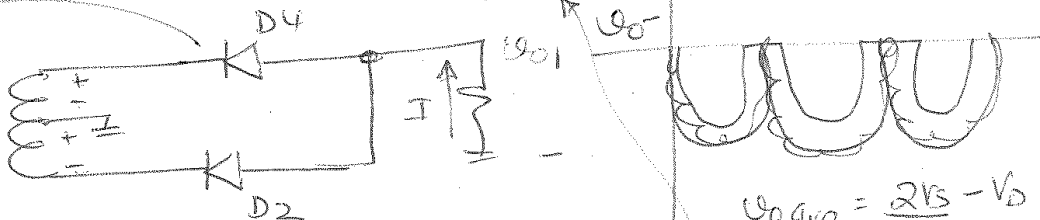PIV $V_S - V_0 = V_S + (V_S - 0.7) = 2V_S - 0.7 = 39.2V$




positive $\frac{1}{2}$ cycle $D2$ ON, $D4$ OFF
 negative $\frac{1}{2}$ cycle $D2$ OFF, $D4$ ON

$$V_{o,avg} = \frac{2V_S - V_0}{\pi}$$

$$12V = \frac{2V_S - 0.7}{\pi}$$


$$V_S = 19.95V //$$

4.

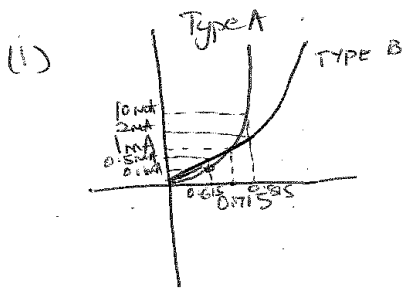

Type B
 ΔV change larger
 for large change in I.

So should
 choose Type A.

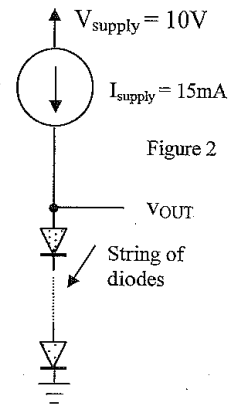

(ii)
$$V_2 = V_1 + nV_T \ln \frac{I_2}{I_1}$$

$$0.1V = nV_T \ln \frac{10mA}{1mA}$$

$$nV_T = 0.0434mV$$

$$V_2 = 0.715 + 0.0434 \ln \frac{15mA}{1mA} = 0.8326V = V_{diode}$$

To get 5V $N \times 0.8326 = 5 \Rightarrow N = 6.005 \approx 6 \text{ diodes}$

$$V_{out} = N \times V_{diode}$$

(iii) when $I_L = 5mA \Rightarrow I_{diode} = 15mA - 5mA = 10mA$

$$\Rightarrow V_{diode} = 0.815 \text{ as seen in graph}$$

$$V_{out} = 6 \times 0.815 = 4.89V$$

$$\% \text{ change} = \frac{4.89 - 5}{5} \times 100 \approx \underline{\underline{-2.2\%}}$$