

**Group Number:**

Group 9: Shiyu Ye

**NAMES (FIRST AND LAST NAME):**

Mulia Widjaja (Noble)

Venus Li

### **In-Class Assignment 3**

ELEN 21/COEN 21 – Fall 2022

Instructor: Maria Kyrarini

Date: 11/15/2022

Time: 1 hour and 30 minutes

Number of pages: 3

**Important Notes:**

- Be sure to read all the problems carefully and answer all questions.
- Be sure to answer all parts of each question.
- **Submit only one answer for each question.**
- Multiple solutions for one question will not be graded.
- **Clearly show all the steps of your work.**
- **Answers without explanation will not be graded.**
- The Engineering School Honor Code applies.

$$26 + 25 + 30 + 4 = (85)$$

### Problem 1 (30 points)

Design a counter using positive edge D flip-flops that will count as follows:

- when  $X=0$  and  $Y=0$ , the counter runs through the following states: 3,2,1,0,3,2,...
- when  $X=0$  and  $Y=1$ , the counter runs through the following states: 0,1,2,3,0,1,...
- when  $X=1$  and  $Y=d$ , the counter runs through the following states: 0,2,0,2,...

Draw a simplified circuit with a minimum number of flip-flops and a minimum network of AND, OR, NOT, and XOR gates.

**Note:** You can use the following Boolean Expression without proving it:

- $x \oplus y = \bar{x} \cdot \bar{y} + x \cdot y$

### Problem 2 (30 points)

A Moore state machine has an input  $w$  and an output  $z$ . The machine is a sequence detector that produces  $z = 1$  when it detects 01; otherwise  $z = 0$ .

- Draw the state diagram and provide the state-assigned table with the one-hot encoding approach. [10 points]
- Derive a simplified circuit from the state-assigned table using JK flip-flops. **Note:** Do not draw the simplified circuit but describe it with equations. [20 points]

### Problem 3 (30 points)

A Moore state machine has an input  $w$  and two outputs  $z1$ ,  $z2$ . The machine is a sequence detector that produces  $z1 = 1$  ( $z2 = 0$ ) when it detects 111 and  $z2=1$  ( $z1=0$ ) when it detects 101; otherwise  $z1$ ,  $z2 = 0$ .

- Draw the state diagram. [20 points]
- Provide the state table and the minimum state-assigned table. [10 points]

### Problem 4 (10 points)

A universal shift register can shift in both the left-to-right and right-to-left directions, can hold values and it has parallel-load capability. Draw a circuit for such a 2-bit universal shift register.

**Note:** The problem will NOT be graded if explanation is missing.

## Boolean Algebra Properties

5a.	$x \cdot 0 = 0$	10a.	$x \cdot y = y \cdot x$	<i>Commutative</i>
5b.	$x + 1 = 1$	10b.	$x + y = y + x$	
6a.	$x \cdot 1 = x$	11a.	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	<i>Associative</i>
6b.	$x + 0 = x$	11b.	$x + (y + z) = (x + y) + z$	
7a.	$x \cdot x = x$	12a.	$x \cdot (y + z) = x \cdot y + x \cdot z$	<i>Distributive</i>
7b.	$x + x = x$	12b.	$x + y \cdot z = (x + y) \cdot (x + z)$	
8a.	$x \cdot \bar{x} = 0$	13a.	$x + x \cdot y = x$	<i>Absorption</i>
8b.	$x + \bar{x} = 1$	13b.	$x \cdot (x + y) = x$	
9.	$\bar{\bar{x}} = x$	14a.	$x \cdot y + x \cdot \bar{y} = x$	<i>Combining</i>
		14b.	$(x + y) \cdot (x + \bar{y}) = x$	
		15a.	$\overline{x \cdot y} = \bar{x} + \bar{y}$	<i>DeMorgan's theorem</i>
		15b.	$\overline{x + y} = \bar{x} \cdot \bar{y}$	
		16a.	$x + \bar{x} \cdot y = x + y$	<i>Consensus</i>
		16b.	$x \cdot (\bar{x} + y) = x \cdot y$	
		17a.	$x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$	
		17b.	$(x + y) \cdot (y + z) \cdot (\bar{x} + z) = (x + y) \cdot (\bar{x} + z)$	



①

Present

Next

0 = 00

1 = 01

2 = 10

3 = 11

3, 2, 1, 0, 3, ...

0, 1, 2, 3, 0, ...

0, 2, 0, 2

I never write the same symbol for current and next states!

You have to mention that next state is equal to FF input  
 $D(t) = Q(t+1)$

we need eq. for the FF inputs!

26

X	Y	Present		Next	
		$n_1^{Q_1(t)}$	$n_2^{Q_2(t)}$	$n_1^{Q_1(t+1)}$	$n_2^{Q_2(t+1)}$
0	0	0	0	1	1
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	1	0
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	0	0
1	0	0	0	1	0
1	0	0	1	d	d
1	0	1	0	0	0
1	0	1	1	d	d
1	1	0	0	1	0
1	1	0	1	d	d
1	1	1	0	0	0
1	1	1	1	d	d

$Y=d$

$Y=d$

$n_1(n_{ext}) = \bar{n}_1 \cdot \bar{n}_2 \cdot \bar{Y} + Y \cdot \bar{n}_1 \cdot n_2 + \bar{n}_1 \cdot X + n_1 \cdot n_2 \cdot \bar{Y}$

$Y \backslash n_1 n_2$	00	01	11	10
00	1	0	1	1
01	0	1	d	d
11	1	0	d	d
10	0	1	0	0

$= \bar{Y}(\bar{n}_1 \oplus n_2) + Y \bar{n}_1 n_2 + \bar{n}_1 X$

Handwritten notes at the top of the page, possibly a title or header, including the word "Introduction" and some illegible text.


Handwritten notes in the lower-left section of the page, including the word "Conclusion" and several lines of illegible text.

$n_2(t+1)$ :

$n_1 n_2 \backslash XY$	00	01	11	10
00	1	1	0	0
01	0	0	d	d
11	0	0	d	d
10	1	1	0	0

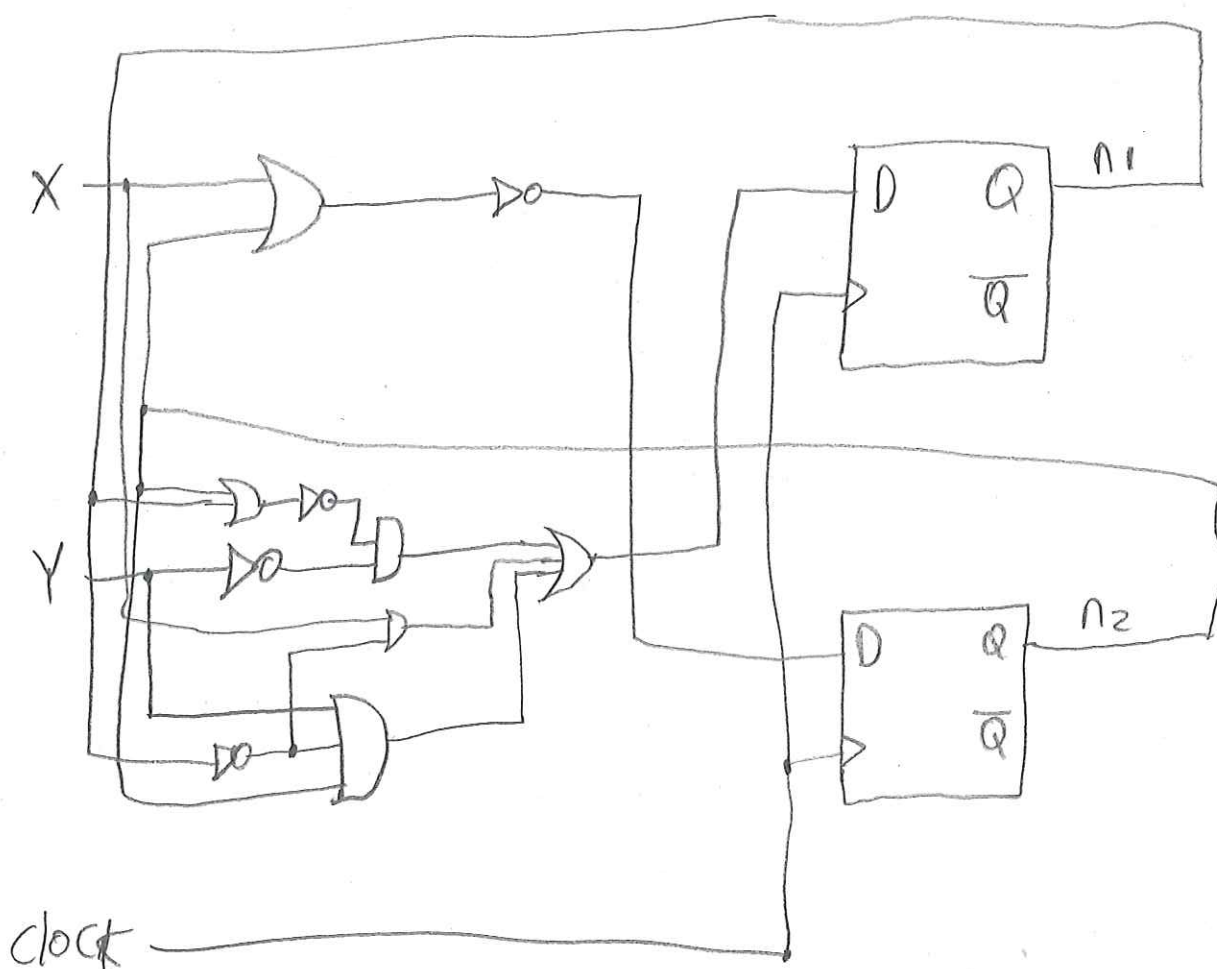(#1)

$$n_2(t+1) = \overline{n_2} \overline{X} = \overline{n_2 + X} = D_2(t)$$



Solution for  $D_1(t)$ : From truth table we observe:

For  $x=0$ :  $y=0$ :  $D_1(t) = \overline{Q_1(t) \oplus Q_2(t)}$

$y=1$ :  $D_1(t) = Q_1(t) \oplus Q_2(t)$

For  $x=1$ :  $D_1(t) = \overline{Q_1(t)}$

Therefore:  $D_1(t) = \overline{x} \cdot [\overline{y} \cdot (\overline{Q_1(t) \oplus Q_2(t)}) + y \cdot (Q_1(t) \oplus Q_2(t))] + x \cdot \overline{Q_1(t)} =$   
 $= \overline{x}(t) \cdot (\overline{y(t)} \oplus Q_1(t) \oplus Q_2(t)) + x \cdot \overline{Q_1(t)}$






②

$z = 1, 01, \text{ else, } z = 0$

④. state digram      state table      one hot encoding

state      nstate      output

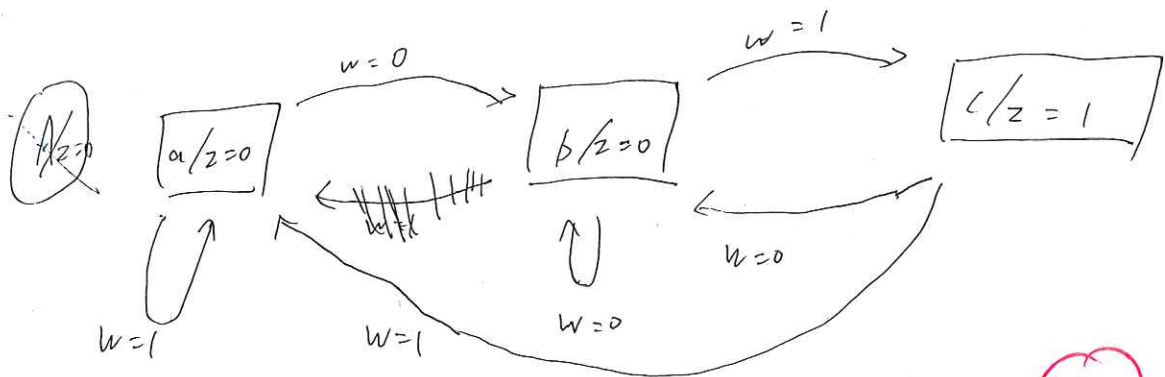

State Table:

Present States	Next States		Outputs
	W=0	W=1	
A	B	A	0
B	B	<del>B</del> C	0
C	B	A	1

10



A = 001

B = 010

C = 100

One hot Encoding

	p state	n states		output
		w=0	w=1	
00	A	010	001	0
01	B	010	100	0
10	C	010	001	1

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q(t)





present Next FF inputs

w	p state		Next state		J <sub>2</sub> K <sub>2</sub>		J <sub>1</sub> K <sub>1</sub>		Z
	y <sub>2</sub>	y <sub>1</sub>	y <sub>2</sub>	y <sub>1</sub>	J <sub>2</sub>	K <sub>2</sub>	J <sub>1</sub>	K <sub>1</sub>	
0	0	0	0	1	0	d	1	d	0
0	0	1	0	1	0	d	d	0	0
0	1	0	0	1	d	1	1	d	1
0	1	1	d	d	d	d	d	d	d
1	0	0	0	0	0	d	0	d	0
1	0	1	1	0	1	d	d	1	0
1	1	0	0	0	d	1	0	d	1
1	1	1	d	d	d	d	d	d	d

Q	Q(t+1)	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

$J_2 = w \cdot y_1$

w \ y <sub>2</sub>	00	01	11	10
y <sub>1</sub> 0	0	d	d	0
y <sub>1</sub> 1	0	d	<b>d</b>	<b>1</b>

$K_2 = 1$

w \ y <sub>2</sub>	00	01	11	10
y <sub>1</sub> 0	d	1	1	d
y <sub>1</sub> 1	d	d	d	d

$J_1 = \bar{w}$

w \ y <sub>2</sub>	00	01	11	10
y <sub>1</sub> 0	<b>1</b>	<b>1</b>	0	0
y <sub>1</sub> 1	d	d	d	d

$K_1 = w$

w \ y <sub>2</sub>	00	01	11	10
y <sub>1</sub> 0	d	d	d	d
y <sub>1</sub> 1	0	d	d	1

you have to use the state assign table from a!

w	y <sub>2</sub>		Z	
	00	01	11	10
y <sub>1</sub> 0	0	<b>1</b>	<b>1</b>	0
y <sub>1</sub> 1	0	d	d	0

$Z = Y_2$

15




# Problem 3

$$111 - z_1 = 1, z_2 = 0$$

$$101 - z_1 = 0, z_2 = 1$$

both 0  
otherwise

a.

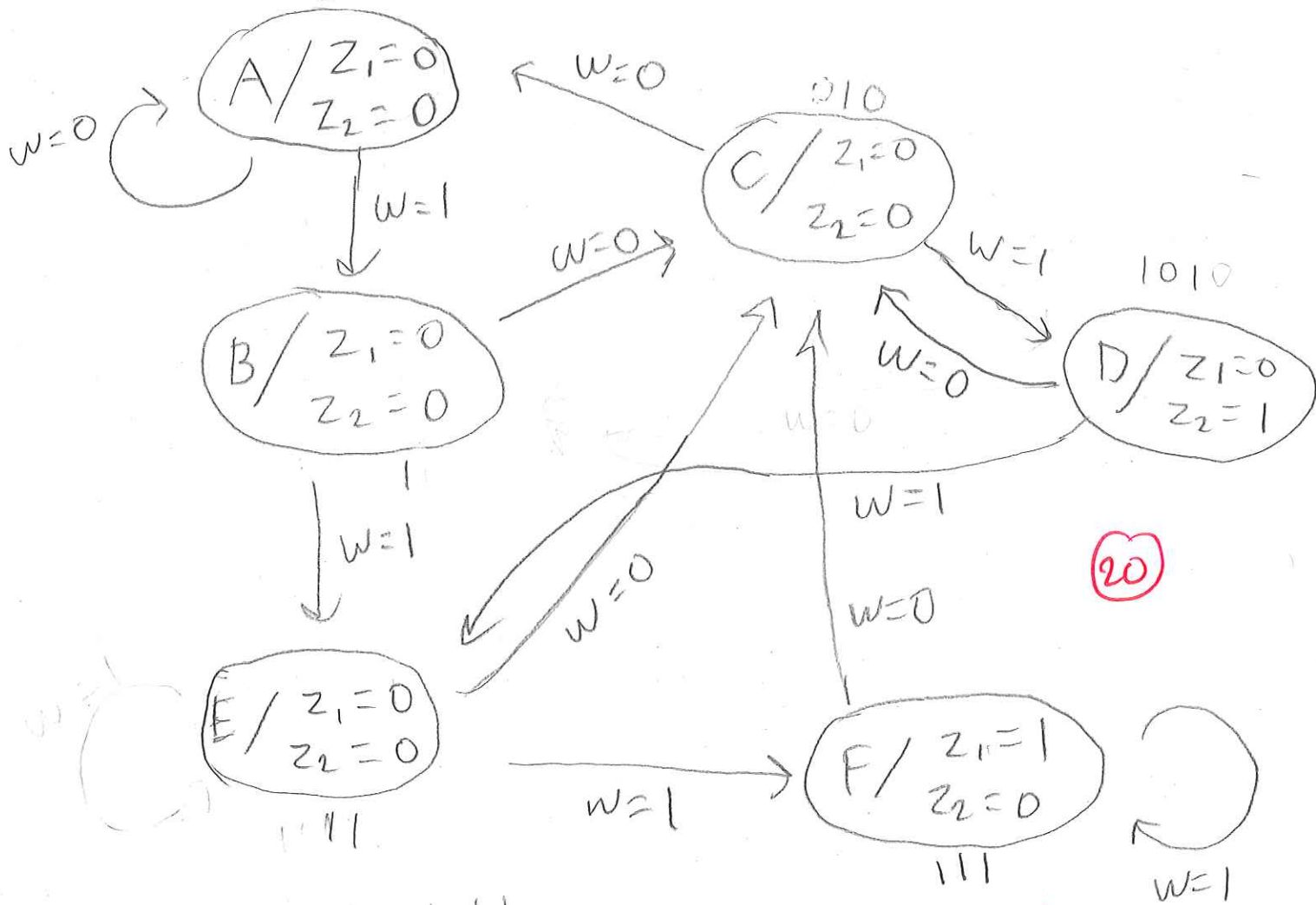

b.

State table

Current State	Next state		Output	
	$w=0$	$w=1$	$z_1$	$z_2$
A	A	B	0	0
B	C	E	0	0
C	A	D	0	0
D	C	E	0	1
E	C	F	0	0
F	C	F	1	0



# Problem 3

b. cont,

	Current state			Next state						Output	
	$y_2$	$y_1$	$y_0$	$w=0$			$w=1$			$z_1$	$z_2$
	$y_2$	$y_1$	$y_0$	$y_2$	$y_1$	$y_0$	$y_2$	$y_1$	$y_0$	$z_1$	$z_2$
A	0	0	0	0	0	0	0	0	1	0	0
B	0	0	1	0	1	0	1	0	0	0	0
C	0	1	0	0	0	0	0	1	1	0	0
D	0	1	1	0	1	0	1	0	0	0	1
E	1	0	0	0	1	0	1	0	1	0	0
F	1	0	1	0	1	0	1	0	1	1	0
X	1	1	0	d	d	d	d	d	d	d	d
X	1	1	1	d	d	d	d	d	d	d	d






# Problem 4

- 2 bits
- shift left 01
- shift right 10
- hold 00
- parallel load 11

$w_1$	$w_0$	Action
0	0	Hold
0	1	Shift left
1	0	Shift right
1	1	Parallel load

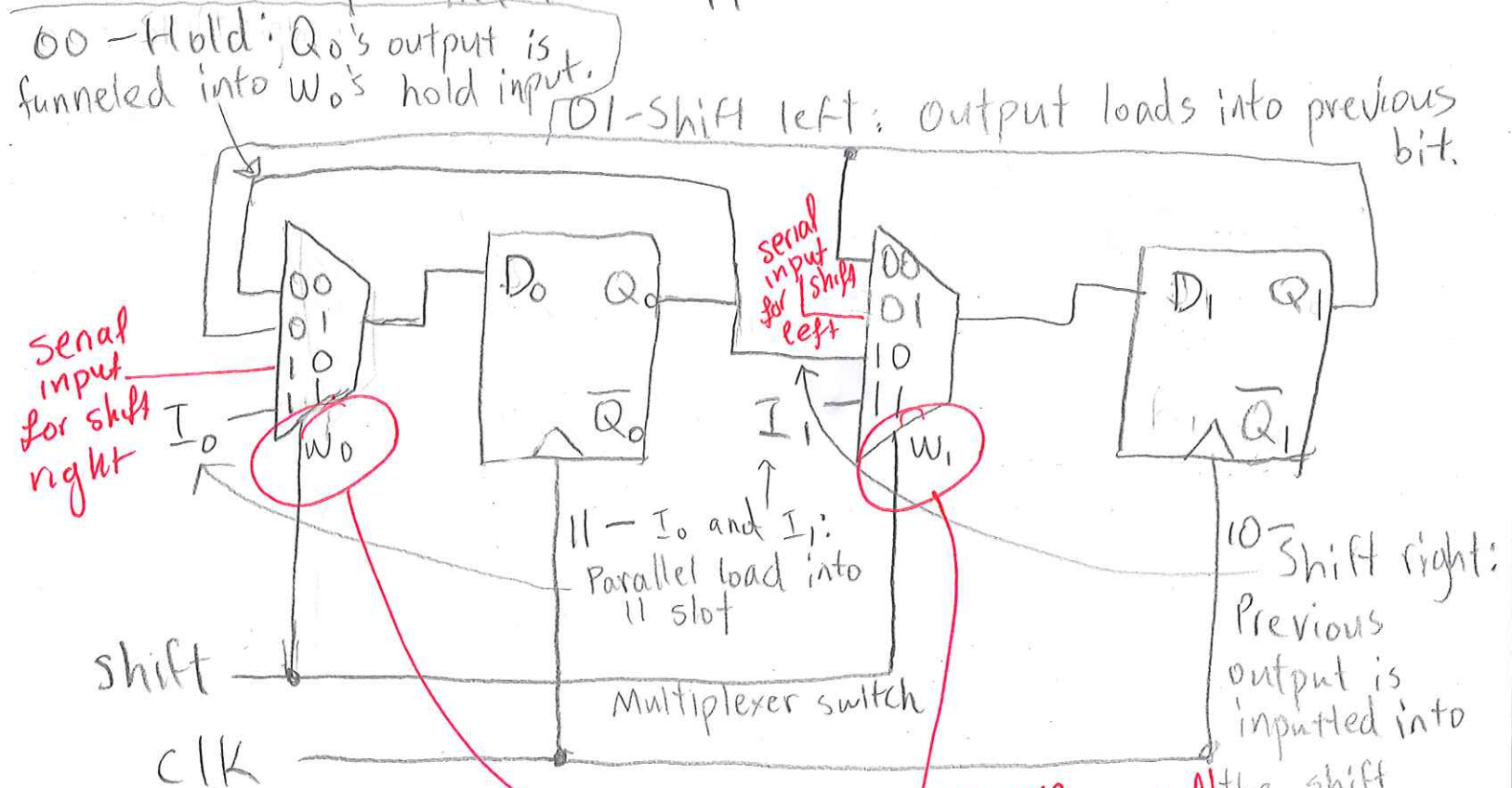

~~D0's 10 is empty because there is nothing to "shift right" into its mux. D1's 01 is also empty bc there is nothing on its right, to "shift left" from.~~

wrong!

4

PLEASE REVIEW MY HW SOLUTIONS  
AND HW FEEDBACK!

