

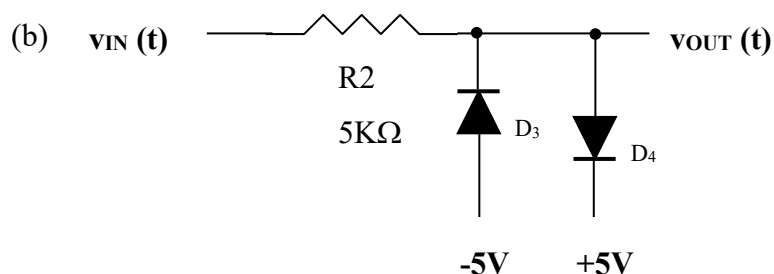


SANTA CLARA UNIVERSITY	ELEN 115 – Spring 2023	S. Krishnan
Homework #6		

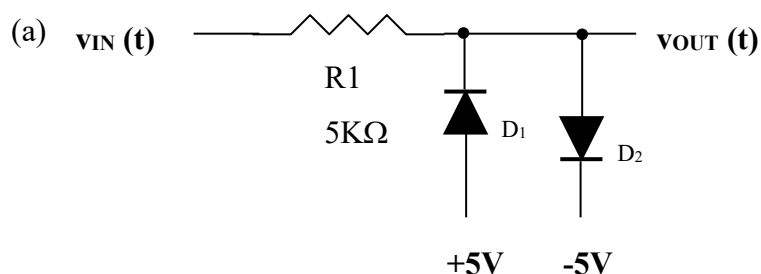1. For each circuit, the diodes are ideal.
  - (i) Clearly explain how the circuit functions by showing conditions when each diode is on and when it is off.
  - (ii) For his design plot the transfer characteristic  $v_{INB}$  versus  $v_{IN}$  indicating the values of all significant points and the values of the slopes of all segments
  - (iii) Which of these circuits **DOES** function as a diode clamp that keeps the output voltage between -5 and +5 volts. **Explain your answer.**
  - (iv) Which of these circuits **DOES NOT** function as a diode clamp that keeps the output voltage between -5 and +5 volts. **Explain your answer.**



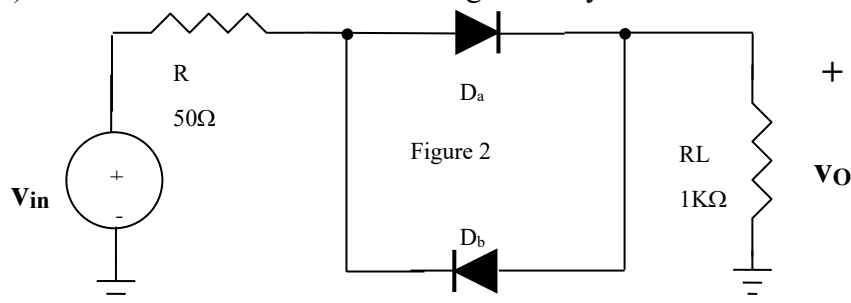
2. A young design engineer decides to try a new configuration for a rectifier. His attempt is the circuit shown in Figure 2 where identical diodes  $D_a$  and  $D_b$  are used. Assume diodes are ideal. The designer gives the input  $v_{in} = 5\sin 4\pi t$  to the circuit.
  - (i) For each half cycle indicate the ON and OFF state of the diodes.
  - (ii) Draw the input voltage and the corresponding output voltage  $v_o$  vs. time.
  - (iii) Find the average value of the output voltage.
  - (iv) Is this rectifier efficient? Explain your answer.
  - (v) Find the peak diode current in each diode.
  - (vi) Find the maximum reverse voltage seen by each diode.



3. 4.74

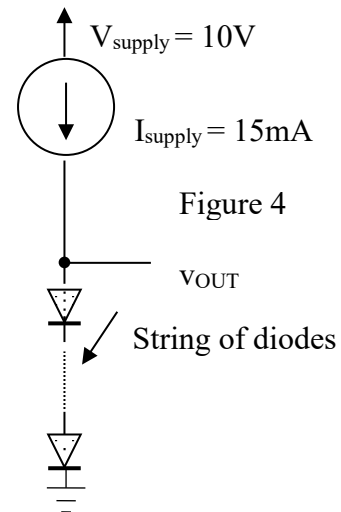4. A designer has to build a regulator circuit as shown in Figure 4 to provide an output voltage  $V_{OUT}$  of 5V using one of two types of diodes. Given that **both types of diodes** have a voltage of 0.715V at 1mA current. For the diode of **TYPE A** the voltage changes by 0.1V/decade change in current while for the diode of **TYPE B** the voltage increases by 0.1V when the current through it doubles. **Do not assume the values for  $V_T$ .**

- Which type of diode should the designer pick for building an efficient regulator?  
Clearly explain the reasons for your choice.
- How many diodes of the type chosen in (a) would be in the string to obtain the required  $V_{OUT}$  at nominal  $I_{supply}$  and no load condition.
- Find the **percentage change** in  $V_{OUT}$  when a load current of 5mA is drawn from the circuit.



5. The regulator in Figure 5 employs a zener diode  $D_Z$  that is specified to have a 8V drop at a test current of 25mA with  $r_z = 10\Omega$  and  $I_{ZK} = 0.2mA$ .

- Find **the value of R** needed to obtain an output voltage  $V_{out} = 7.8V$  at nominal supply voltage  $V_s$  and no load.
- With the value of R as obtained in (a) and nominal  $V_s$  find the **the value of  $V_{out}$**  with a load resistance of
  - $R_L = 10k\Omega$
  - $R_L = 1k\Omega$

